

Lab 3: Motion

For the rest of this semester you will be designing SIXT33N, a mischievous little robot who *might* just do what you want - if you design it correctly. Our end goal is to have SIXT33N listen to your voice commands and execute the corresponding drive command. Over the course of this semester, we will be implementing different parts of this project, from the circuits to the algorithms necessary for voice classification and control. In Lab 2, you learned about digital/analog interfaces, which is how your Launchpad, which will serve as the brain of SIXT33N, collects information from and interacts with the world. In this lab, **you will build SIXT33N's legs**: you will build the motor control circuits that enable SIXT33N to move around (the "legs") and the encoder circuits that enable your Launchpad to detect how far and fast SIXT33N has moved.

The goals of this phase are as follows:

- Construct motor controller circuits
- Construct encoder circuits
- Test encoder circuits

Part 1: Motor Drivers

SIXT33N uses 9V DC motors. This means the maximum voltage that can be delivered to the motors is 9V, but the motors will move (albeit more slowly) with voltages less than 9V. There is some minimum voltage required to deliver enough power to the motors to overcome the static friction and start them, but after that point, we treat the motor speed as approximately linear with the applied voltage (this will be the basis of the system model you develop in the next lab).

Because it is difficult to use the Launchpad to control a true DC signal within 0V and 3.3V (e.g. 2.2V), we will instead make use of its PWM function. A PWM, or pulse-width modulation, signal is a square wave with a variable duty cycle D (the proportion of a cycle period for which the power source is turned on, or logic HIGH) shown in Figure 1. PWM is used to digitally change the average voltage delivered to a load by varying the duty cycle. If the frequency is large enough, the on-off switching is imperceptible, but the average voltage (V_{AVG}) delivered to the load changes proportionally with the duty cycle, as shown in the figure. Hence, changing the duty cycle corresponds to changing the DC voltage supplied to the motor. For example, you can get an average voltage of 2.2V by setting the duty cycle to $\frac{2.2}{3.3} = 66\%$.

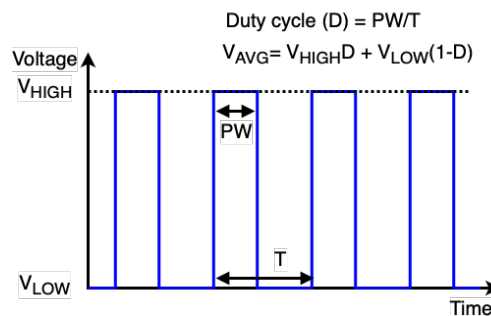


Figure 1: PWM Signal

We will use the Launchpad's PWM pins to set the duty cycle for each motor's PWM signal. However, the Launchpad's logical HIGH¹ voltage is 3.3V, which is not enough to directly drive the motors: even if your motor does turn on at 3.3V when you test it with the power supply, the Launchpad cannot supply enough current to power the motors (the motors each need 100-200 mA to run, while the Launchpad can only supply 20-30 mA from its pin). This is where the motor driver circuits come in.

¹The logic-level signals are denoted as HIGH and LOW, where HIGH=3.3V and LOW=0V for the Launchpad.

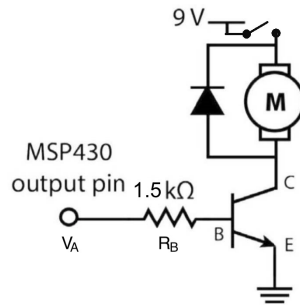


Figure 2: Motor Controller Circuits

The PWM pin from the Launchpad is connected via a resistor to the “Base (B)” of an NPN BJT (bipolar junction transistor). This transistor, in reality, behaves a bit differently from the NMOS with which you are familiar, but for this class, you may assume that it is functionally the same as an NMOS, behaving as a voltage-controlled switch. On the BJT, the three terminals are analogous to those of an NMOS: the “Base (B)” is the gate, the “Collector (C)” is the drain, and the “Emitter (E)” is the source. The reason the resistor is there is because, unlike MOS transistors, there is a current flowing into the “Base (B)” terminal of the BJT which directly affects the current flowing through the “Collector (C)” terminal. We use the resistor to limit this base current in order to protect both the BJT itself and the Launchpad pin supplying the current.

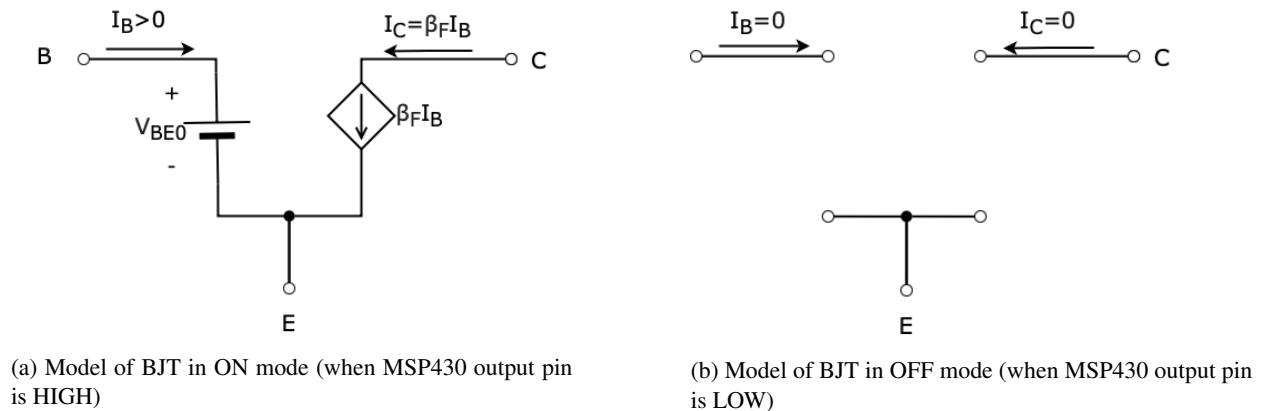


Figure 3: Model of NPN BJT in Different Modes

The BJT in Figure 2 is switching between the **ON** and **OFF** modes when the MSP430 output pin V_A is HIGH (3.3V) and LOW (0V) respectively. The model for both ON and OFF states are shown in Figure 3. When the BJT turns on, V_{BE} can be modeled as a fixed voltage source between the Base and Emitter terminals with a voltage value of V_{BE0} , which is usually between 0.6V to 0.8V. In ON mode, there is a **Current Controlled Current Source** modeled between the “Collector (C)” and “Emitter (E)”, i.e., current at the “Collector (C)” is an amplified version of current at the “Base (B)” (notice that I_B has to flow into the “Base (B)” for the relation $I_C = \beta_F I_B$ to hold.) β_F is called the **Common-Emitter Current Gain**. When the MSP430 output pin V_A is HIGH (3.3V), the voltage across the resistor R_B in Figure 2 is $V_{HIGH} - V_{BE0}$. So we can calculate the current flowing into the “Base (B)”, I_B , and the current flowing into the “Collector (C)”, I_C , as

$$I_B = \frac{V_{HIGH} - V_{BE0}}{R_B} \quad (1)$$

$$I_C = \beta_F I_B = \beta_F \frac{V_{HIGH} - V_{BE0}}{R_B} \quad (2)$$

From equations above, we know that the resistor in the motor controller circuit (Figure 2) is used for defining the current flow through the MSP430 output pin, BJT, and motor. Therefore, we should carefully choose the value of the resistor considering the maximum current that BJT and MSP430 pin can handle and the current required to drive the motor. As we increase the value of the resistor, the current into the “Base (B)” decreases, which in turn reduces the current flow through the motor, slowing down the motor rotation.

Ignoring the diode in the schematic, the low-power, low-voltage signal from the Launchpad switches the BJT on and off: when the Launchpad signal is HIGH (3.3V), the BJT is on, we have $9V - V_{CE}$ dropped across the motor (V_{CE} is the voltage across the current control current source in Figure 3a) and current can flow through the motor and BJT. When the Launchpad signal is LOW (0V), the BJT is off. As shown in Figure 3b, the BJT is open at all terminals. Therefore, no current is allowed to flow into the motor and there is no voltage drop across the motor (0V). Our Launchpad PWM wave that only spanned 0V-3.3V thus has been amplified to a signal that roughly spans 0V-9V (neglecting the V_{CE}) across the motor! Note that because the voltage dropped across the motor is HIGH (9V) when the Launchpad PWM is HIGH (3.3V) and LOW (0V) when the Launchpad PWM is LOW (0V), the PWM of the voltage dropped across the motor has the same duty cycle as the Launchpad PWM. By changing the duty cycle of the Launchpad PWM, we can thus modulate the average voltage across the motor to a voltage between 0V to 9V, and therefore change its speed.


Moreover, the BJT is capable of handling far more current than the Launchpad pins can tolerate, allowing the necessary hundreds of mA to flow through the motor so it can run. The Launchpad only needs to supply the small amount of current the BJT needs flowing into its base terminal to function (this is a key difference between the NPN BJT and NMOS) and the BJT will amplify that current to be used by the motor. With this circuit, we have thus supplied the motor with a high-power PWM signal.

You may be wondering why we have the diode connected across the motor. We add this diode because motors have inductive properties; the current flowing through the motor cannot change instantaneously. When we turn off the BJT, we are cutting off all current from flowing through the BJT. Above, where we ignored the diode, we assumed the motor could instantly go from an ON to OFF state. However, because the motor has inductive properties, if we did not have the diode in the circuit, the current through the motor would have to instantaneously drop from hundreds of mA (ON) to 0A (OFF), causing a huge voltage spike at the Collector of the BJT, which would be disastrous. In order to prevent this from happening, we add the diode as a pathway to allow current to flow through it when the BJT is turned off, enabling the current to drop over time instead of instantaneously. Once the current decreases sufficiently, the diode turns off, and the motor is just connected to an open circuit, meaning no current will flow across the motor. This results in no voltage drop across the motor.

We have simplified our analysis and description of the different components we use in the motor circuit drastically so as to remain in scope for this class. If you would like to learn more about these components after doing the lab, please read the [extra reading note](#) for this lab for more information.

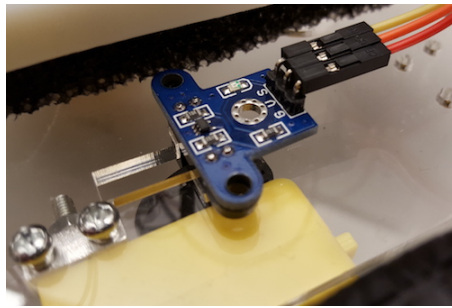Part 2: Encoders

The encoders we will be using in our labs are called photointerruptors. As a wheel on the car turns, there is an encoder disc with cutouts in it that turns with the wheel. The encoder shines a light between its two “legs”, and as the wheel turns between them, the beam of light is interrupted by the spokes of the encoder disc at a rate proportional to the velocity of the car. The Launchpad is therefore able to detect how fast the wheel is turning by looking at the number of times that the encoder records an interruption in the beam of light, which is what we call a “tick”, over a specific time interval.



(a) Top view of encoders



(b) Bottom view of encoders

Figure 4: Encoders

From an electrical point of view, the way the Launchpad interacts with the encoder is with different voltage levels. When the beam of light is unblocked, the encoder's signal pin (S), which the Launchpad takes as input, will output a logic HIGH voltage (roughly 3.3V). When the beam of light is blocked, the encoder's signal pin outputs a logic LOW voltage (roughly 0V). As the wheel rotates and causes the encoder disc to repeatedly block and unblock the beam, the encoder will repeatedly output alternating logic HIGH and LOW signals, generating a square wave. By counting the raw number of rising edges (logic LOW to logic HIGH) or falling edges (logic HIGH to logic LOW) and counting the number of edges that arrive during a specified period of time, the Launchpad can determine how far the car has driven and how fast it's moving, respectively.


For this lab, we have given you a .ino file for you to use to test your encoders with. It cycles through 4 tests: neither wheels move, left wheel moves, right wheel moves, and both wheels move. The purpose of the first phase is to ensure that your encoders don't generate any readings if you aren't moving at all. You will run this test twice: once with your encoder discs removed, and once with your encoder discs on. You need to run it once with your encoder discs removed so we don't get any false positives; we don't want your encoder to be generating any readings if there's nothing there to interrupt the beam of light in the first place.

Written by Mia Mirkovic (2019)

Edited by Steven Lu, Yi-Hsuan Shih (2021). Version 2.0, 2021


Edited by Steven Lu (2022). Version 3.0, 2022

Appendix A: Resistor Codes

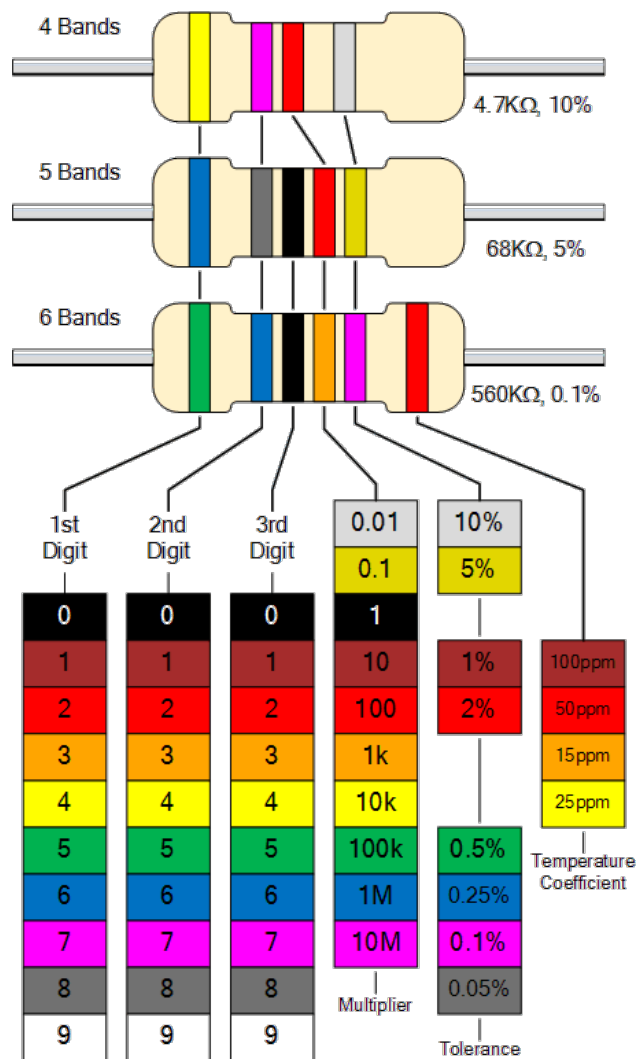

Appendix B: Capacitor Codes

Capacitors

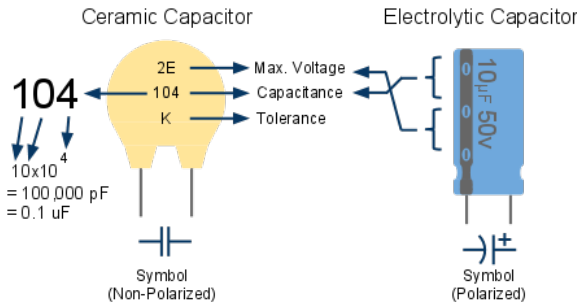

Max. Operating Voltage	
Code	Max. Voltage
1H	50V
2A	100V
2T	150V
2D	200V
2E	250V
2G	400V
2J	630V

Capacitance Conversion Values		
Microfarads (μF)	Nanofarads (nF)	Picofarads (pF)
0.000001 μF	0.001 nF	1 pF
0.00001 μF	0.01 nF	10 pF
0.0001 μF	0.1 nF	100 pF
0.001 μF	1 nF	1,000 pF
0.01 μF	10 nF	10,000 pF
0.1 μF	100 nF	100,000 pF
1 μF	1,000 nF	1,000,000 pF
10 μF	10,000 nF	10,000,000 pF
100 μF	100,000 nF	100,000,000 pF

Tolerance	
Code	Percentage
B	± 0.1 pF
C	± 0.25 pF
D	± 0.5 pF
F	$\pm 1\%$
G	$\pm 2\%$
H	$\pm 3\%$
J	$\pm 5\%$
K	$\pm 10\%$
M	$\pm 20\%$
Z	+80%, -20%

References

Original Project Part 1 notebook written by Nathaniel Mailoa and Emily Naviasky (2016).

Horowitz, P. and Hill, W. (2015). *The Art of Electronics*. 3rd ed. Cambridge: Cambridge University Press, ch 4.

Horowitz, P. and Hill, W. (2015). *The Art of Electronics*. 3rd ed. Cambridge: Cambridge University Press, ch 2.

Sedra, A. S. and Smith, K. C. (2015). *Microelectronic Devices and Circuits*. 7th ed. Oxford: Oxford University Press, ch 3.

Sedra, A. S. and Smith, K. C. (2015). *Microelectronic Devices and Circuits*. 7th ed. Oxford: Oxford University Press, ch 6.

<https://www.electronics-tutorials.ws/wp-content/uploads/2018/05/resistor-res5.gif>

<https://www.bragitoff.com/wp-content/uploads/2015/09/CapacitorsCheatSheet.png>