

# **EE16B**

# **Designing Information**

# **Devices and Systems II**

**Lecture 3B**


**RLC circuits and 2nd Order Diff EQ**

# Announcements

---

- Last time:
  - Transistors Switch RC model
  - Finish review of complex numbers
    - Euler Formula
  - Solution for sinusoidal input
- Today:
  - Second order systems
  - Intro to VDE
  - RLC circuits
  - Resonant Tank

# Example 1: RLC Circuits

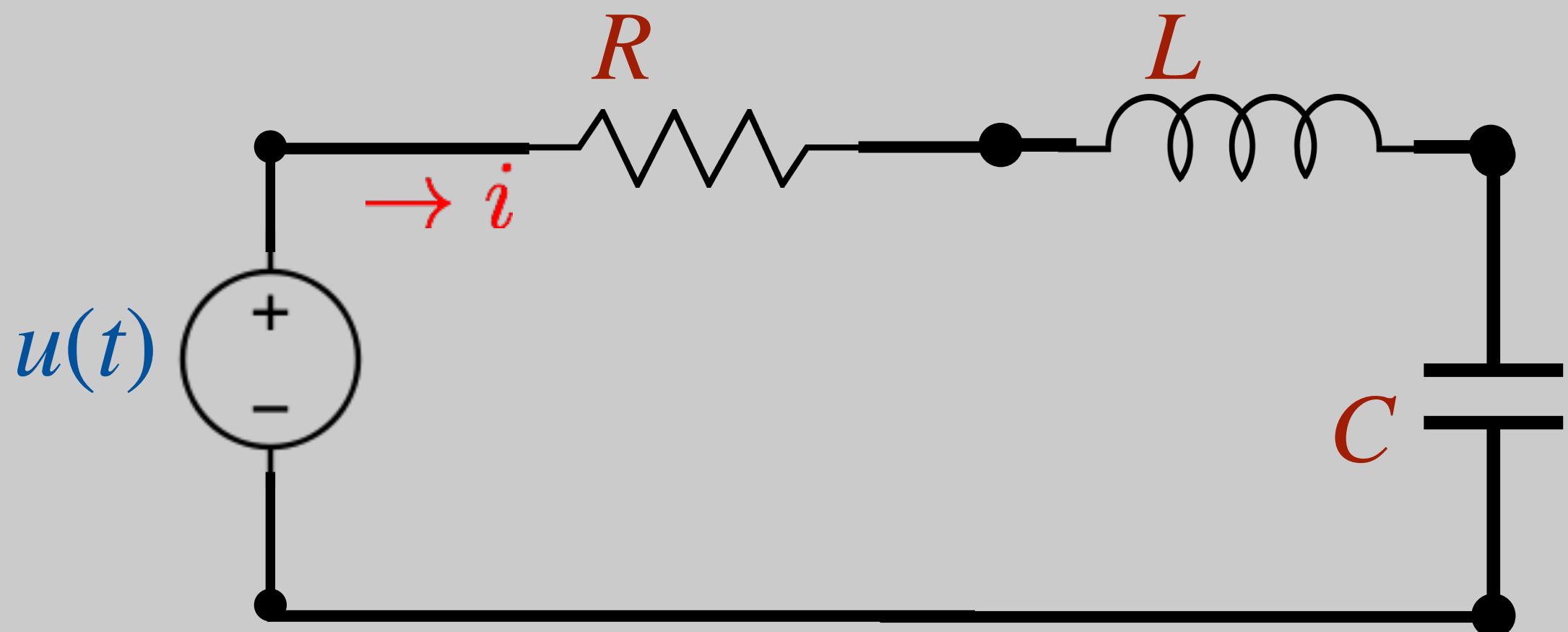


From KVL:  $V_R + V_L + V_C = u$

$$L \frac{di(t)}{dt} = V_L = u - V_c - V_R = u - V_c - Ri$$

$$C \frac{dV_C(t)}{dt} = i$$



# Example 1: RLC Circuits

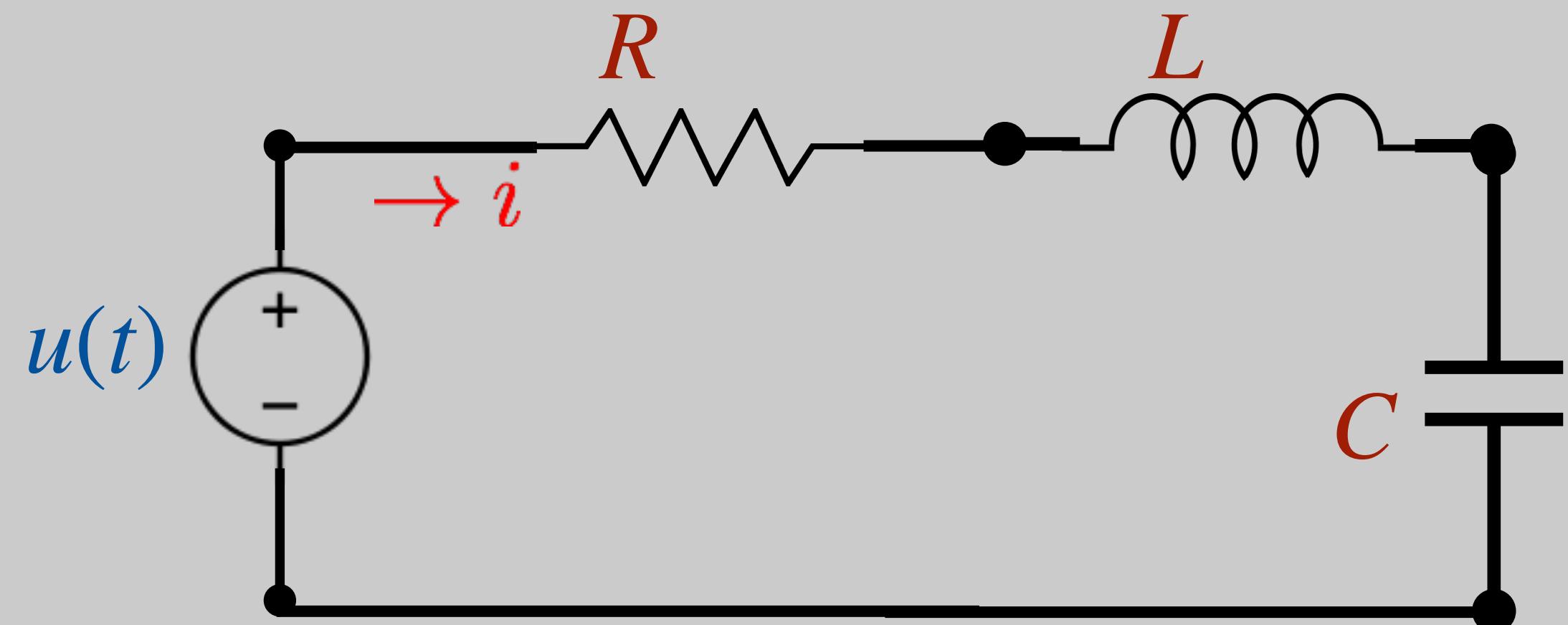

From KVL:  $V_R + V_L + V_C = u$

$$L \frac{di(t)}{dt} = V_L = u - V_c - V_R = u - V_c - Ri$$

$$C \frac{dV_C(t)}{dt} = i$$

$$\frac{d}{dt} V_c(t) = \frac{1}{C} i(t)$$

$$\frac{d}{dt} i(t) = -\frac{1}{L} V_c(t) - \frac{R}{L} i(t) + \frac{1}{L} u(t)$$

# Example 1: RLC Circuits

Two (coupled) 1st order Diff. EQ!

Write in matrix form:

$$\begin{bmatrix} \frac{d}{dt}V_{c_1} \\ \frac{d}{dt}i_2 \end{bmatrix} = \begin{bmatrix} & \\ & \end{bmatrix} \begin{bmatrix} V_c \\ i \end{bmatrix} + \begin{bmatrix} & \\ & \end{bmatrix} u(t)$$

$$\frac{d}{dt}V_c(t) = \frac{1}{C}i(t)$$
$$\frac{d}{dt}i(t) = -\frac{1}{L}V_c(t) - \frac{R}{L}i(t) + \frac{1}{L}u(t)$$

# Example 1: RLC Circuits

Two (coupled) 1st order Diff. EQ!

Write in matrix form:

$$\begin{bmatrix} \frac{d}{dt}V_{c_1} \\ \frac{d}{dt}\vec{i} \end{bmatrix} = \begin{bmatrix} 0 & \frac{1}{C} \\ -\frac{1}{L} & -\frac{R}{L} \end{bmatrix} \begin{bmatrix} V_c \\ i \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{L} \end{bmatrix} u(t)$$

$$\frac{d}{dt}\vec{x}(t) \quad A$$

$$\vec{x}(t) \quad \vec{B}$$

$$\frac{d}{dt}V_c(t) = \frac{1}{C}i(t)$$
$$\frac{d}{dt}i(t) = -\frac{1}{L}V_c(t) - \frac{R}{L}i(t) + \frac{1}{L}u(t)$$

# VDE / State Space

---

$$\begin{bmatrix} \frac{d}{dt}V_{c_1} \\ \frac{d}{dt}V_{c_2} \end{bmatrix} = \begin{bmatrix} 0 \\ -\frac{1}{L} \end{bmatrix} + \begin{bmatrix} \frac{1}{C} \\ -\frac{R}{L} \end{bmatrix} \begin{bmatrix} V_c \\ i \end{bmatrix} + \begin{bmatrix} 0 \\ \frac{1}{L} \end{bmatrix} u(t)$$

General Case:

$$\frac{d}{dt}\vec{x}(t) = A\vec{x}(t) + Bu(t)$$

Also called state-space (more in week 6!)

Q: How to solve for  $\vec{x}(t)$ ?

# Change of Variables - diagonalization

$$\frac{d}{dt} \vec{x}(t) = A\vec{x}(t) + Bu(t)$$

Let  $T$  be an invertible matrix:  $\vec{z}(t) = T\vec{x}(t) \Leftrightarrow \vec{x}(t) = T^{-1}\vec{z}(t)$

Then,

$$\begin{aligned} \frac{d}{dt} \vec{z}(t) &= T \frac{d}{dt} \vec{x}(t) = TA\vec{x}(t) + TBu(t) \\ &= TAT^{-1}\vec{z}(t) + TBu(t) \end{aligned}$$

Choose  $T$ , such that  $A_{\text{new}} = TAT^{-1}$  is diagonal!

$$\frac{d}{dt} \vec{z}(t) = A_{\text{new}} \vec{z}(t) + B_{\text{new}} u(t)$$

## Change of Variables - diagonalization

$$\frac{d}{dt} \vec{z}(t) = A_{\text{new}} \vec{z}(t) + B_{\text{new}} u(t)$$

$$A_{\text{new}} = \begin{bmatrix} \lambda_1 & 0 & \cdots & 0 \\ 0 & \lambda_2 & \cdots & 0 \\ & & \ddots & \\ 0 & 0 & \cdots & \lambda_n \end{bmatrix}$$

$$\frac{d}{dt} \vec{z}(t) = \begin{bmatrix} \boxed{\lambda_1 & 0 & \cdots & 0} \\ 0 & \lambda_2 & \cdots & 0 \\ & & \ddots & \\ 0 & 0 & \cdots & \lambda_n \end{bmatrix} \vec{z}(t) + \underbrace{v(t)}_{B_{\text{new}} u(t)} = B_{\text{new}} u(t)$$


$$\frac{d}{dt} z_1(t) = \lambda_1 z_1(t) + v_1(t)$$

Go back to original variable by:  $\vec{x}(t) = T^{-1} \vec{z}(t)$
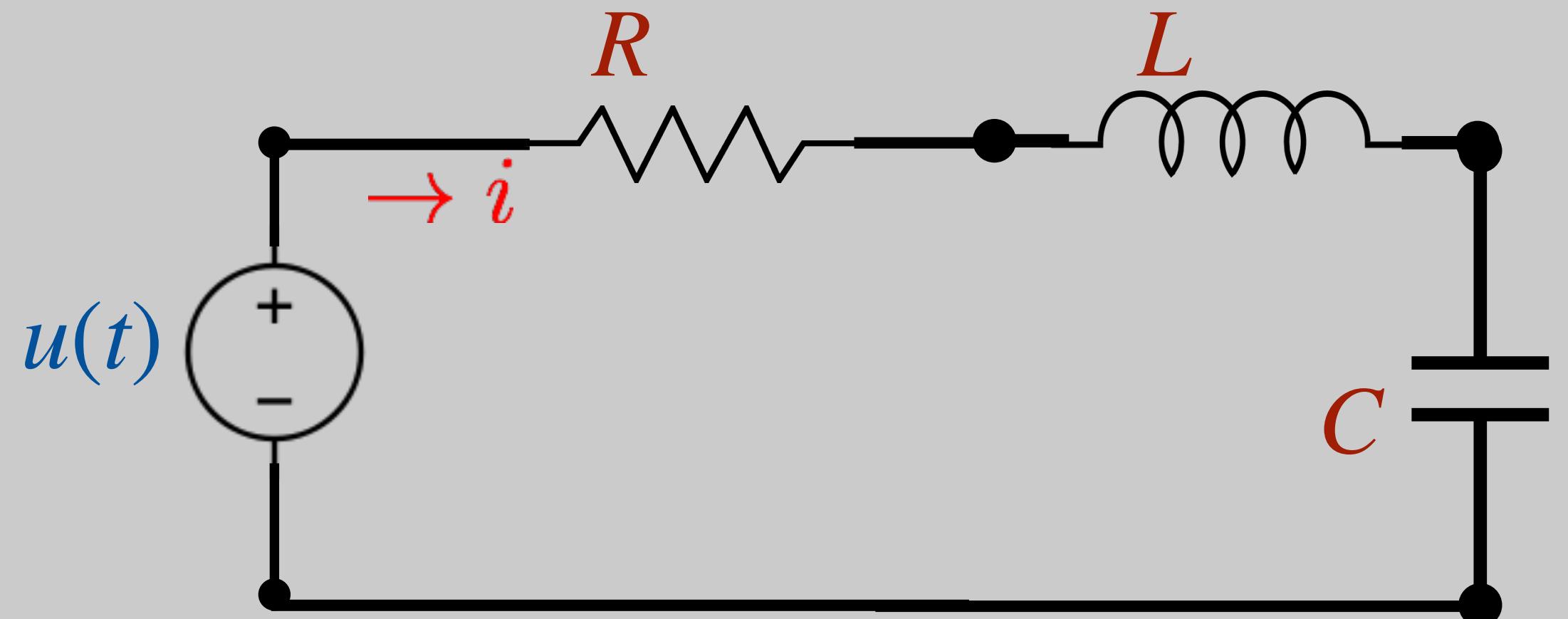
# Back to the RLC circuit

$$(1) \frac{d}{dt}V_c(t) = \frac{1}{C}i(t)$$

$$(2) \frac{d}{dt}i(t) = -\frac{1}{L}V_c(t) - \frac{R}{L}i(t) + \frac{1}{L}u(t)$$



Time derivative of (1)

$$\Rightarrow \frac{d^2}{dt^2}V_c(t) = \frac{1}{C} \frac{d}{dt}i(t) = -\frac{1}{LC}V_c(t) - \frac{R}{LC}i(t) + \frac{1}{LC}u(t)$$

Substitute (2)

$$\begin{aligned} \text{Substitute (1)} \\ &= -\frac{1}{LC}V_c(t) - \frac{RC}{LC} \frac{d}{dt}V_c(t) + \frac{1}{LC}u(t) \end{aligned}$$

$$\frac{d^2}{dt^2}V_c(t) + \frac{R}{L} \frac{d}{dt}V_c(t) + \frac{1}{LC}V_c(t) = \frac{1}{LC}u(t)$$

One 2nd order Diff. EQ!

# Homogeneous Solution

$$\frac{d^2}{dt^2}V_c(t) + \frac{R}{L}\frac{d}{dt}V_c(t) + \frac{1}{LC}V_c(t) = 0$$


Define:

$$\alpha = \frac{R}{2L} \quad \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\frac{d^2}{dt^2}V_c(t) + 2\alpha\frac{d}{dt}V_c(t) + \omega_0^2V_c(t) = 0$$

$$As^2e^{st} + 2\alpha Ase^{st} + \omega_0^2Ae^{st} = 0$$

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

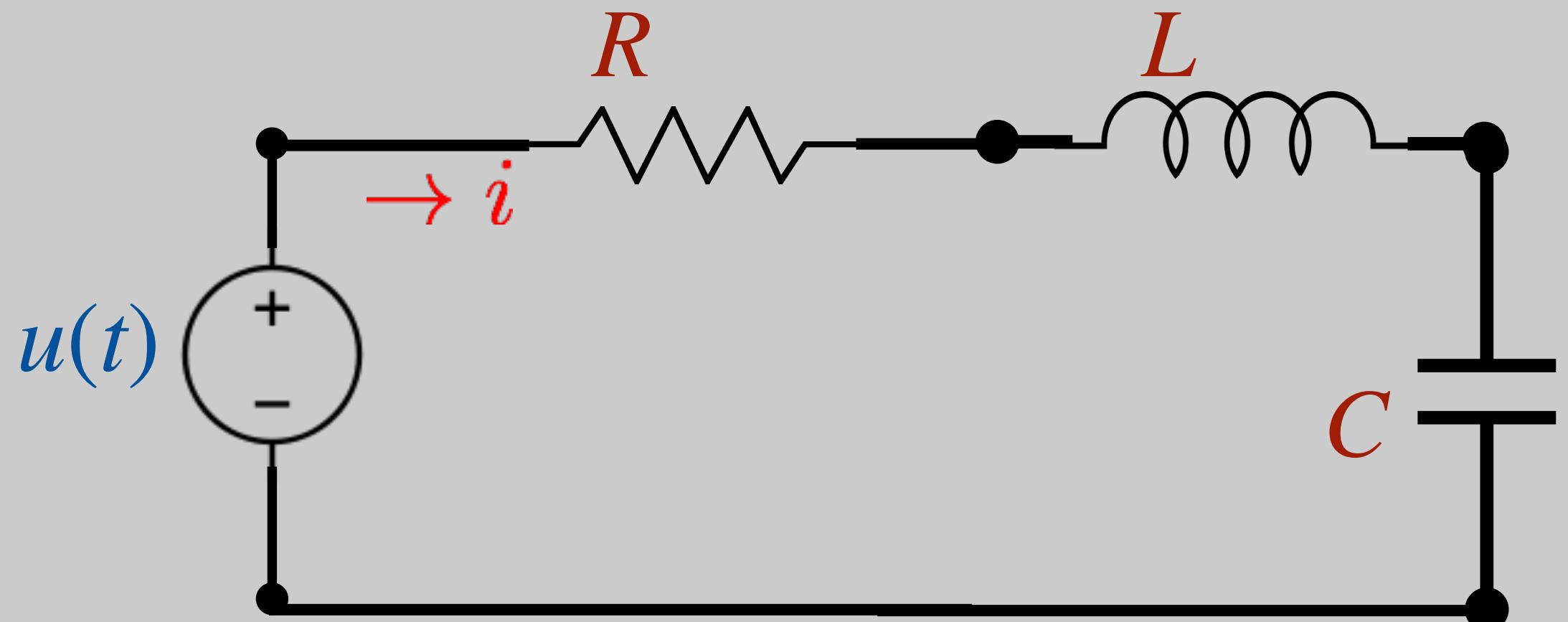

Guess:  $V_c(t) = Ae^{st}$

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

# Homogeneous Solution

$$\frac{d^2}{dt^2}V_c(t) + 2\alpha \frac{d}{dt}V_c(t) + \omega_0^2 V_c(t) = 0$$

$$a = \frac{R}{2L}$$


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\zeta = \frac{\alpha}{\omega_0}$$

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

- |  |                           |                                  |
|--|---------------------------|----------------------------------|
| $\alpha > \omega_0, \zeta > 1 \Rightarrow$ | 2 real solutions          | $\Rightarrow$ Exponential decay  |
| $\alpha = \omega_0, \zeta = 1 \Rightarrow$ | 2 same solutions          | $\Rightarrow$ Exponential decay  |
| $\alpha < \omega_0, \zeta < 1 \Rightarrow$ | 2 complex conj. solutions | $\Rightarrow$ decay+oscillations |

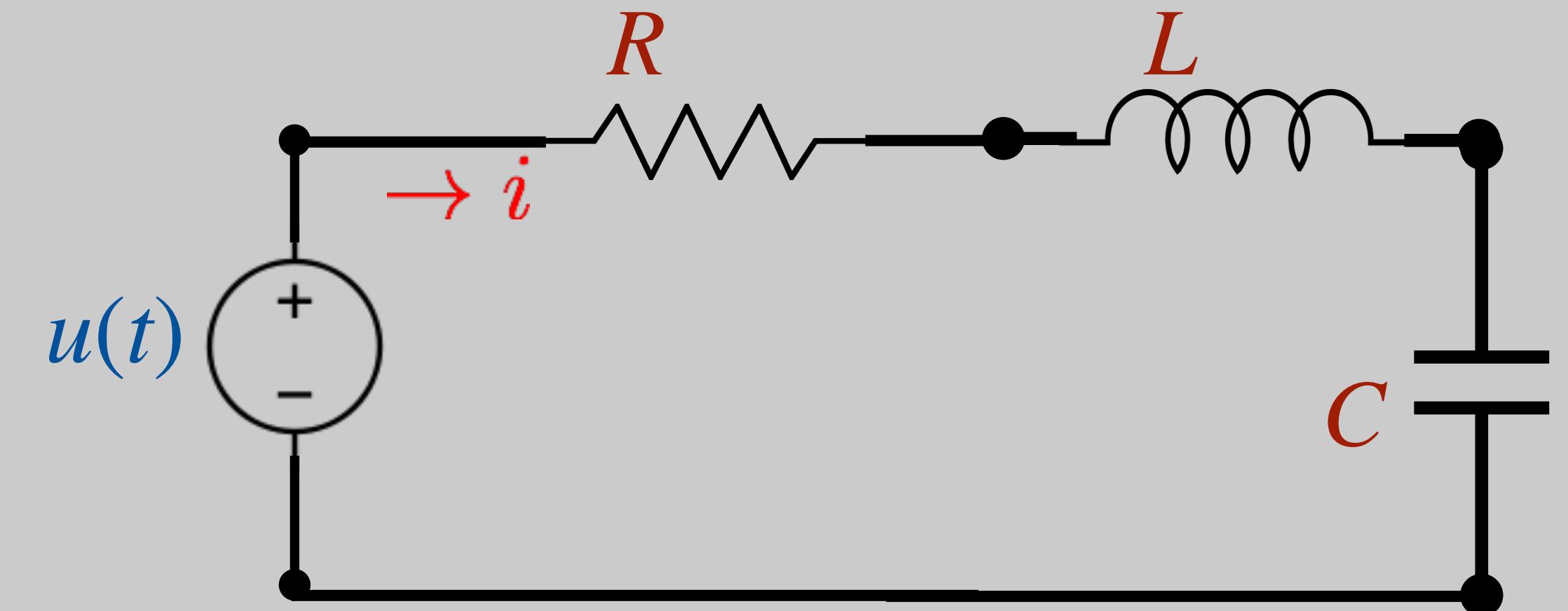

Damping coefficient (associated with decay)

Resonance frequency (associated with oscillations)

$$V_c(t) = Ae^{st}$$

# Overdamped

$$\frac{d^2}{dt^2}V_c(t) + 2\alpha \frac{d}{dt}V_c(t) + \omega_0^2 V_c(t) = 0$$

$\alpha > \omega_0$  2 real solutions:


$$V_c(t) = Ae^{s_1 t} + Be^{s_2 t}$$

From Initial conditions:

$$u(0) = V_{DD}$$

$$V_c(0) = V_{DD} \Rightarrow V_c(0) = Ae^0 + Be^0 = V_{DD} \Rightarrow A + B = V_{DD}$$
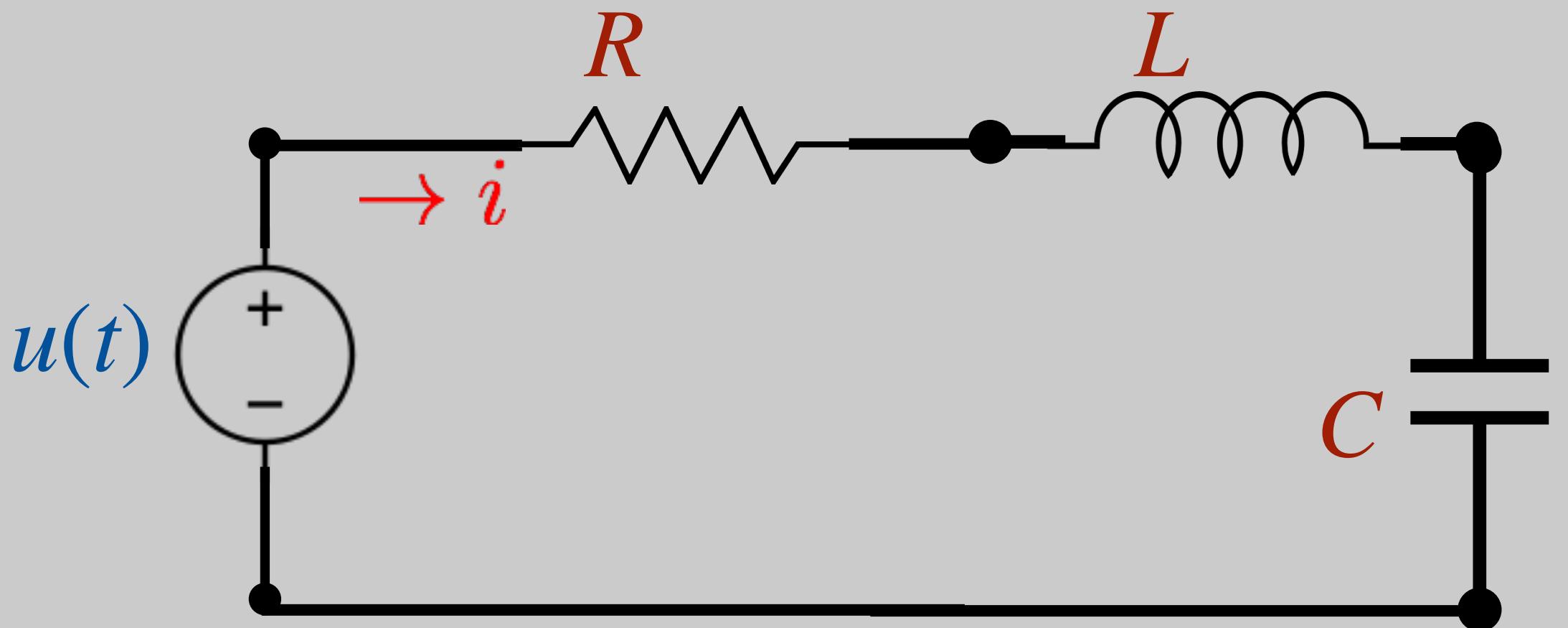
$$i_L(0) = 0 \Rightarrow i_L(0) = 0 \Rightarrow C \frac{d}{dt}V_c(0) = 0 \Rightarrow As_1 + Bs_2 = 0$$



# Overdamped

$$\frac{d^2}{dt^2}V_c(t) + 2\alpha \frac{d}{dt}V_c(t) + \omega_0^2 V_c(t) = 0$$

$\alpha > \omega_0$  2 real solutions:

$$V_c(t) = Ae^{s_1 t} + Be^{s_2 t}$$

From Initial conditions:

$$u(0) = V_{DD}$$


$$V_c(0) = V_{DD} \Rightarrow V_c(0) = Ae^0 + Be^0 = V_{DD} \Rightarrow A + B = V_{DD}$$

$$i_L(0) = 0 \Rightarrow i_L(0) = 0 \Rightarrow C \frac{d}{dt} V_c(0) = 0 \Rightarrow As_1 + Bs_2 = 0$$

$$\begin{pmatrix} 1 & 1 \\ s_1 & s_2 \end{pmatrix} \begin{pmatrix} A \\ B \end{pmatrix} = \begin{pmatrix} V_{DD} \\ 0 \end{pmatrix} \Rightarrow \frac{1}{s_2 - s_1} \begin{pmatrix} s_2 & -1 \\ -s_1 & 1 \end{pmatrix} \begin{pmatrix} V_{DD} \\ 0 \end{pmatrix} =$$

$$A = \frac{s_2}{s_2 - s_1} V_{DD}$$

$$B = -\frac{s_1}{s_2 - s_1} V_{DD}$$

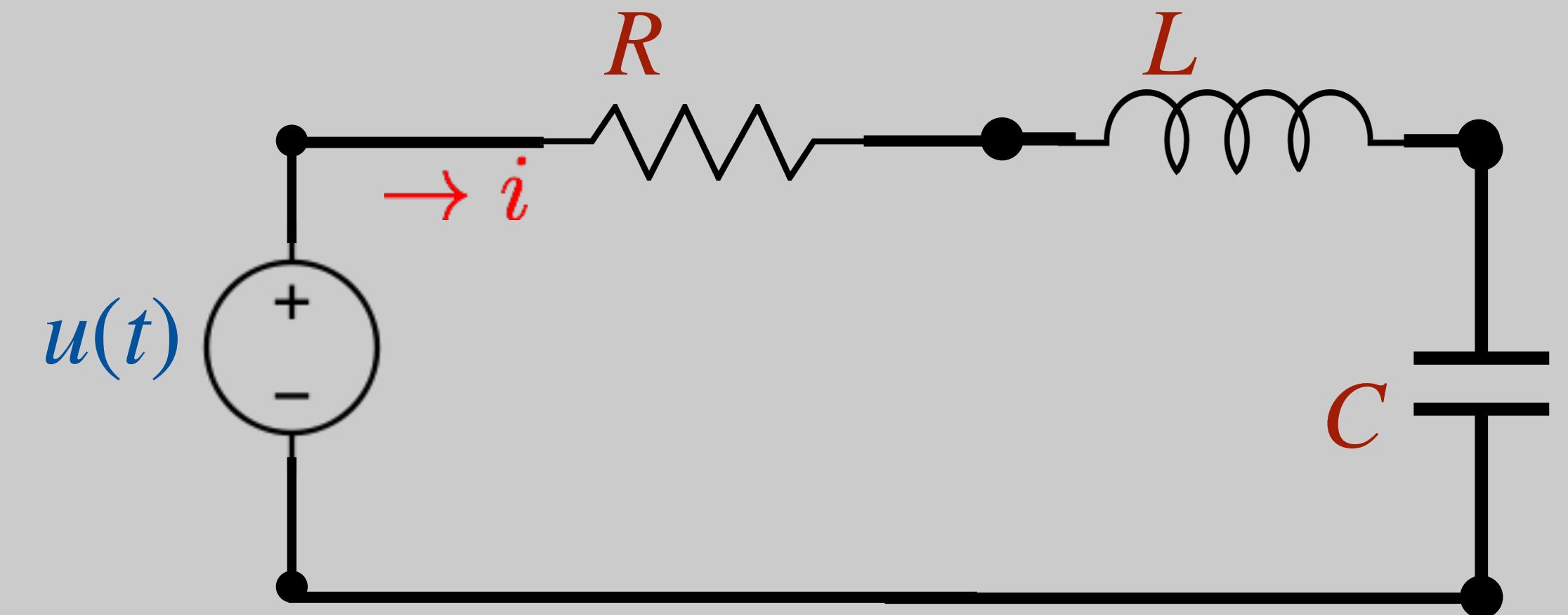

# Overdamped

$$V_c(t) = Ae^{s_1 t} + Be^{s_2 t}$$




$$A = \frac{s_2}{s_2 - s_1} V_{DD}$$

$$B = -\frac{s_1}{s_2 - s_1} V_{DD}$$

$$\alpha = 20$$

$$\omega_0 = 10$$

$$\zeta = 2$$

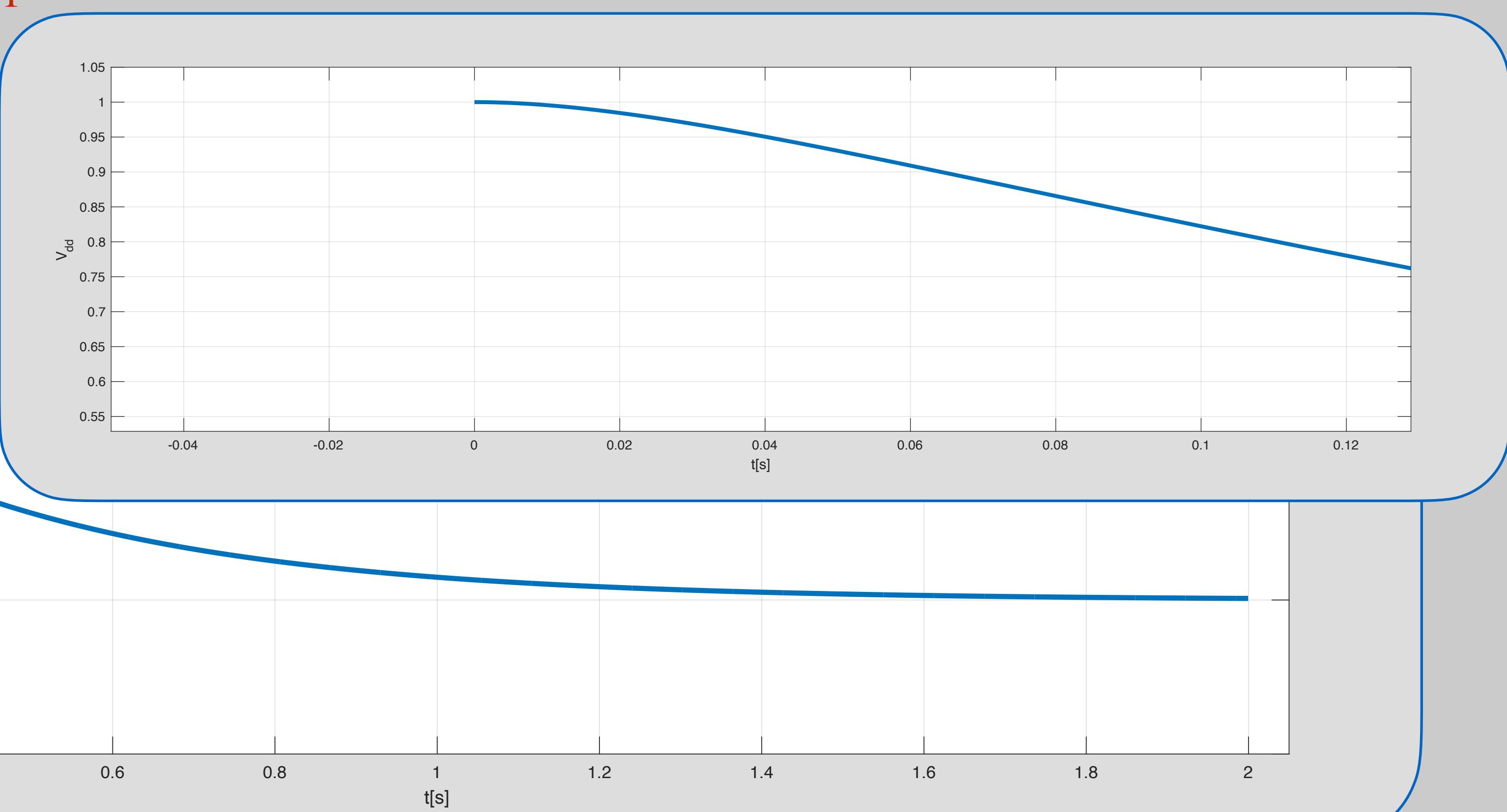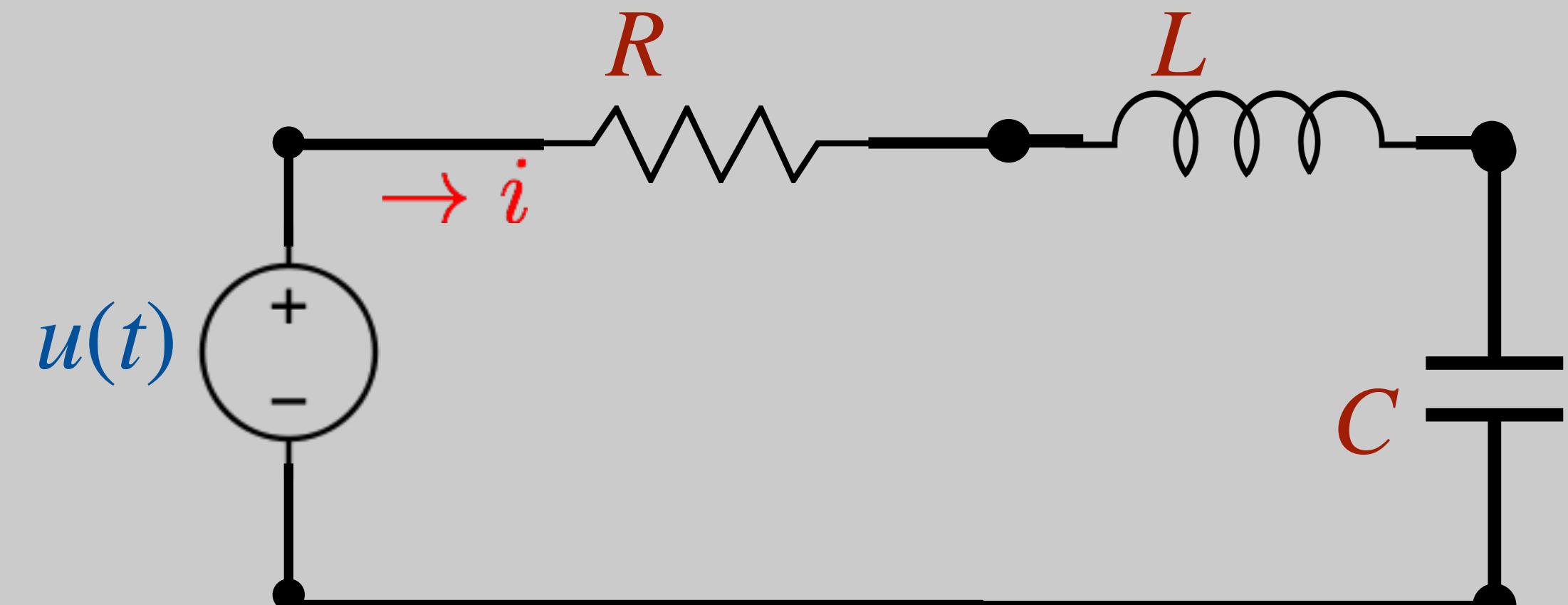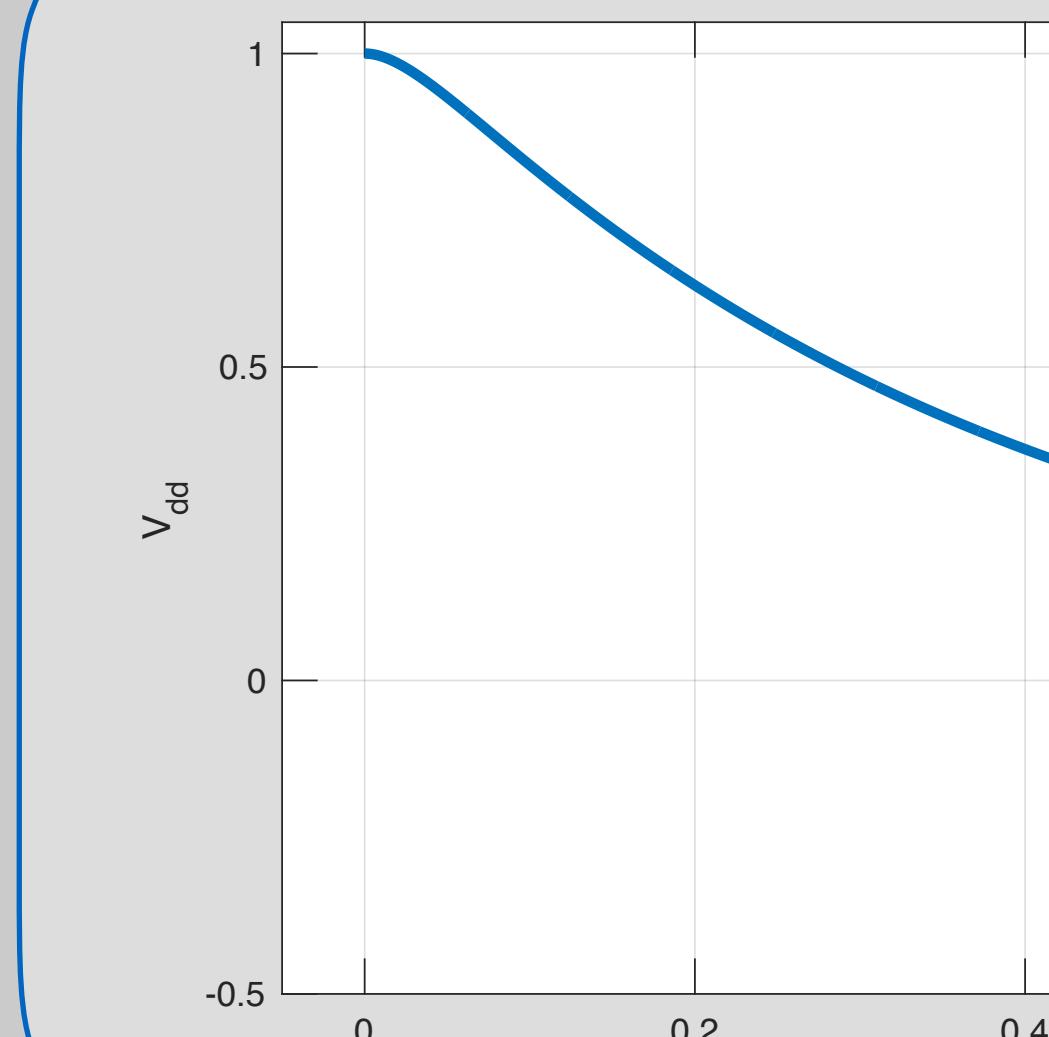


# Underdamped

$$\frac{d^2}{dt^2}V_c(t) + 2\alpha \frac{d}{dt}V_c(t) + \omega_0^2 V_c(t) = 0$$

$\alpha < \omega_0$     2 complex conjugate solutions:

$$V_c(t) = Ae^{s_1 t} + Be^{s_2 t}$$

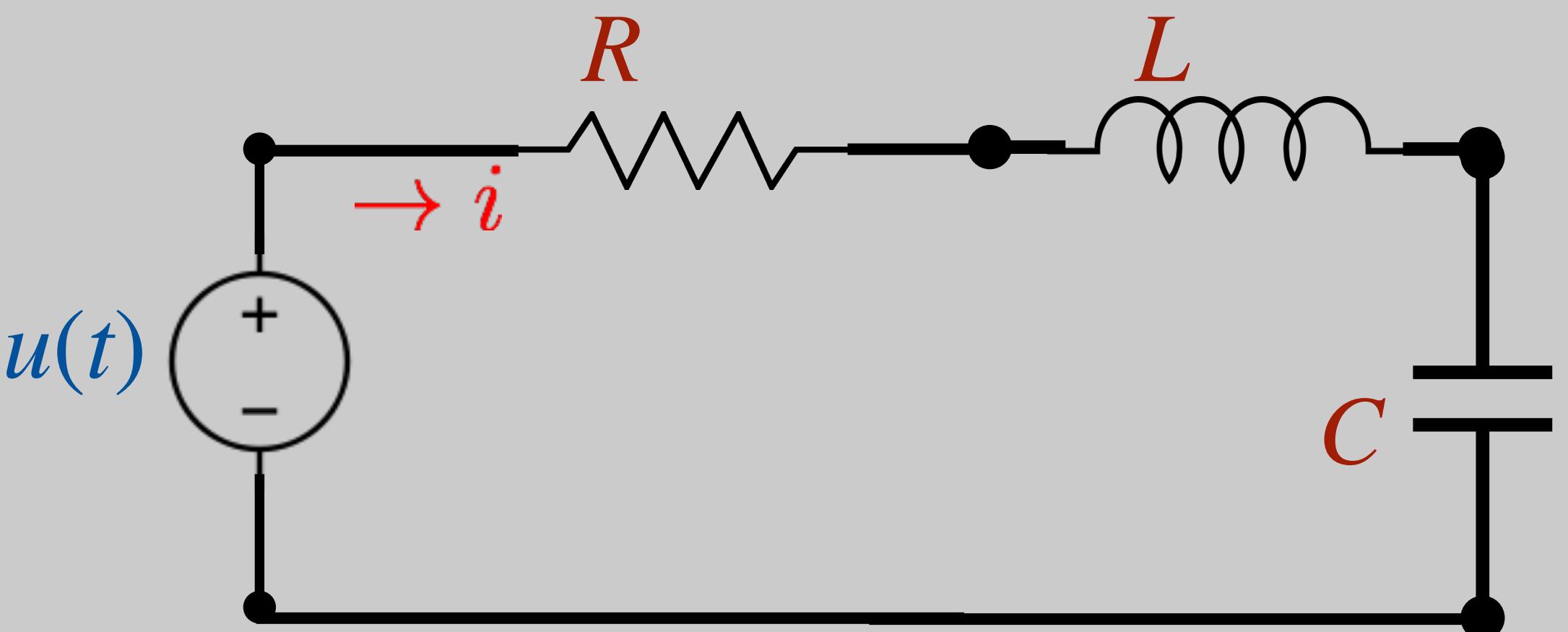

# Underdamped

$$\frac{d^2}{dt^2}V_c(t) + 2\alpha \frac{d}{dt}V_c(t) + \omega_0^2 V_c(t) = 0$$

$\alpha < \omega_0$  2 complex conjugate solutions:

$$V_c(t) = Ae^{s_1 t} + Be^{s_2 t}$$


From Initial conditions:

$$u(0) = V_{DD}$$

$$V_c(0) = V_{DD} \Rightarrow V_c(0) = Ae^0 + Be^0$$

$$i_L(0) = 0 \Rightarrow i_L(0) = 0 \Rightarrow C \frac{d}{dt} V_c(0) = 0$$
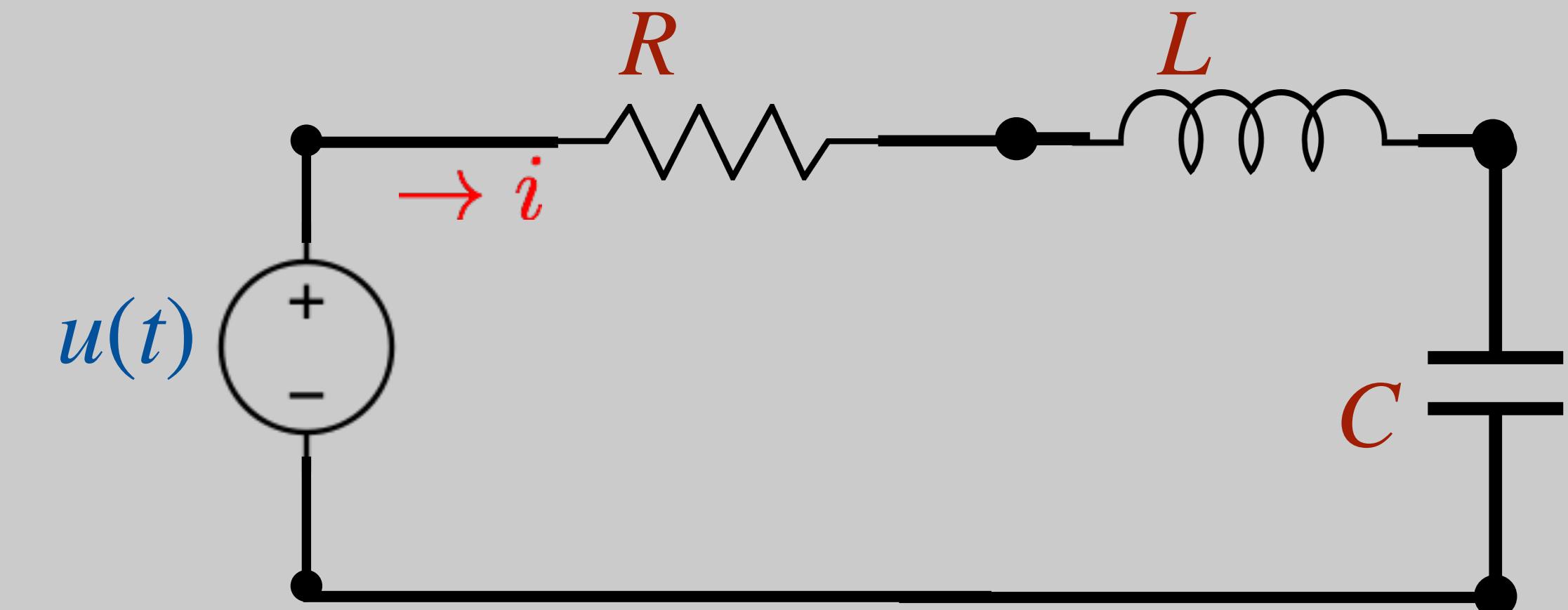
$$\begin{pmatrix} 1 & 1 \\ s_1 & s_2 \end{pmatrix} \begin{pmatrix} A \\ B \end{pmatrix} = \begin{bmatrix} V_{DD} \\ 0 \end{bmatrix} \Rightarrow \frac{1}{s_2 - s_1} \begin{pmatrix} s_2 & -1 \\ -s_1 & 1 \end{pmatrix} \begin{bmatrix} V_{DD} \\ 0 \end{bmatrix} \Rightarrow B = -\frac{s_1}{s_2 - s_1} V_{DD}$$



# ~~Overdamped~~ Underdamped


$$V_c(t) = Ae^{s_1 t} + Be^{s_2 t}$$

$$A = \frac{s_2}{s_2 - s_1} V_{DD} \quad B = -\frac{s_1}{s_2 - s_1} V_{DD}$$

$a < \omega_0$  2 complex conjugate solutions:

$$A = \frac{-\alpha - j\omega_n}{-2j\omega_n} V_{DD} \quad B = -\frac{-\alpha + j\omega_n}{-2j\omega_n} V_{DD}$$
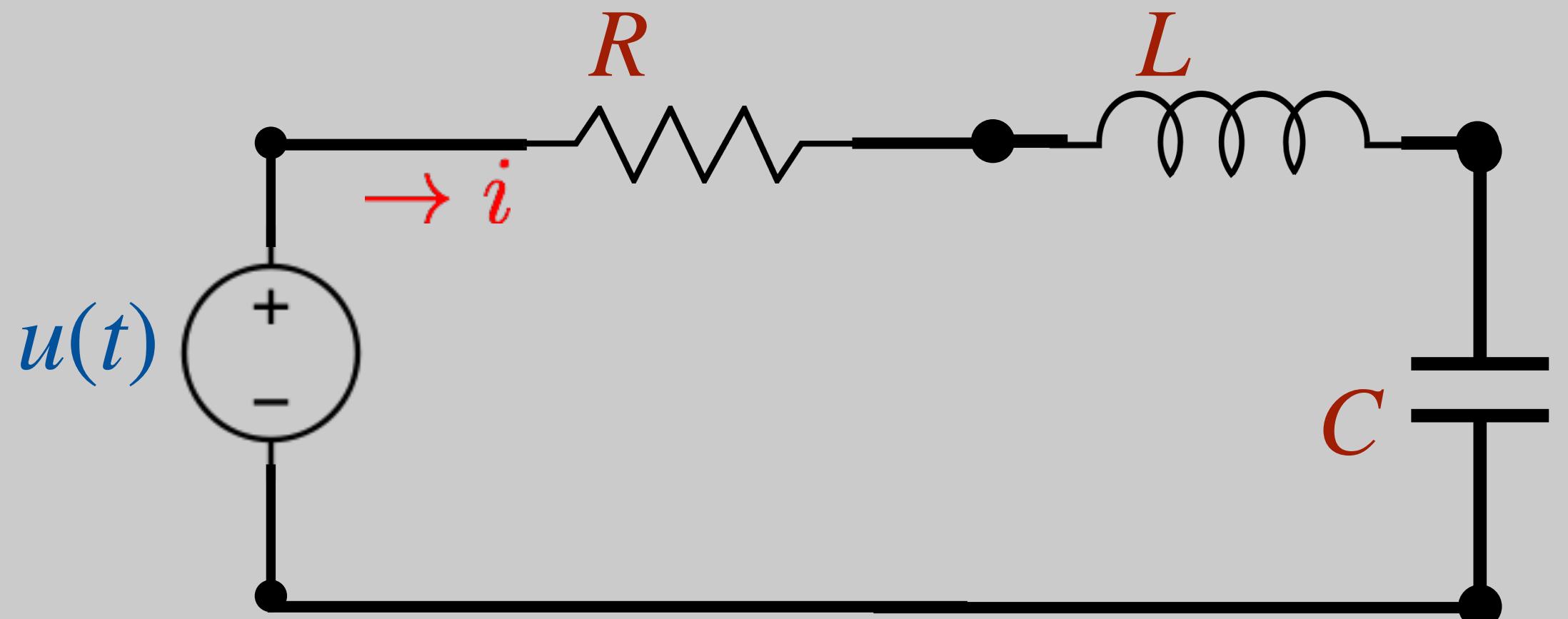
$$V_c(t) = \frac{\alpha + j\omega_n}{2j\omega_n} V_{DD} e^{(-\alpha + j\omega_n)t} + \frac{-\alpha + j\omega_n}{2j\omega_n} V_{DD} e^{(-\alpha - j\omega_n)t}$$



$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$j\omega_n = \sqrt{\alpha^2 - \omega_0^2}$$

$$s_1 = -\alpha + j\omega_n$$

$$s_2 = -\alpha - j\omega_n$$

Overshadowed Underdamped

$$V_c(t) = \frac{\alpha + j\omega_n}{2j\omega_n} V_{DD} e^{(-\alpha + j\omega_n)t} + \frac{-\alpha + j\omega_n}{2j\omega_n} V_{DD} e^{(-\alpha - j\omega_n)t}$$

$$= V_{DD} e^{-\alpha t} \left( \frac{e^{j\omega_n t} + e^{-j\omega_n t}}{2} \right)$$

Overdamped      Underdamped

$$V_c(t) = \frac{\alpha + j\omega_n}{2j\omega_n} V_{DD} e^{(-\alpha + j\omega_n)t} + \frac{-\alpha + j\omega_n}{2j\omega_n} V_{DD} e^{(-\alpha - j\omega_n)t}$$

$$= V_{DD} e^{-\alpha t} \left( \frac{e^{j\omega_n t} + e^{-j\omega_n t}}{2} \right) + V_{DD} \frac{\alpha}{\omega_n} e^{-\alpha t} \left( \frac{e^{j\omega_n t} - e^{-j\omega_n t}}{2j} \right)$$

$$= V_{DD} e^{-\alpha t} \cos(\omega_n t) + V_{DD} \frac{\alpha}{\omega_n} e^{-\alpha t} \sin(\omega_n t)$$

$$= V_{DD} e^{-\alpha t} \left( \cos(\omega_n t) + \frac{\alpha}{\omega_n} \sin(\omega_n t) \right)$$

~~Overdamped~~ Underdamped

$$V_c = V_{DD} e^{-\alpha t} \left( \cos(\omega_n t) + \frac{\alpha}{\omega_n} \sin(\omega_n t) \right)$$



$$\alpha = 5$$

$$\omega_0 = 10$$

$$\zeta = 0.5$$

$\omega_n$ : oscillation frequency

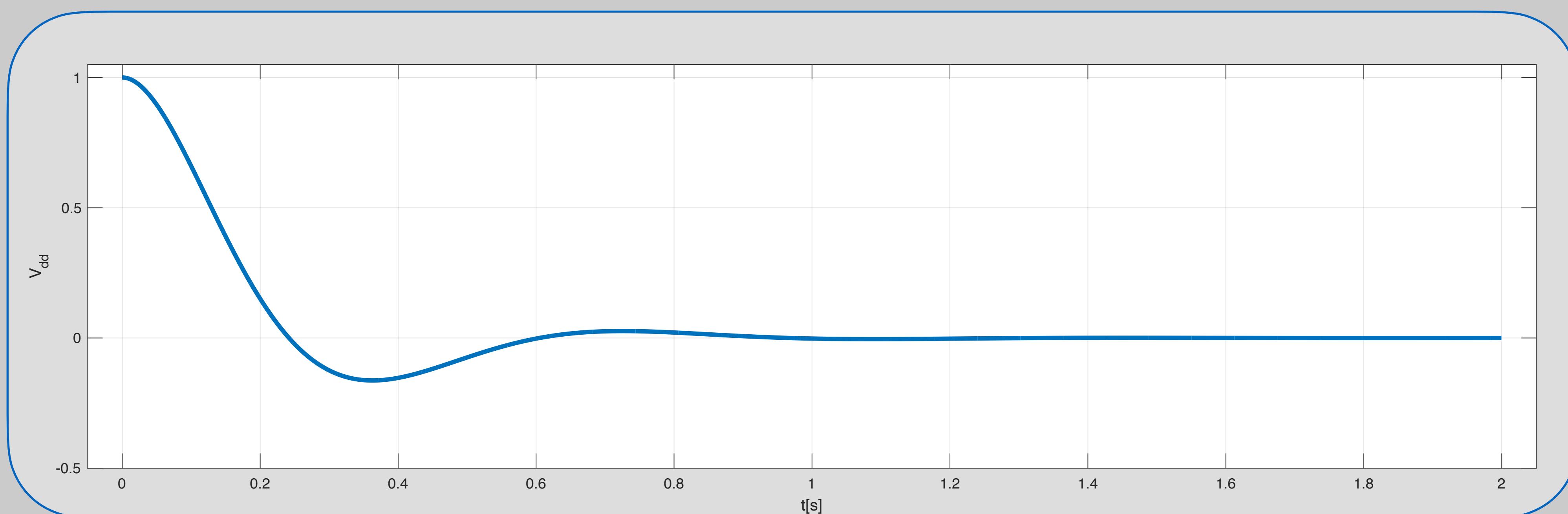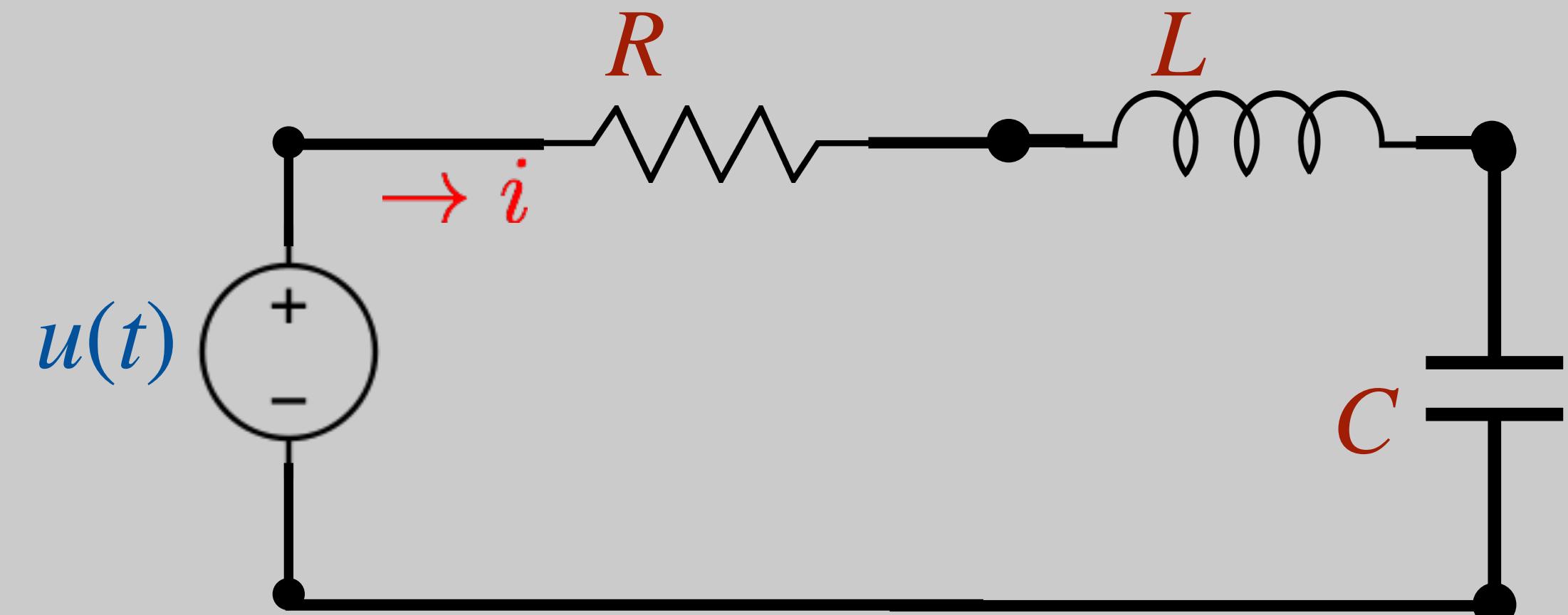$\omega_0$ : resonance frequency, when no damping ( $\alpha = 0, R = 0$ )



# Overdamped      Underdamped

$$V_c = V_{DD} e^{-\alpha t} \left( \cos(\omega_n t) + \frac{\alpha}{\omega_n} \sin(\omega_n t) \right)$$

$$\alpha = 5$$



$$\omega_0 = 10$$

$$\zeta = 0.5$$

$$\zeta = 0.3$$

$\omega_n$ : oscillation frequency

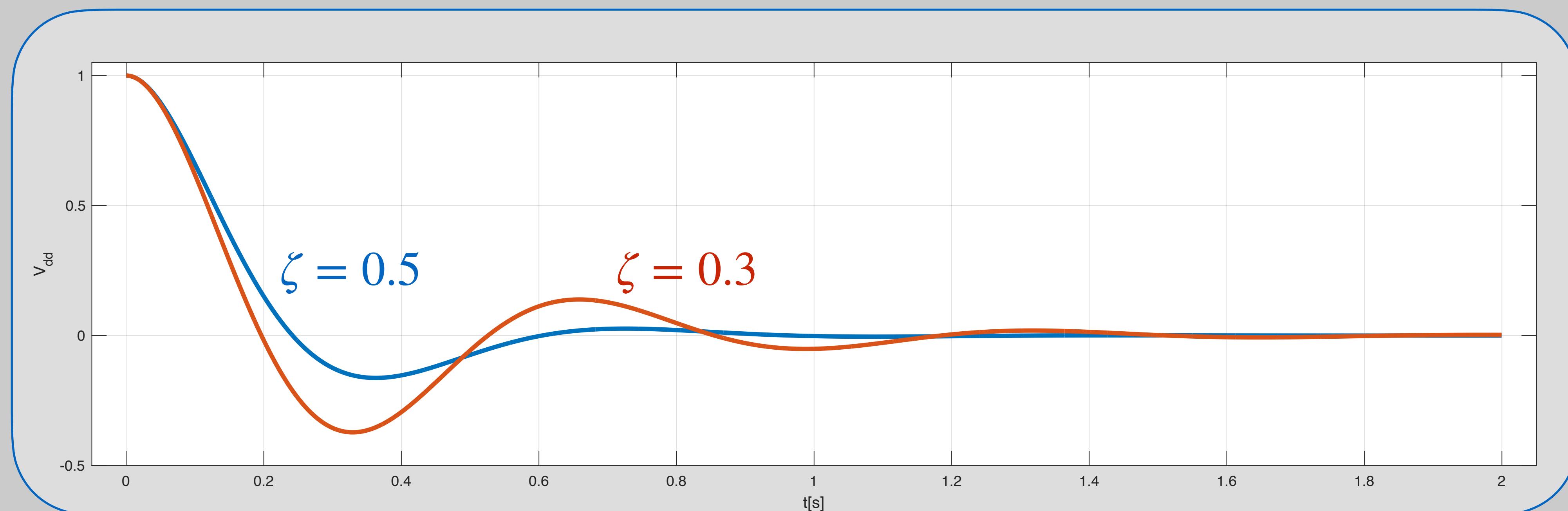
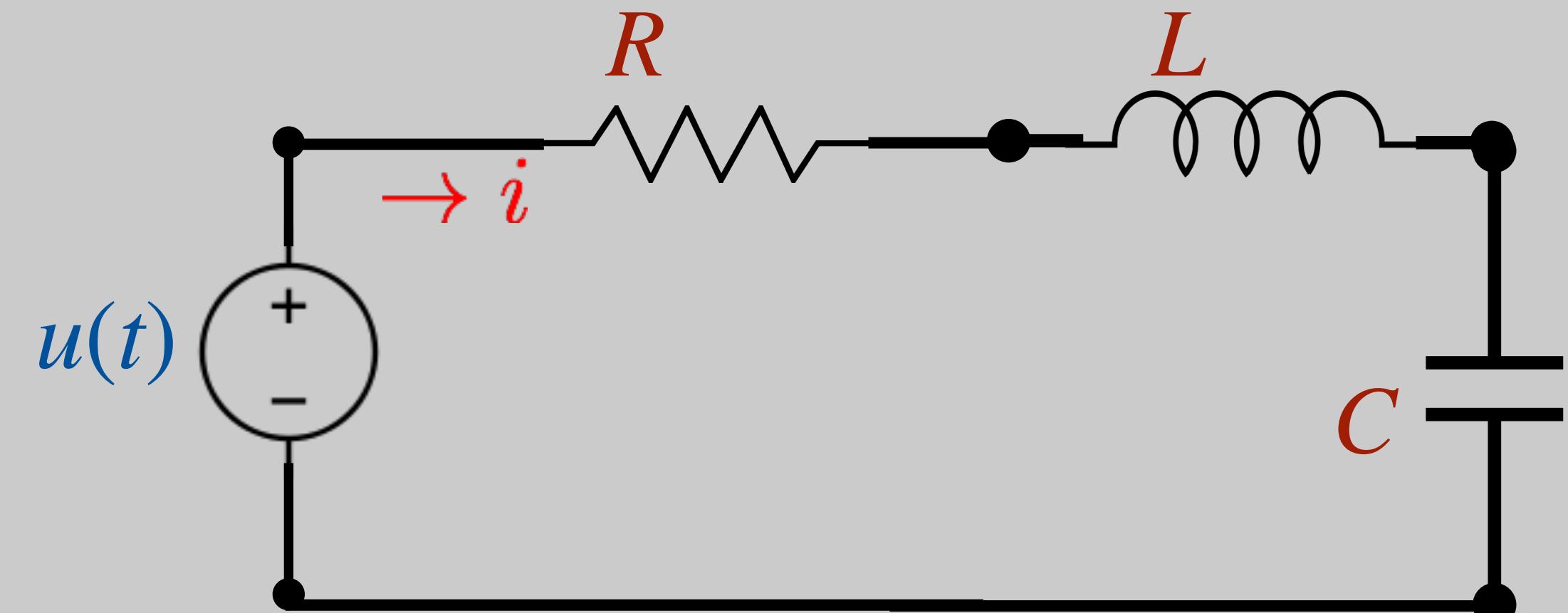
$\omega_0$ : resonance frequency, when no damping ( $\alpha = 0, R = 0$ )


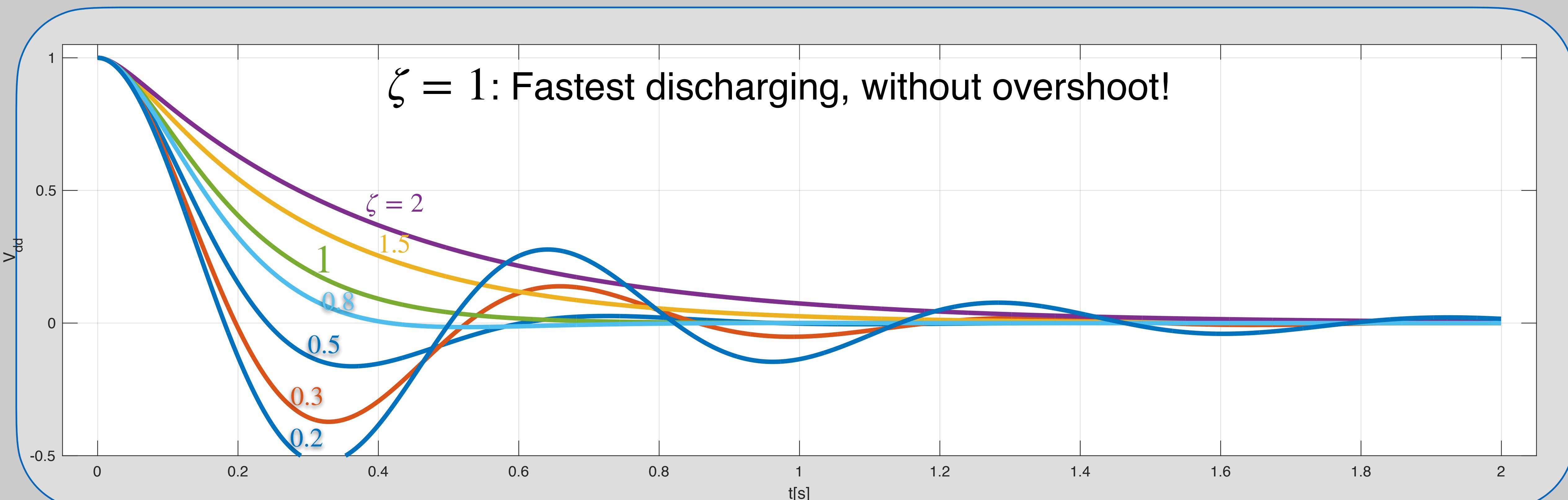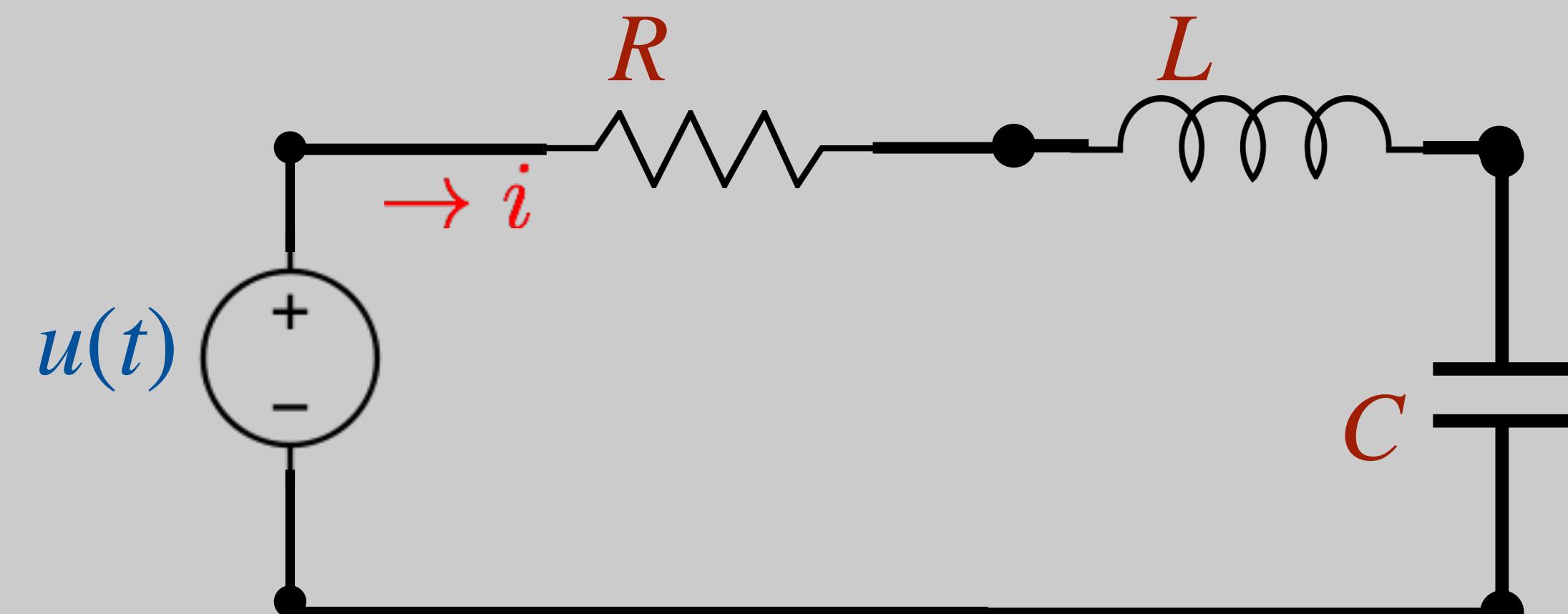
# RLC Homogeneous Response

$$V_c(t) = Ae^{s_1 t} + Be^{s_2 t}$$

$$A = \frac{s_2}{s_2 - s_1} V_{DD} \quad B = -\frac{s_1}{s_2 - s_1} V_{DD}$$




# Critically Damped

$$\frac{d^2}{dt^2}V_c(t) + 2\alpha \frac{d}{dt}V_c(t) + \omega_0^2 V_c(t) = 0$$

$a = \omega_0$  2 identical solutions:

$$V_c(t) = Ae^{s_1 t} + Be^{s_1 t}$$

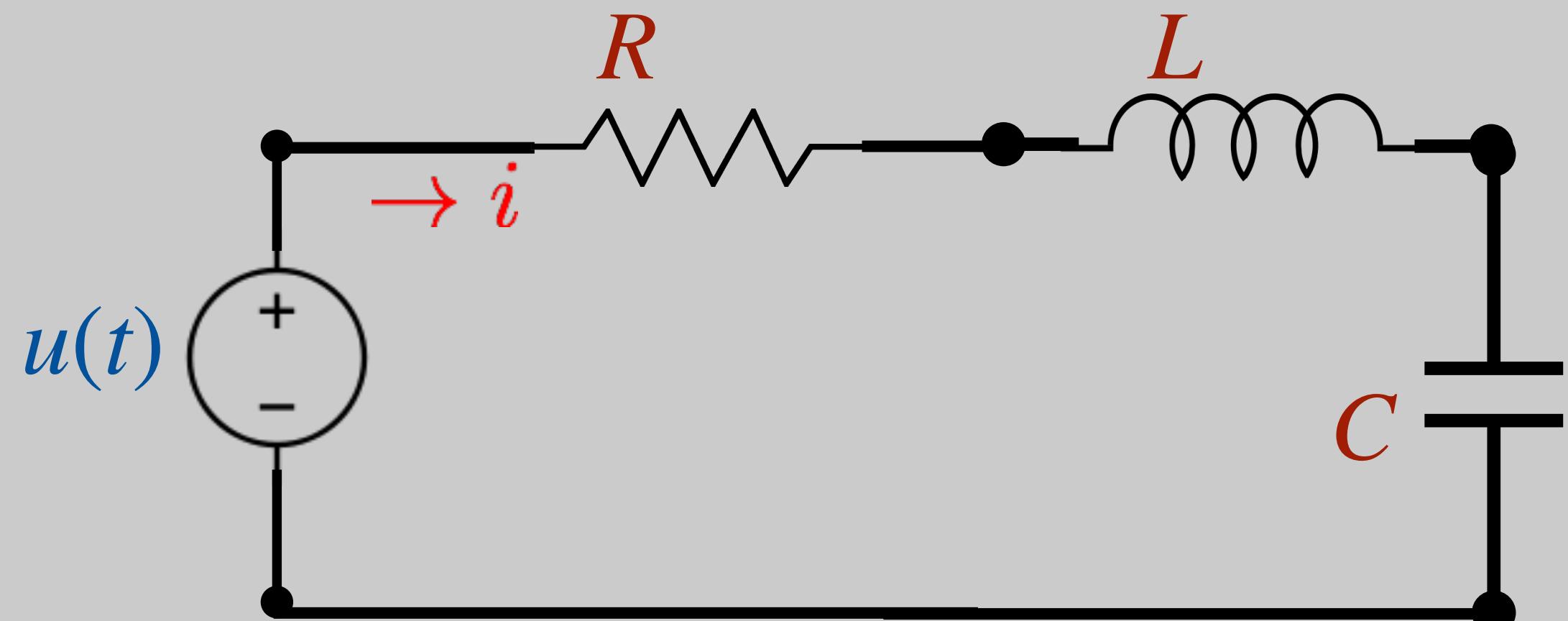

Problem! One initial condition....

Proceed with  $s_1, s_2$  for now....

# Critically Damped

$$\frac{d^2}{dt^2}V_c(t) + 2\alpha \frac{d}{dt}V_c(t) + \omega_0^2 V_c(t) = 0$$

$a = \omega_0$  2 identical solutions:

$$V_c(t) = Ae^{s_1 t} + Be^{s_1 t}$$

From Initial condition

$$u(0) = V_{DD}$$


$$V_c(0) = V_{DD}$$

$$i_L(0) = 0$$

$$\begin{pmatrix} 1 & 1 \\ s_1 & s_2 \end{pmatrix} \begin{pmatrix} A \\ B \end{pmatrix} = \begin{bmatrix} V_{DD} \\ 0 \end{bmatrix} \Rightarrow \frac{1}{s_2 - s_1} \begin{pmatrix} s_2 - 1 \\ -s_1 & 1 \end{pmatrix} \begin{pmatrix} A \\ B \end{pmatrix} = \begin{bmatrix} V_{DD} \\ 0 \end{bmatrix}$$

Problem! One initial condition....

Proceed with  $s_1, s_2$  for now....

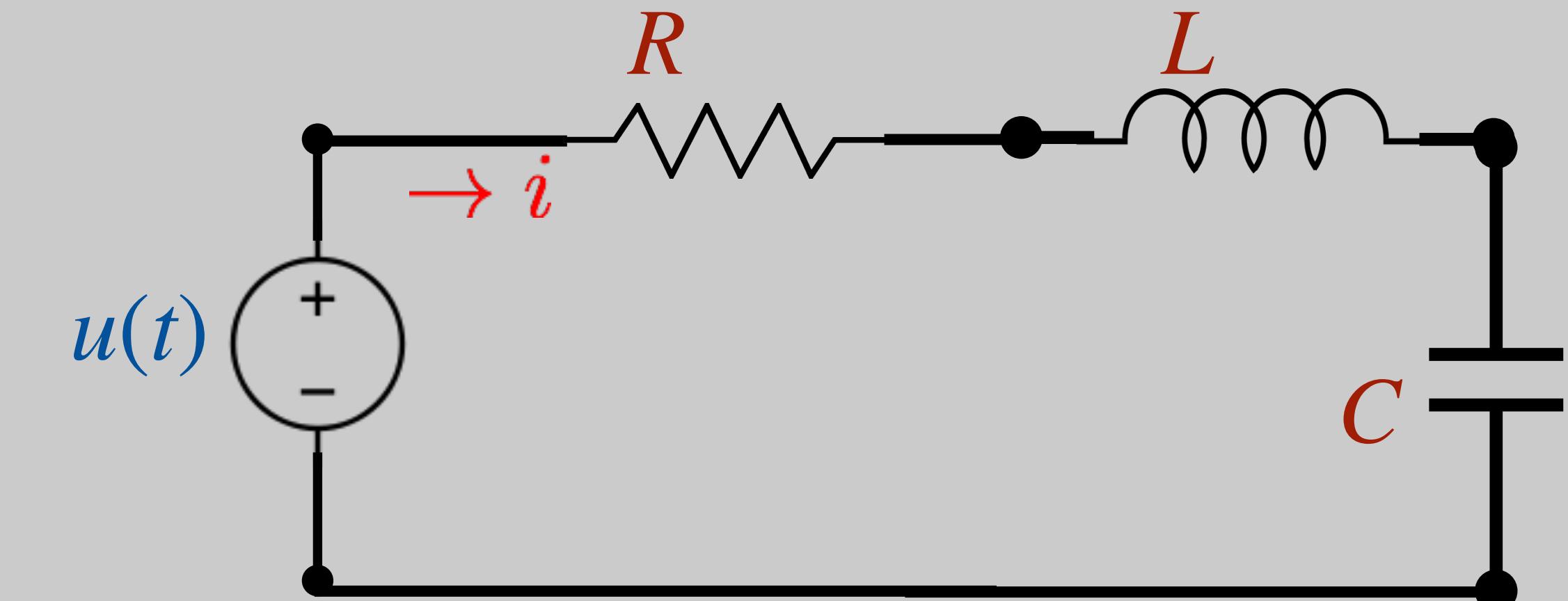

*Same as before!!!!*


$$A = \frac{s_2}{s_2 - s_1} V_{DD}$$

$$B = -\frac{s_1}{s_2 - s_1} V_{DD}$$
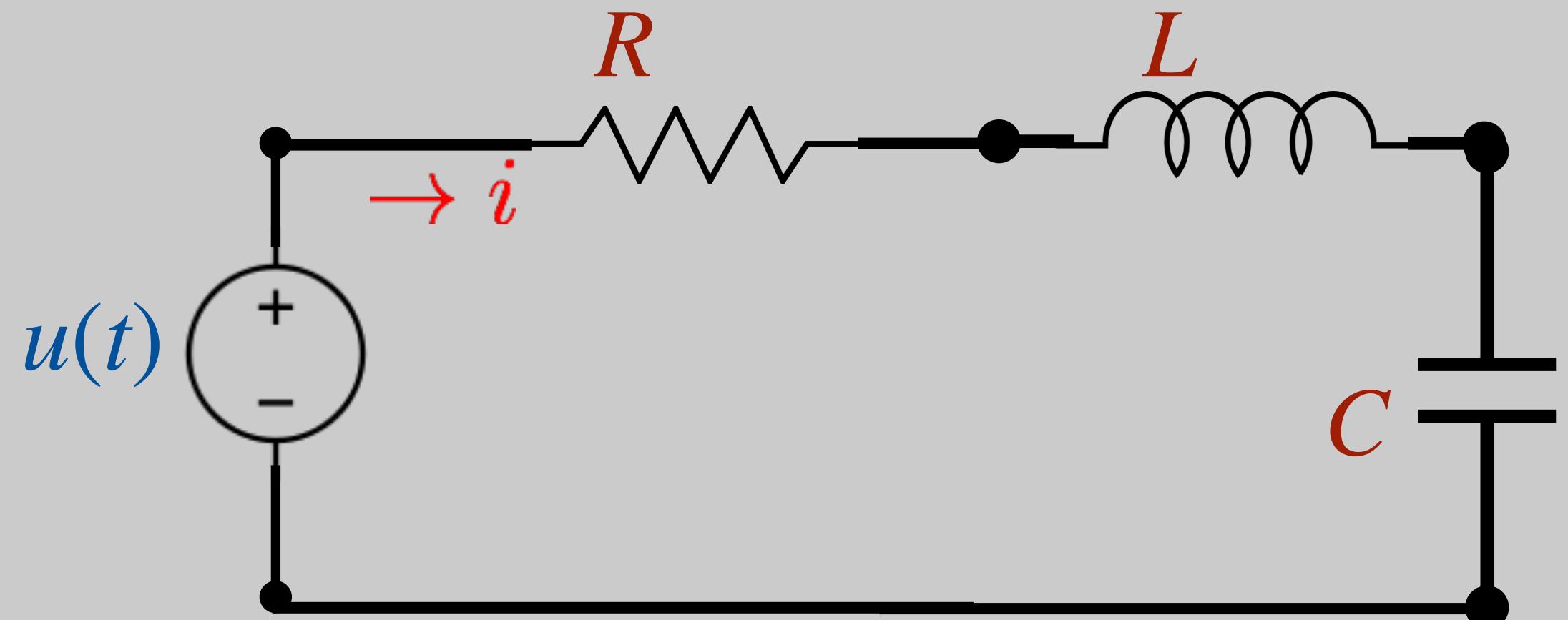
# Critically Damped

$$V_c(t) = Ae^{s_1 t} + Be^{s_2 t}$$

$$A = \frac{s_2}{s_2 - s_1} V_{DD} \quad B = -\frac{s_1}{s_2 - s_1} V_{DD}$$



$$\lim_{s_2 \rightarrow s_1} V_c(t) = V_{DD} \frac{s_2 e^{s_1 t} - s_1 e^{s_2 t}}{s_2 - s_1}$$

L'Hopital's rule:

$$= V_{DD} \frac{e^{s_1 t} - s_1 t e^{s_2 t}}{1} = V_{DD} (e^{s_1 t} - s_1 t e^{s_1 t})$$

General solution for repeated roots:

$$V_c(t) = Ae^{s_1 t} + Bte^{s_1 t}$$

## Recap:

---

$$a = \frac{R}{2L}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$\zeta = \frac{\alpha}{\omega_0}$$

$$Q = \frac{1}{2\zeta} = \frac{\omega_0 L}{R} = \sqrt{\frac{L}{CR^2}}$$

$\alpha > \omega_0, \zeta \cancel{>} 1 \Rightarrow$  Overdamped

$$\frac{d^2}{dt^2}V_c(t) + 2\alpha\frac{d}{dt}V_c(t) + \omega_0^2V_c(t) = u(t)$$

Damping coefficient (associated with decay)

Resonance frequency

Damping Ratio

Quality factor

$\alpha > \omega_0, \zeta \cancel{<} 1 \Rightarrow$  Overdamped  $\Rightarrow$  Exponential decays

$\alpha = \omega_0, \zeta = 1 \Rightarrow$  Critically damped  $\Rightarrow$  Fastest decay without oscillations

$\alpha < \omega_0, \zeta \cancel{<} 1 \Rightarrow$  Underdamped  $\Rightarrow$  decay+oscillations

$$\omega_n = \sqrt{\alpha^2 - \omega^2} \quad \text{Oscillation frequency}$$