

## 1 RC Circuits

In this problem, we will be using differential equations to find the voltage across a capacitor over time in an RC circuit. We set up our problem by first defining three functions over time:  $I(t)$  is the current at time  $t$ ,  $V(t)$  is the voltage across the circuit at time  $t$ , and  $V_C(t)$  is the voltage across the capacitor at time  $t$ .

Recall from 16A that the voltage across a resistor is defined as  $V_R = RI_R$  where  $I_R$  is the current across the resistor. Also, recall that the voltage across a capacitor is defined as  $V_C = \frac{Q}{C}$  where  $Q$  is the charge across the capacitor.

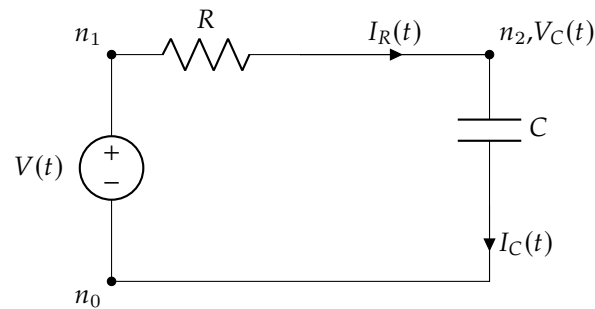


Figure 1: Example Circuit

- a) First, find an equation that relates the current through the capacitor  $I_C(t)$  with the voltage across the capacitor  $V_C(t)$ .

### Answer

Charge  $Q_C(t)$  and current  $I_C(t)$  are related as

$$I_C(t) = \frac{d}{dt} Q_C(t)$$

Differentiating  $V_C(t) = \frac{Q_C(t)}{C}$  in terms of  $t$ , we get

$$\frac{dV_C(t)}{dt} = \frac{dQ_C(t)}{dt} \frac{1}{C}$$

Using the charge-current relationship above, we can write

$$\frac{d}{dt} V_C(t) = I(t) \frac{1}{C}$$

- b) Using nodal analysis, write a differential equation for the capacitor voltage  $V_C(t)$ . Note that this is also the voltage for the node  $n_2$ .

### Answer

We first list out our device equations to obtain the branch currents for the circuit in Figure 1. The current flowing through the resistor  $R$  is given by Ohm's law to be

$$I_R(t) = \frac{V_{n_1}(t) - V_{n_2}(t)}{R}. \quad (1)$$

The current through the capacitor is given by

$$I_C(t) = C \frac{d}{dt} V_{n_2}(t). \quad (2)$$

Next, we write Kirchoff's current law equations at the nodes. For node  $n_2$ , we have

$$I_R(t) = I_C(t)$$

With  $n_0$  as the reference node, we have

$$V_{n_1} = V(t)$$

. Substituting the values of  $I_R(t)$  and  $I_C(t)$  from equations 1 and 2 above, we get

$$C \frac{d}{dt} V_{n_2}(t) = \frac{V_{n_1}(t) - V_{n_2}(t)}{R}$$

$$RC \frac{d}{dt} V_{n_2}(t) = V(t) - V_{n_2}(t)$$

Since the node voltage  $V_{n_2}(t)$  is same as the capacitor voltage  $V_C(t)$ , we can express the evolution of capacitor voltage  $V_C(t)$  as

$$RC \frac{d}{dt} V_C(t) = V(t) - V_C(t)$$

- c) Let's suppose that at  $t = 0$ , the capacitor is charged to a voltage  $V_{DD}$  ( $V_C(0) = V_{DD}$ ). Let's also assume that  $V(t) = 0$  for all  $t \geq 0$ .

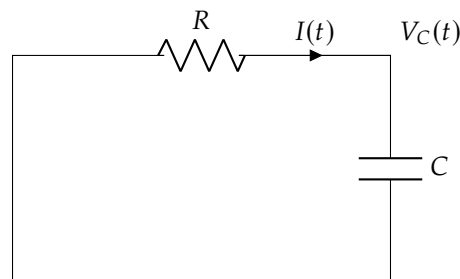


Figure 2: Circuit for part (d)

Solve the differential equation for  $V_C(t)$  for  $t \geq 0$ .

### Answer

Because  $V(t) = 0$ , our differential equation simplifies to

$$RC \frac{dV_C(t)}{dt} + V_C(t) = 0$$

Doing some algebraic manipulations gives us

$$\frac{dV_C(t)}{dt} = -\frac{1}{RC}V_C(t)$$

This equation tells us that we are looking for some function  $V_C(t)$  such that when we take its derivative, we get the same function  $V_C(t)$  multiplied by a scalar  $-\frac{1}{RC}$ . Because the derivative is equal to a scalar times itself, we think that the solution  $V_C(t)$  will probably be of the form  $Ae^{bt}$ , where  $A$  and  $b$  are both constants. In this case we see that  $b = -\frac{1}{RC}$ , and we find that

$$V_C(t) = Ae^{-\frac{1}{RC}t}$$

We still need to solve for the constant  $A$  in front of the exponential, and we use  $V_C(0) = K$  to help us find  $A$ . Setting  $t = 0$  in the equation gives us

$$\begin{aligned} V_C(0) &= Ae^{-\frac{1}{RC}0} \\ &= Ae^0 \\ &= A \\ &= V_{DD} \end{aligned}$$

Thus, we see that  $A = V_{DD}$ , and our solution is

$$V_C(t) = V_{DD}e^{-\frac{1}{RC}t}$$

- d) Now, let's suppose that we start with an uncharged capacitor  $V_C(0) = 0$ . We apply some constant voltage  $V(t) = V_{DD}$  across the circuit. Solve the differential equation for  $V_C(t)$  for  $t \geq 0$ .

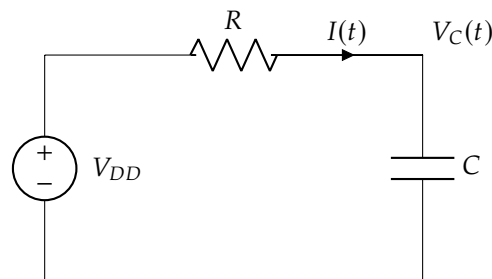


Figure 3: Circuit for part (e)

### Answer

Substituting  $V(t) = V_{DD}$  into our solution from part (c):

$$RC \frac{dV_C(t)}{dt} + V_C(t) = V_{DD}$$

Rearranging the differential equation we get

$$\frac{d}{dt}V_C = -\frac{1}{RC}V_C(t) + \frac{V_{DD}}{RC}$$

This differential equation looks similar to the one in the previous part but we notice that there is an extra  $\frac{V_{DD}}{RC}$  term. If we were to again guess the solution  $V_C(t) = Ae^{-\frac{t}{RC}}$  we see that:

$$\begin{aligned} -\frac{1}{RC}Ae^{-\frac{t}{RC}} &= -\frac{1}{RC}Ae^{-\frac{t}{RC}} + \frac{V_{DD}}{RC} \\ 0 &= \frac{V_{DD}}{RC} \end{aligned}$$

We end up with an equation that is impossible to solve meaning there must have been a problem with our guess. Therefore, we will improve our guess by trying the solution  $V_C(t) = Ae^{-\frac{t}{RC}} + B$ . Taking its derivative and plugging it into the differential equation, we get

$$\begin{aligned} \frac{dV_C(t)}{dt} &= -\frac{1}{RC}V_C(t) + \frac{V_{DD}}{RC} \\ -\frac{1}{RC}Ae^{-\frac{t}{RC}} &= -\frac{1}{RC}(Ae^{-\frac{t}{RC}} + B) + \frac{V_{DD}}{RC} \\ 0 &= -\frac{B}{RC} + \frac{V_{DD}}{RC} \end{aligned}$$

This tells us that  $B = V_{DD}$ . Now to solve for  $A$ , we plug in the initial condition  $V_C(0) = 0$

$$V_C(0) = Ae^{-\frac{0}{RC}} + V_{DD} = A + V_{DD} = 0$$

It follows that  $A = -V_{DD}$  so our final solution to the differential equation will be

$$V_C(t) = -V_{DD}e^{-\frac{t}{RC}} + V_{DD} = V_{DD}(1 - e^{-\frac{t}{RC}})$$

Alternate Method using Substitution of Variables:

We want to arrange this equation to be in a form that we know how to solve:

$$\frac{d}{dt}V_C = \frac{V_{DD} - V_C(t)}{RC}$$

This is not quite the form we have seen before, as the term on the right is not equal to the term being differentiated. Let's instead define a new variable  $\tilde{V}_C(t) = V_C(t) - V_{DD}$ . Note that  $\frac{d\tilde{V}_C(t)}{dt} = \frac{dV_C(t)}{dt}$ . We can substitute these into our differential equation and obtain

$$\begin{aligned} RC \frac{dV_C(t)}{dt} + V_C(t) - V_{DD} &= 0 \\ RC \frac{d\tilde{V}_C(t)}{dt} + \tilde{V}_C(t) &= 0 \end{aligned}$$

In this equation, we have now removed  $V_{DD}$  from the left hand because of how we defined  $\tilde{V}_C(t)$ . We can now solve the differential equation using the same method as in the previous part to get

$$\tilde{V}_C(t) = Ae^{-\frac{t}{RC}}$$

Substituting  $V_C(t) = V_{DD} + \tilde{V}_C(t)$  back into this equation gives us

$$V_C(t) = V_{DD} + Ae^{-\frac{t}{RC}}$$

Using in the initial condition  $V_C(0) = 0$ , we get:

$$0 = V_{DD} + Ae^{-\frac{0}{RC}} = V_{DD} + A \implies A = -V_{DD}$$

Therefore,

$$\begin{aligned} V_C(t) &= V_{DD} - V_{DD}e^{-\frac{t}{RC}} \\ &= V_{DD}(1 - e^{-\frac{t}{RC}}) \end{aligned}$$

## 2 Graphing RC Responses

Consider the following RC Circuit with a single resistor  $R$ , capacitor  $C$ , and voltage source  $V(t)$ .

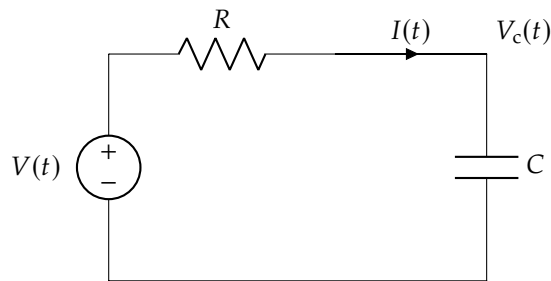


Figure 4: Example Circuit

- a) Let's suppose that at  $t = 0$ , the capacitor is charged to a voltage  $V_{DD}$  ( $V_c(0) = V_{DD}$ ) and that  $V(t) = 0$  for all  $t \geq 0$ . Plot the response  $V_c(t)$ .

### Answer


We can represent the RC Circuit with the following first order differential equation

$$\frac{dV_c(t)}{dt} = -\frac{1}{RC}V_c(t)$$

Since the initial condition is  $V_c(0) = V_{DD}$ , the solution to this differential equation will be  $V_c(t) = V_{DD}e^{-\frac{t}{RC}}$ .

To plot this response by using a graphing tool or by plotting points and connecting the dots. We've plotted the response when  $V_{DD} = 5$  and  $RC = 1$ .

Voltage Graph for Discharging Capacitor

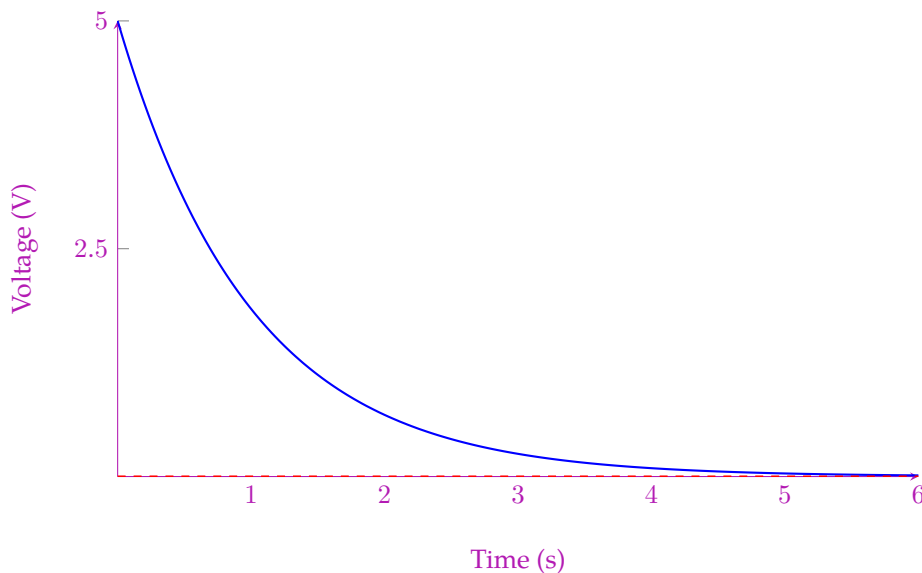


- b) Now let's suppose that at  $t = 0$ , the capacitor is uncharged ( $V_c(0) = 0$ ) and that  $V(t) = V_{DD}$  for all  $t \geq 0$ . Plot the response  $V_c(t)$ .

**Answer**

We can represent the RC Circuit with the following first order differential equation

$$\frac{dV_c(t)}{dt} = -\frac{1}{RC}V_c(t) + \frac{V_{DD}}{RC}$$

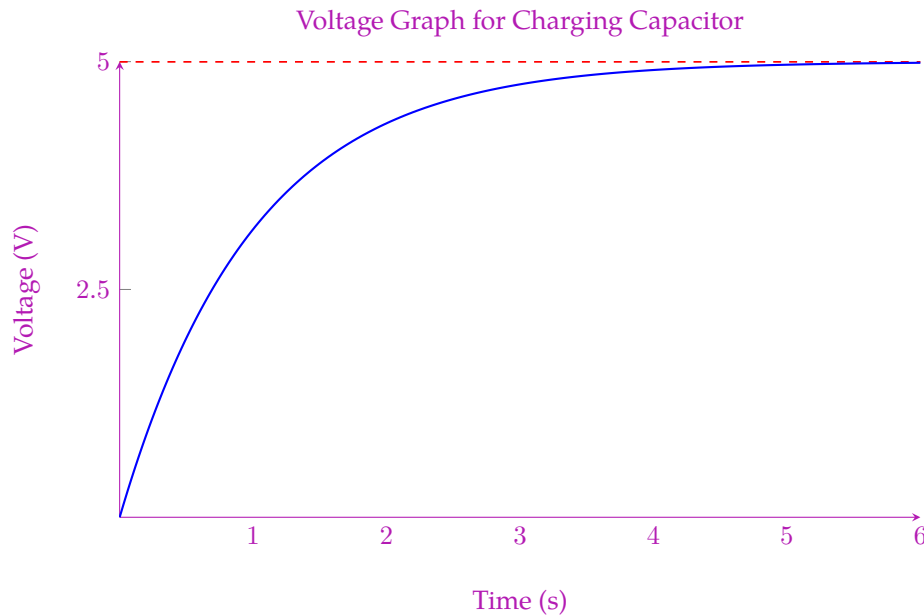The solution to this differential equation is  $V_c(t) = V_{DD}(1 - e^{-\frac{t}{RC}})$  and we can plot its response again by using a graphing tool. We've plotted the response when  $V_{DD} = 5$  and  $RC = 1$ .



To better understand our responses, we now define a **time constant** which is a measure of how long it takes for the capacitor to charge or discharge. Mathematically, we define  $\tau$  as the time at which  $V_c(\tau)$  is  $\frac{1}{e} = 36.8\%$  away from its steady state value.

- c) Suppose that  $V_{DD} = 5\text{ V}$ ,  $R = 100\ \Omega$ , and  $C = 10\ \mu\text{F}$ . What is the time constant  $\tau$  for this circuit?

**Answer**

The time constant for an RC circuit with a single resistor and capacitor will be  $\tau = RC$ . To show this, we look at the discharging case in part (a), let  $V_c(\tau) = \frac{V_{DD}}{e}$  and solve for  $\tau$ .

$$\begin{aligned} V_c(\tau) &= V_{DD}e^{-\frac{\tau}{RC}} = \frac{V_{DD}}{e} \\ e^{-\frac{\tau}{RC}} &= \frac{1}{e} \\ \ln(e^{-\frac{\tau}{RC}}) &= \ln\left(\frac{1}{e}\right) \\ -\frac{\tau}{RC} &= -1 \\ \tau &= RC \end{aligned}$$

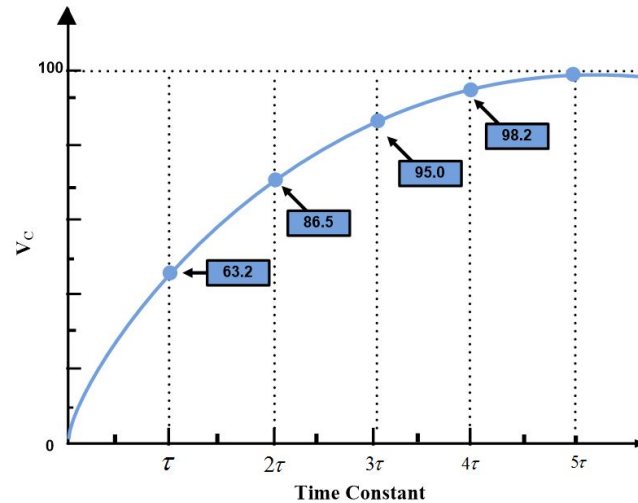


Figure 5: Different values of capacitor voltage at different times, relative to  $\tau$ .

Alternatively we could've solved for  $\tau$  by considered the charging case from part (b) and solved for  $V_c(\tau) = V_{DD}(1 - \frac{1}{e})$ .

- d) Going back to part (b), on what order of magnitude of time (nanoseconds, milliseconds, 10's of seconds, etc.) does this circuit settle ( $V_c$  is  $> 95\%$  of its value as  $t \rightarrow \infty$ )?

### Answer

The time constant  $\tau$  of an RC circuit is just  $\tau = RC$ . For our circuit:

$$\tau = RC = 100 \Omega \cdot 10 \mu\text{F} = 0.001 \text{ s}$$

After 3 time constants, the voltage will be 95% of its steady state value

$$3\tau = 0.003 \text{ s}$$

The circuit will settle on the order of milliseconds. Alternatively, this value can be found by using algebra:

$$0.95V_{DD} = V_{DD}(1 - e^{-\frac{t}{RC}})$$

$$-0.05 = -e^{-\frac{t}{RC}}$$

$$0.05 = e^{-\frac{t}{RC}}$$

$$\ln(0.05) = -\frac{t}{RC}$$

$$-3 = -\frac{t}{0.001}$$

$$t = 0.003 \text{ seconds}$$

- e) Give 2 ways to reduce the settling time of the circuit if we are allowed to change one component in the circuit.




**Answer**

To reduce settling time we reduce  $\tau$ . We can achieve this by


- Lowering the value of  $R$  or
- Lowering the value of  $C$ .

Notice how the value of  $V_{DD}$  does not change the settling time.

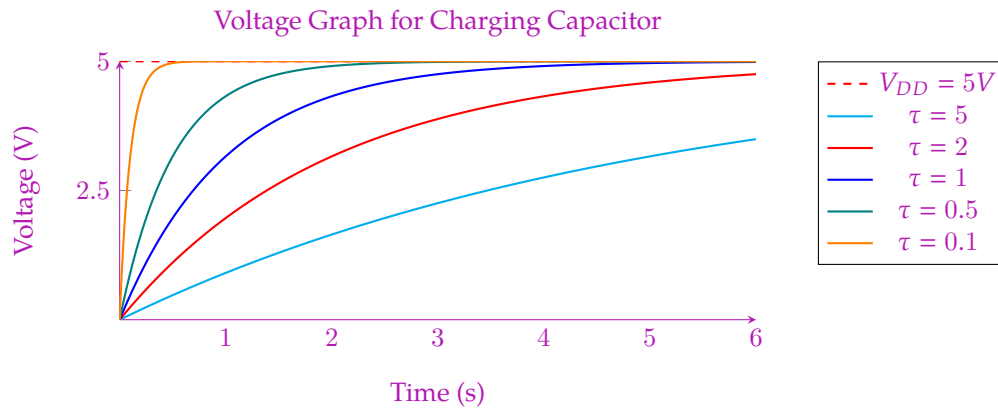
We've plotted the responses for a couple of  $\tau$  values below. As  $\tau$  approaches 0, the response  $V_c$  will approach an ideal square wave.



- f) Suppose we have a source  $V(t)$  that alternates between 0 and  $V_{DD} = 1V$ . Given  $RC = 0.1s$ , plot the response  $V_c$  if  $V_c(0) = 0$ .

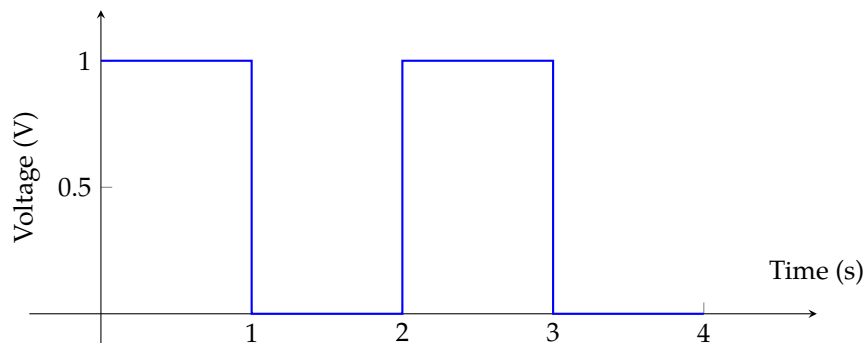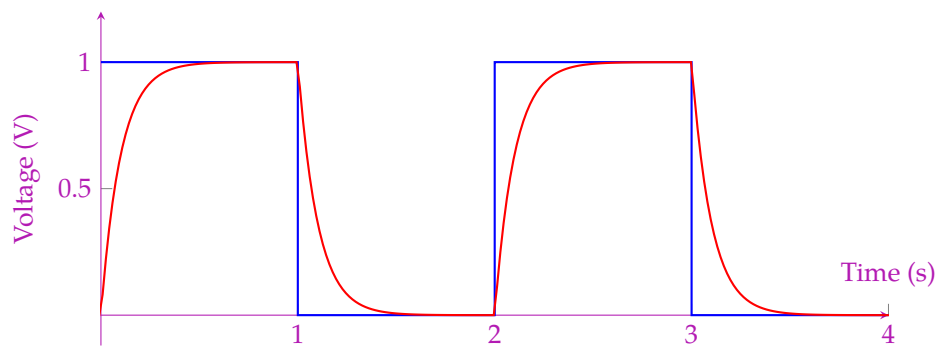**Answer**

The input switches between high and low every second while  $\tau = RC = 0.1s$ . This means the capacitor will charge and discharge for  $10\tau$  so we can approximate it as fully charged and discharged after 1 second.



g) Now suppose we have the same source  $V(t)$  but  $RC = 1$  s, plot the response  $V_c$  if  $V_c(0) = 0$ .

### Answer

The input has stayed the same while  $\tau = RC = 1$  s. This means the capacitor will only charge and discharge for one time constant or up to around 63%.

