

For this discussion, [Note 1](#) is helpful for the differential equations, and [Note j](#) covers the complex numbers fundamentals.

1. RC Circuits: Solving the Differential Equations

Recall that in [the last discussion](#), we were tasked with analyzing an example RC circuit (in [1](#)) and using element equations (governing equations for resistors and capacitors) to formulate a differential equation. This equation describes the time-varying behavior of this circuit. Specifically, we had the following differential equation:

$$RC \frac{dV_C(t)}{dt} + V_C(t) = V(t) \tag{1}$$

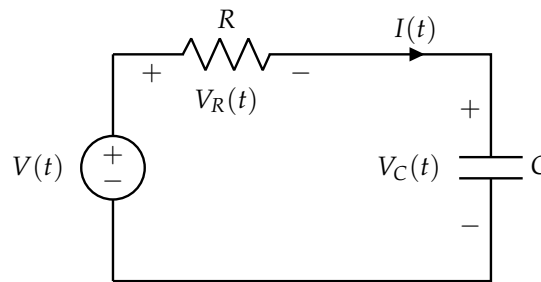


Figure 1: Sample RC Circuit

Our goal is to now solve this differential equation for the voltage across the capacitor, $V_C(t)$. Recall that, in the previous discussion and lecture, we covered two kinds of differential equations:

$$\frac{dx(t)}{dt} = \lambda x(t) \tag{2}$$

$$\frac{dx(t)}{dt} = \lambda x(t) + u \tag{3}$$

where $\lambda, u \in \mathbb{R}$. Eq. (2) has a solution of the form

$$x(t) = Ae^{bt} \tag{4}$$

for some constants $A, b \in \mathbb{R}$ that we have to find. We can solve the differential equation in eq. (3) by performing a change of variables operation. This will yield a new differential equation that resembles eq. (2), and reversing the change of variables operation will give us the solution to eq. (3).

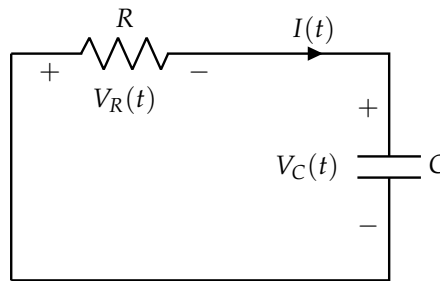


Figure 2: RC Circuit for part [1.a](#). Note that the voltage source has been turned off (0 V) for this subpart, and the initial voltage on the capacitor is V_{DD} .

- (a) Let's suppose that at $t = 0$, the capacitor is charged to a voltage V_{DD} ($V_C(0) = V_{DD}$). Let's also assume that $V(t) = 0$ for all $t \geq 0$ (voltage source is turned off). **Solve the differential equation for $V_C(t)$ for $t \geq 0$.**

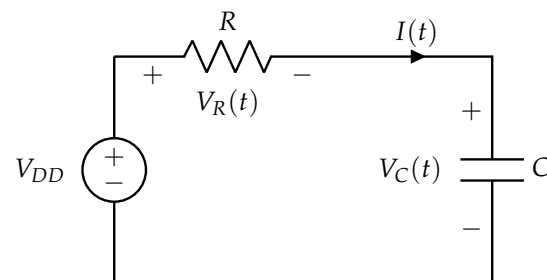


Figure 3: Circuit for part 1.b

- (b) Now, let's suppose that we start with an uncharged capacitor $V_C(0) = 0$. We apply some constant voltage $V(t) = V_{DD}$ across the circuit for all $t \geq 0$. **Solve the differential equation for $V_C(t)$ for $t \geq 0$.**
- (c) We now want to combine the principles from the previous two subparts to understand the voltage waveform when a switch occurs at some time t . Specifically, suppose that at $t = 0$, $V(t) = 0\text{ V}$, $V_C(0) = V_{DD}$. Then, at some $t = t_{\text{switch}}$, the voltage source is turned on $V(t) = V_{DD}$ for $t \geq t_{\text{switch}}$. **Find the equation for the overall capacitor voltage as a function of time (for times before and after t_{switch}).**


2. Complex Algebra (Review)

(a) Express the following values in polar forms: -1 , j , $-j$, $(j)^{\frac{1}{2}}$, and $(-j)^{\frac{1}{2}}$. Recall $j^2 = -1$, and the complex conjugate of a complex number is denoted with a bar over the variable. The complex conjugate is defined as follows: for a complex number $z = x + jy$, the complex conjugate $\bar{z} = x - jy$.

(b) Represent $\sin(\theta)$ and $\cos(\theta)$ using complex exponentials. (*Hint: Use Euler's identity $e^{j\theta} = \cos(\theta) + j\sin(\theta)$.*)

For the next parts, let $a = 1 - j\sqrt{3}$ and $b = \sqrt{3} + j$.

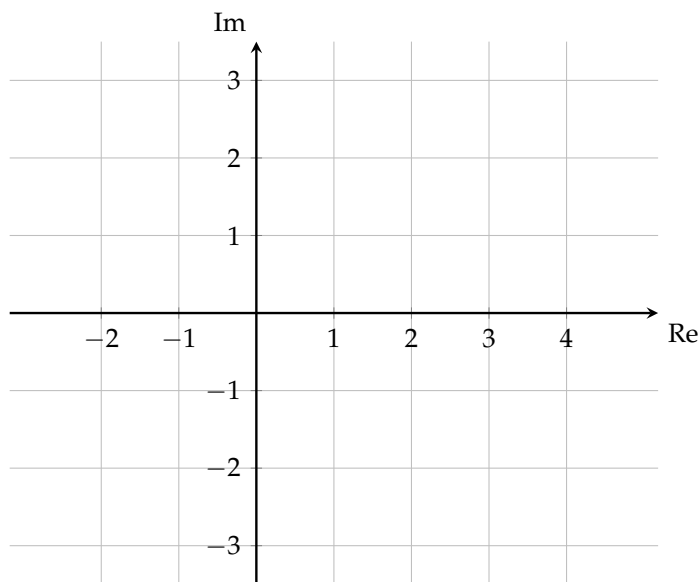(c) Show the number a in complex plane, marking the distance from origin and angle with real axis.



(d) Show that multiplying a with j is equivalent to rotating the complex number by $\frac{\pi}{2}$ or 90° in the complex plane.

(e) **(Practice)** For complex number $z = x + jy$ show that $|z| = \sqrt{z\bar{z}}$, where \bar{z} is the complex conjugate of z .

(f) **(Practice)** Express a and b in polar form.

(g) **(Practice)** Find ab , $a\bar{b}$, $\frac{a}{b}$, $a + \bar{a}$, $a - \bar{a}$, \overline{ab} , $\overline{a\bar{b}}$, and $(b)^{\frac{1}{2}}$.

Contributors:

- Neelesh Ramachandran.
- Anish Muthali.
- Brian Kilberg.
- Kuan-Yun Lee.
- Maruf Ahmed.