


1. Complex Algebra (Review)

(a) **Express the following values in polar forms:** -1 , j , $-j$, $(j)^{\frac{1}{2}}$, **and** $(-j)^{\frac{1}{2}}$. Recall $j^2 = -1$, and the complex conjugate of a complex number is denoted with a bar over the variable. The complex conjugate is defined as follows: for a complex number $z = x + jy$, the complex conjugate $\bar{z} = x - jy$.

(b) Represent $\sin(\theta)$ and $\cos(\theta)$ using complex exponentials. (*Hint:* Use Euler's identity $e^{j\theta} = \cos(\theta) + j\sin(\theta)$.)

For the next parts, let $a = 1 - j\sqrt{3}$ and $b = \sqrt{3} + j$.

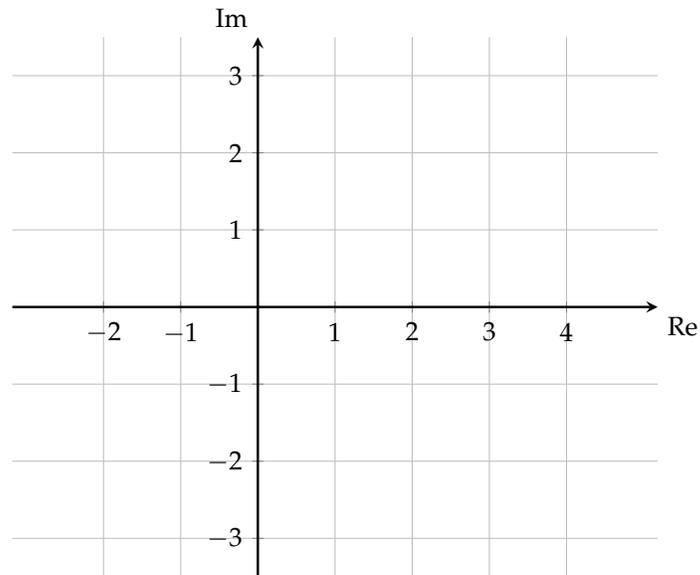(c) Show the number a in complex plane, marking the distance from origin and angle with real axis.



(d) Show that multiplying a with j is equivalent to rotating the complex number by $\frac{\pi}{2}$ or 90° in the complex plane.

(e) For complex number $z = x + jy$ show that $|z| = \sqrt{z\bar{z}}$, where \bar{z} is the complex conjugate of z .

(f) Express a and b in polar form.

(g) Find ab , $a\bar{b}$, $\frac{a}{b}$, $a + \bar{a}$, $a - \bar{a}$, \overline{ab} , $\overline{a\bar{b}}$, and $(b)^{\frac{1}{2}}$.

2. Introduction to Inductors

An inductor is a circuit element analogous to a capacitor; its voltage is proportional to the derivative of the current across it. That is:

$$V_L(t) = L \frac{dI_L(t)}{dt} \quad (1)$$

When first studying capacitors, we analyzed a circuit where a current source was directly attached to a capacitor. In Figure 1, we form the counterpart circuit for an inductor:

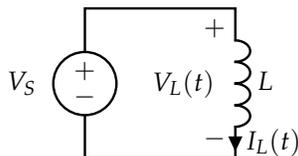


Figure 1: Inductor in series with a voltage source.

- (a) **What is the current through an inductor as a function of time? If the inductance is $L = 3\text{ H}$, what is the current at $t = 6\text{ s}$? Assume that the voltage source turns from 0 V to 5 V at time $t = 0\text{ s}$, and there's no current flowing in the circuit before the voltage source turns on, i.e. $I_L(0) = 0\text{ A}$.**

- (b) Now, we add some resistance in series with the inductor, as in Figure 2.


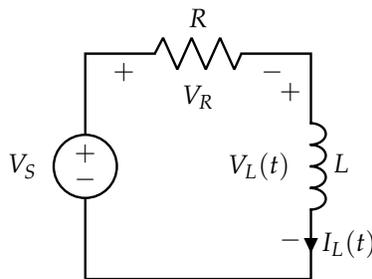



Figure 2: Inductor in series with a voltage source.

Solve for the current $I_L(t)$ and voltage $V_L(t)$ in the circuit over time, in terms of R, L, V_S, t . Note that $I_L(0) = 0$ A. Try to solve this equation by inspection. Otherwise, you can use the following integral for the particular solution (with the proper values and functions):

$$e^{-st} \int e^{st} b(t) dt$$

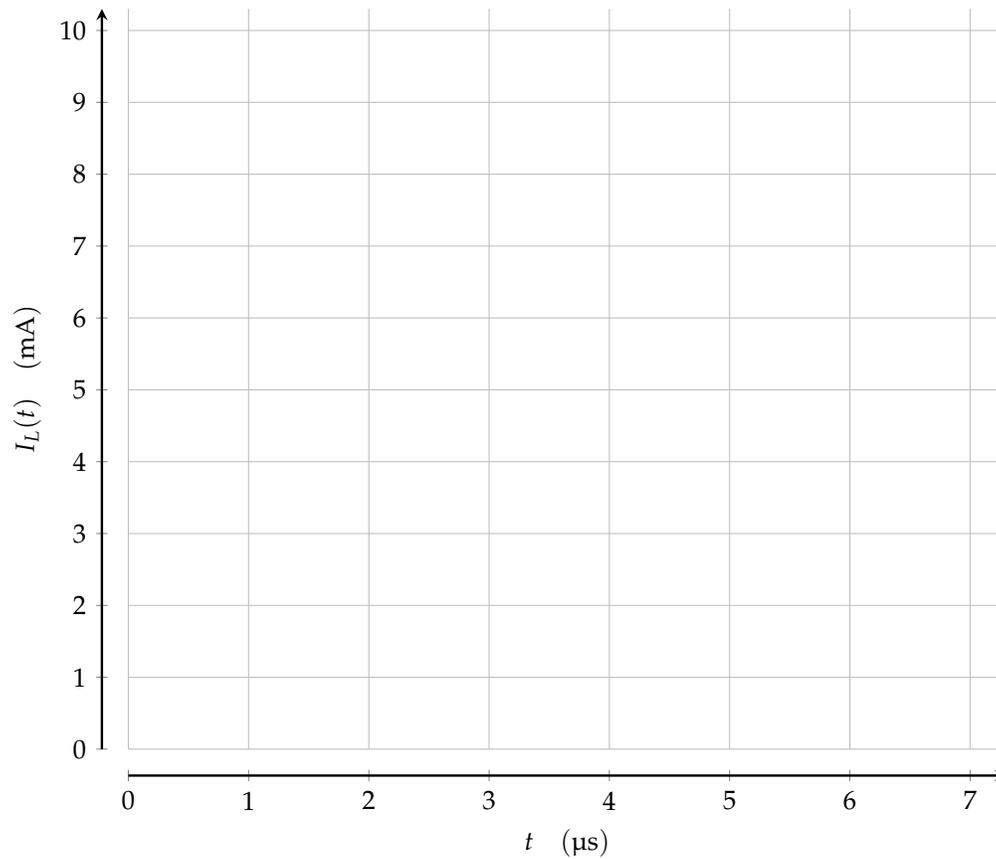- (c) Suppose $R = 500 \Omega, L = 1 \text{ mH}, V_S = 5 \text{ V}$. Plot the current through and voltage across the inductor ($I_L(t), V_L(t)$), as these quantities evolve over time.



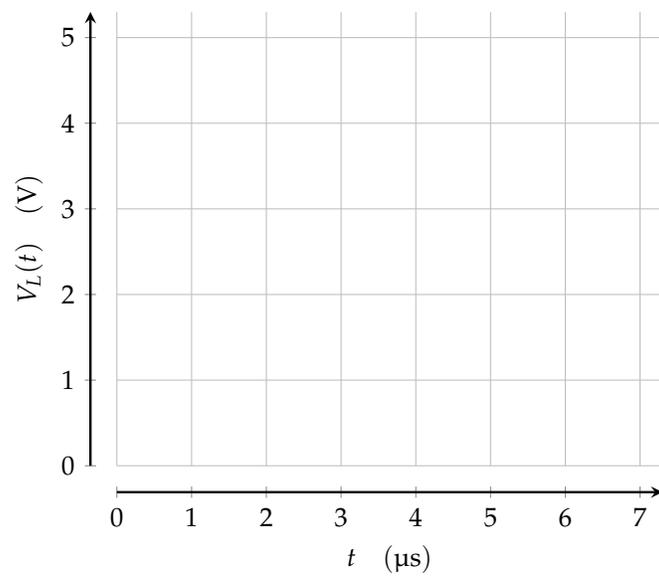**Contributors:**

- Chancharik Mitra.
- Nikhil Jain.
- Neelesh Ramachandran.
- Brian Kilberg.
- Kuan-Yun Lee.
- Maruf Ahmed.
- Anish Muthali.
- Kumar Krishna Agrawal.