

Discussion 3A

1. RL Circuit Solution Methods

Consider the following circuit:

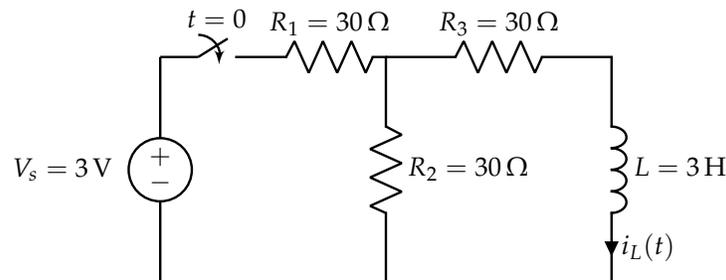


Figure 1

Before time $t = 0$, the circuit reaches a steady state. At time $t = 0$, the switch is closed. Our goal is to find the differential equation for the current through the inductor ($i_L(t)$). One method to approach this problem is to simply use Node Voltage Analysis (NVA). To start, we would define the node voltages in our circuit (including a ground node).

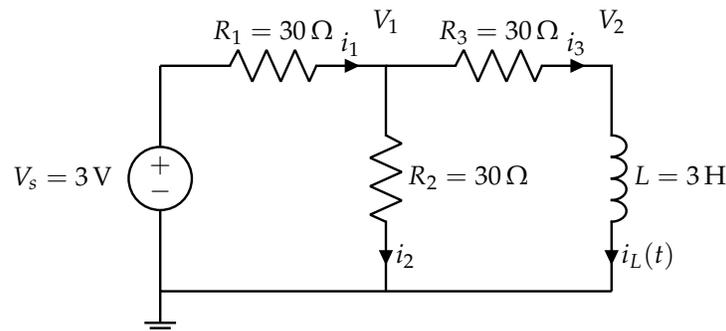


Figure 2

Then, we can set up a system of equations using KCL/KVL to find our desired differential equation.

First, let's perform KCL on the node with defined voltage V_1 .

$$\begin{aligned}
 i_1 &= i_2 + i_3 \\
 \frac{V_s - V_1}{R_1} &= \frac{V_1 - 0}{R_2} + \frac{V_1 - V_2}{R_3} \\
 \frac{3 - V_1}{30} &= \frac{V_1 - 0}{30} + \frac{V_1 - V_2}{30} \\
 V_1 &= 1 + \frac{V_2}{3}
 \end{aligned}$$

Now, let's perform KCL on the node with the defined voltage V_2 .

Note that $V_2 - 0 = V_2$ is the voltage across the inductor so by the inductor I-V relationship, $V_2 = L \frac{di_L}{dt} = 3 \frac{di_L}{dt}$.

$$\begin{aligned} i_3 &= i_L \\ \frac{V_1 - V_2}{R_3} &= i_L \\ \frac{V_1 - V_2}{30} &= i_L \\ \frac{V_1}{30} &= \frac{V_2}{30} + i_L \\ \frac{1}{30} \left(1 + \frac{V_2}{3} \right) &= \frac{V_2}{30} + i_L \\ \frac{1}{45} V_2 + i_L &= \frac{1}{30} \\ \frac{1}{45} \left(3 \frac{di_L}{dt} \right) + i_L &= \frac{1}{30} \\ \frac{di_L}{dt} + 15i_L &= \frac{1}{2} \end{aligned}$$

Thus, we have found the differential equation! However, this method required solving a system of equations; is there another way?

- (a) Another way to approach the problem is to use equivalence. Simplify the voltage source and resistor network into a voltage source and resistor using Thevenin equivalence. Then, reconnect the inductor and **find the differential equation for $i_L(t)$** .

For reference, here is the circuit that we want to simplify using Thevenin equivalence:

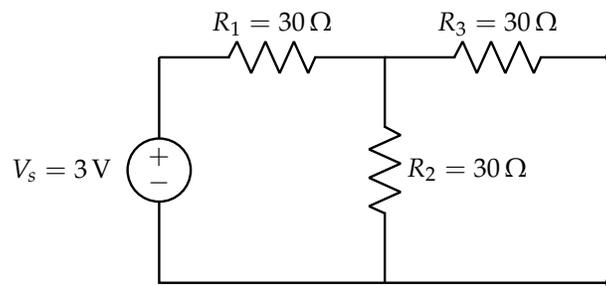


Figure 3

(HINT: Your final differential equation should be the same as the one from the problem introduction.)

- (b) Now, let's start solving the differential equation. First, **find the initial condition $i_L(0)$ for our system**. Remember that the current through the inductor cannot change instantaneously (since this would correspond to infinite voltage through the inductor I-V relationship) so $i_L(0)$ will be the same as the steady state value from $t < 0$.

(HINT: If there is no voltage/current sources connected to this system, can there be any nonzero currents / voltage differences in the system during steady-state?)



- (c) **(OPTIONAL)** Now that we have our differential equation and initial condition, we can now solve for the current $i_L(t)$ as a function of time. **Solve the system for $i_L(t)$** . If you can, try to solve this by inspection. Otherwise, solve using the homogeneous and particular solution method.

2. Transistor Behavior


Unlocked by Lectures 1 and 2

For all NMOS devices in this problem, $V_{tn} = 0.5\text{ V}$. For all PMOS devices in this problem, $|V_{tp}| = 0.6\text{ V}$. **Note: For this problem, we are also using the resistor-switch model for a transistor.**

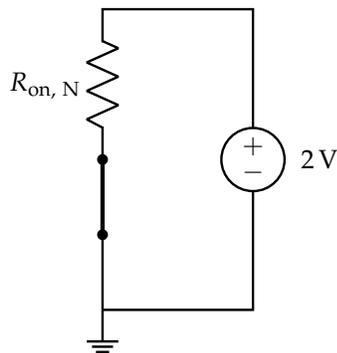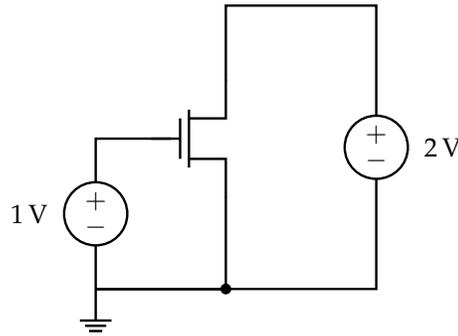(a) Which is the equivalent circuit as seen from the voltage source on the right-hand side of the circuit? **Fill in the correct bubble.**




Circuit A

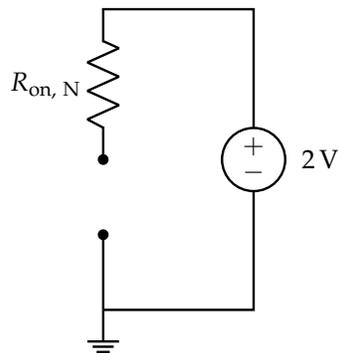


Circuit B


| | A | B |
|---------------------------|-----------------------|-----------------------|
| Equivalent Circuit | <input type="radio"/> | <input type="radio"/> |

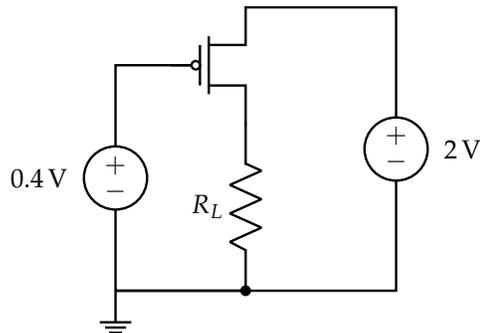(b) Which is the equivalent circuit as seen from the voltage source on the right-hand side of the circuit? **Fill in the correct bubble.**




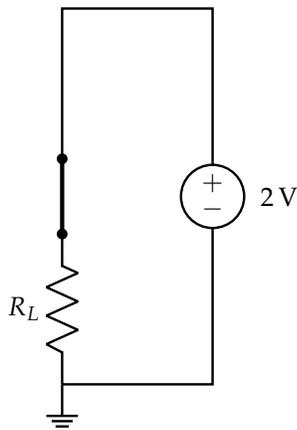

Circuit A

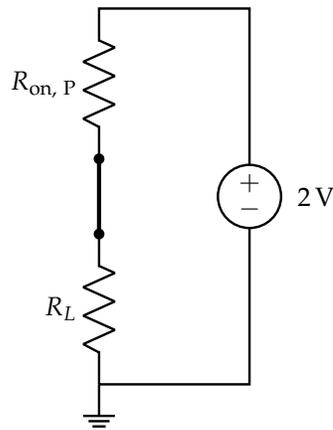



Circuit B

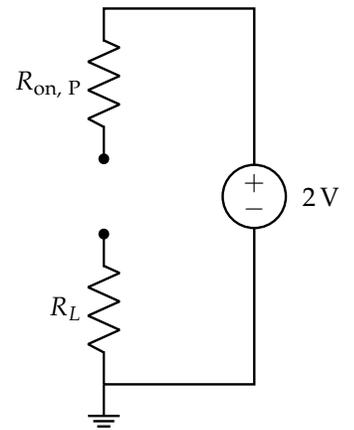


Circuit C

| | A | B | C |
|---------------------------|-----------------------|-----------------------|-----------------------|
| Equivalent Circuit | <input type="radio"/> | <input type="radio"/> | <input type="radio"/> |

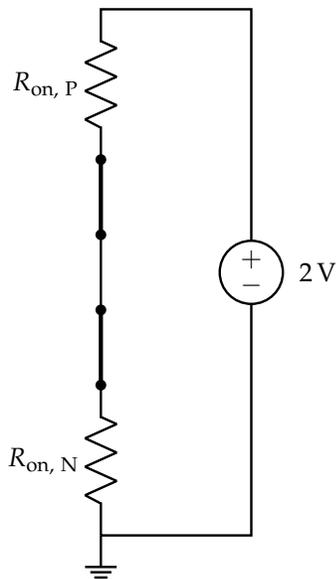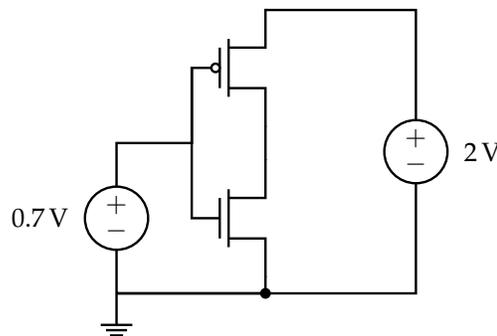
(c) Which is the equivalent circuit as seen from the voltage source on the right-hand side of the circuit? **Fill in the correct bubble.**




Circuit A

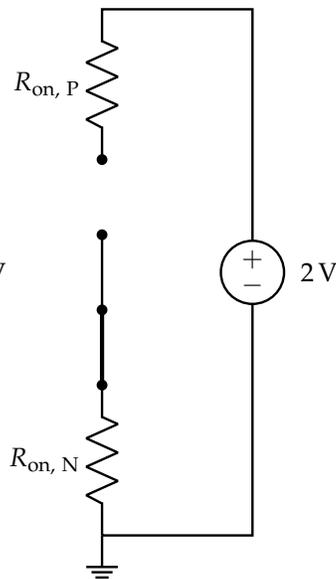

Circuit B

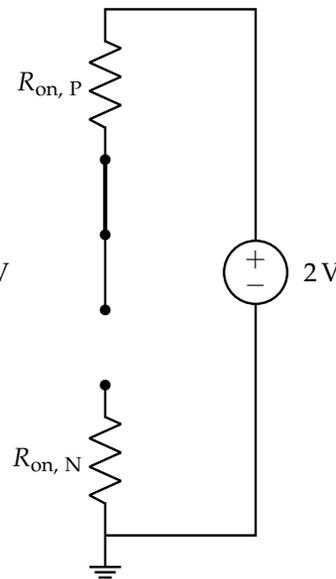

Circuit C

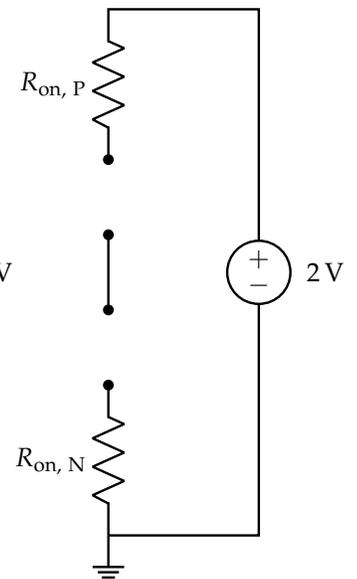

Circuit D

| | A | B | C | D |
|---------------------------|-----------------------|-----------------------|-----------------------|-----------------------|
| Equivalent Circuit | <input type="radio"/> | <input type="radio"/> | <input type="radio"/> | <input type="radio"/> |

Contributors:

- Nikhil Jain.
- Sidney Buchbinder.
- Anant Sahai.
- Chancharik Mitra.