

Discussion 3A

Note 5 along with corresponding lectures are most relevant to this discussion worksheet.

1. Analyzing a Second-Order Circuit (Adapted from Hambley Example 4.5)

A DC source is connected to a series RLC circuit by a switch that closes at $t = 0$ as shown in Figure 3. The initial conditions are $i(0) = 0$ and $v_C(0) = 0$.

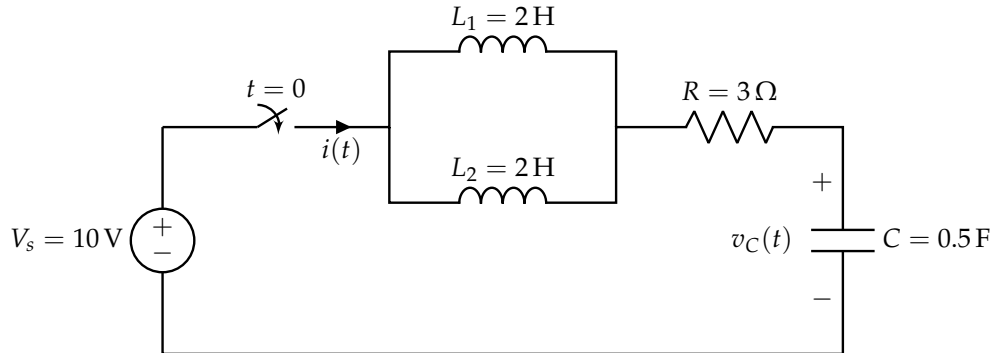


Figure 1: RLC Circuit

- (a) Find the equivalent inductance and redraw the circuit as a standard series RLC.

Solution: Recall that the equivalent inductance of two inductors in parallel is given by $L_{eq} = \left(\frac{1}{L_1} + \frac{1}{L_2}\right)^{-1}$.
Therefore,

$$L = \left(\frac{1}{2} + \frac{1}{2}\right)^{-1} = 1 \text{ H} \quad (1)$$

The resulting circuit is as follows:

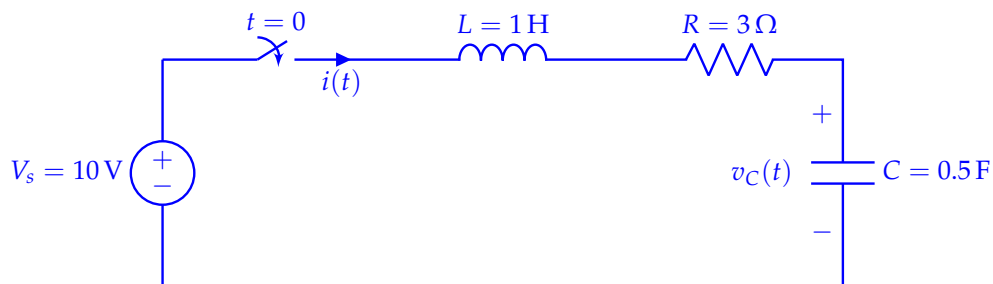


Figure 2: RLC Circuit

- (b) Write the differential equation for $v_C(t)$.

Solution: First, we can write an express for the current in terms of the voltage across the capacitance:

$$i(t) = C \frac{dv_C(t)}{dt} \quad (2)$$

Then, writing a KVL equation for the circuit, we have:

$$v_L(t) + v_R(t) + v_C(t) = V_s \quad (3)$$

$$L \frac{di(t)}{dt} + Ri(t) + v_C(t) = V_s \quad (4)$$

$$(5)$$

Substituting in the expression for current $i(t)$, we get:

$$LC \frac{d^2v_C(t)}{dt^2} + RC \frac{dv_C(t)}{dt} + v_C(t) = V_s \quad (6)$$

$$\frac{d^2v_C(t)}{dt^2} + \frac{R}{L} \frac{dv_C(t)}{dt} + \frac{1}{LC} v_C(t) = \frac{V_s}{LC} \quad (7)$$

- (c) **Redraw the circuit in steady state and find the steady state value for $v_C(t)$.**

Solution: Recall that at steady state, inductors act as shorts and capacitors act as open circuits. Using this knowledge, our redrawn circuit is as follows:

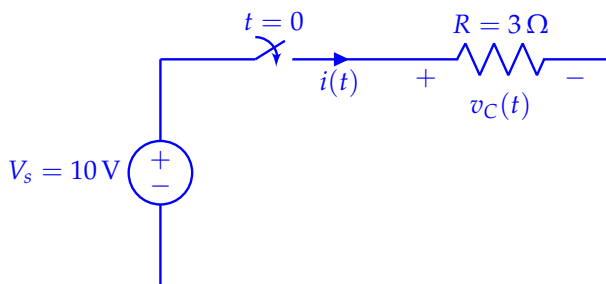


Figure 3: RLC Circuit

Because no current flows into the node with an open circuit, $v_C(t) = V_s = 10\text{ V}$.

- (d) **Solve for $v_C(t)$ if $R = 3\ \Omega$.**

Solution:

Step 1: Solve for the homogeneous solution:

Our equation is in the form:

$$\frac{d^2x(t)}{dt^2} + 2\alpha \frac{dx(t)}{dt} + \omega_0^2 x(t) = f(t) \quad (8)$$

where $f(t) = \frac{V_s}{LC}$ which is a constant. Thus, we know that our solution for $v_C(t)$ will be a combination of the particular solution $v_{Cp}(t)$ and the complementary solution $v_{Cc}(t)$.

Since we have a DC source, we know that the transient or complementary solution will go to 0 over time. Thus, our current and voltage are steady/constant and we can replace inductors with short circuits and capacitors with open circuits. This leads us to determine that $v_{Cp}(t) = V_s = 10\text{ V}$.

Next, we will find the complementary solution $v_{Cc}(t)$ or the homogeneous solution of our differential equation. When finding the complementary solution, we will follow the following 3 steps:

- i. Determine the damping ratio and roots of the characteristic equation
- ii. Select the appropriate form for the homogeneous solution, depending on the value of the damping ratio
- iii. Add the homogeneous solution to the particular solution and determine the values of the coefficients (K_1 and K_2) based on initial conditions.

Here, we have $R = 3\Omega$, so

$$\omega_0 = \sqrt{\frac{1}{LC}} = \sqrt{2} \quad (9)$$

and the damping ratio $\alpha = \frac{R}{2L} = \frac{3}{2}$. Since $\alpha > \omega_0$, we have an overdamped case. **Important:** We consider the exponential candidate solution for our homogeneous solution (i.e. $v_h = e^{st}$). Using this, our differential equation decomposes into:

$$s^2 e^{st} + 3s e^{st} + 2e^{st} = 0 \quad (10)$$

We can view this equation as being in quadratic form (i.e. use the quadratic formula)!

Solving for the roots of our characteristic equation we have:

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad (11)$$

$$= -1.5 + \sqrt{\frac{9}{4} - 2} \quad (12)$$

$$= -1 \quad (13)$$

and

$$s_2 = -\alpha - \omega_0 \sqrt{\alpha^2 - 1} \quad (14)$$

$$= -1.5 - \sqrt{\frac{9}{4} - 1} \quad (15)$$

$$= -2 \quad (16)$$

Step 2: Solve for the particular solution using steady-state analysis (note: refer to part d for more details on this):

We know that the homogeneous solution has the form $K_1 e^{s_1 t} + K_2 e^{s_2 t}$ leading us to have the general solution:

$$v_C(t) = v_{Cp}(t) + v_{Cc}(t) = 10 + K_1 e^{s_1 t} + K_2 e^{s_2 t} \quad (17)$$

Step 3: Utilize the initial conditions to solve for solution coefficients:

Now, we will find the values of K_1 and K_2 using the given initial conditions. It is given $v_C(0) = 0$ V. This gives us that:

$$10 + K_1 + K_2 = 0 \quad (18)$$

Furthermore, since $i(0) = 0$ A we also know that $i(0) = C \frac{dv_C(0)}{dt}$ and thus $\frac{dv_C(0)}{dt} = 0$. Taking the derivative of Equation 17 and plugging in $t = 0$, we get


$$s_1 K_1 e^{s_1(0)} + s_2 K_2 e^{s_2(0)} = 0 \quad (19)$$

$$s_1 K_1 + s_2 K_2 = 0 \quad (20)$$


Now, solving the systems of equations, we get that $K_1 = -20$ and $K_2 = 10$. Substituting these values into Equation 17, we get our final solution:

$$v_C(t) = 10 - 20e^{-t} + 10e^{-2t} \quad (21)$$

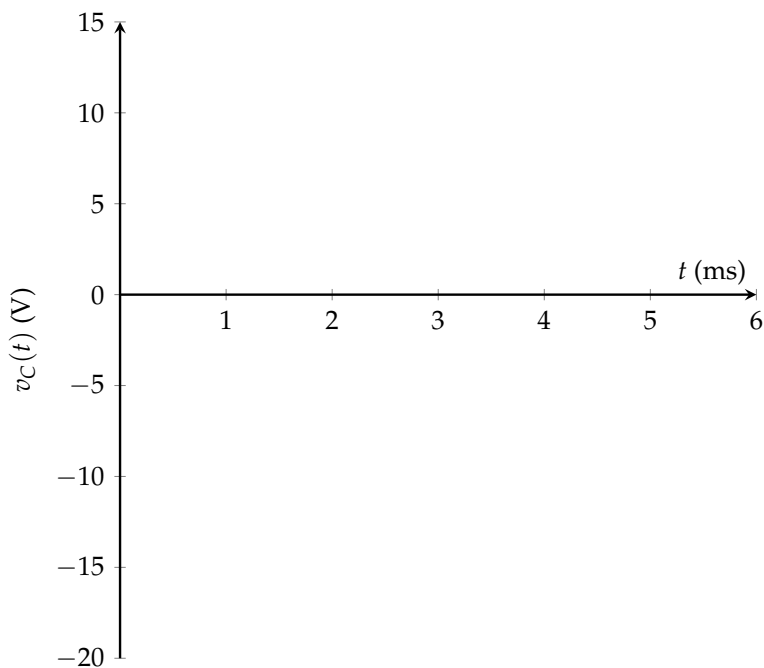- (e) **Plot the equation you calculated for $v_C(t)$.** It may be helpful to draw out each term in your general solution and then add them together.



Solution:

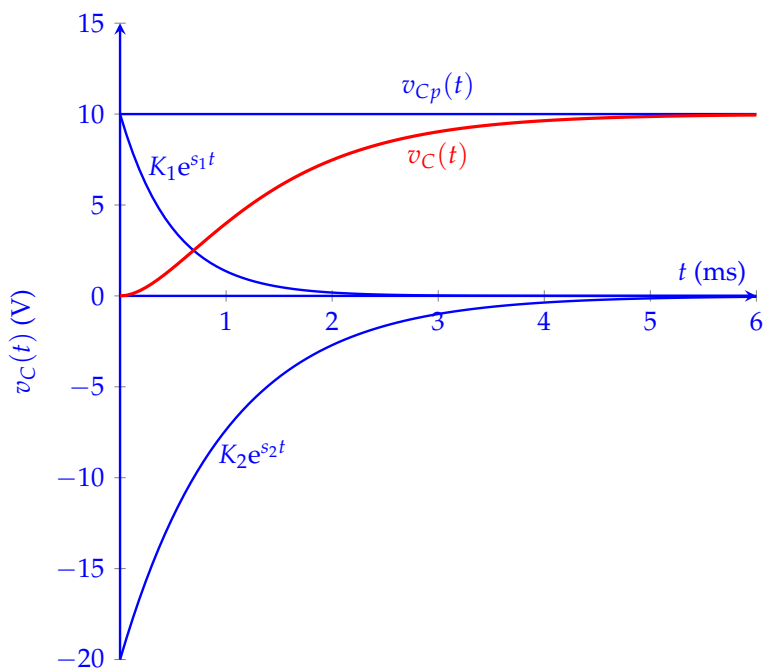

Contributors:

- Chancharik Mitra.
- Nikhil Jain.