

Discussion 4A

1. Using the Transfer Function to Determine the Output (Adapted from Hambley Example 6.1)

The transfer function $H(j\omega)$ of a filter is shown in Figure 1.

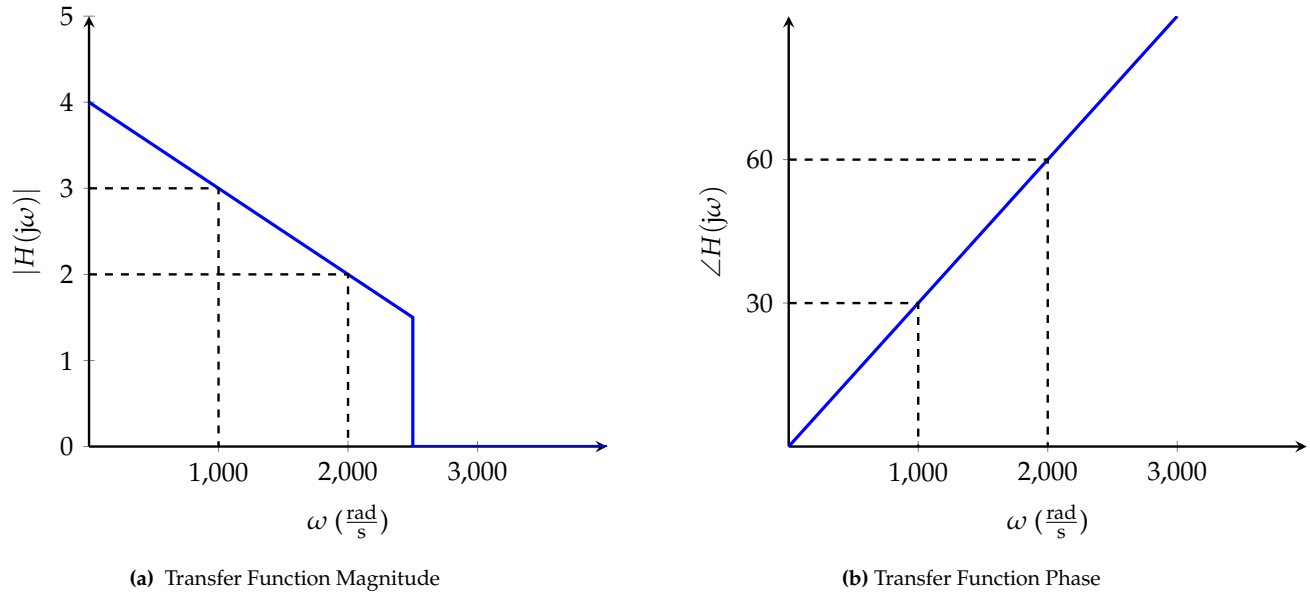


Figure 1: Transfer Function $H(j\omega)$

If the input signal is given by

$$v_{in}(t) = 2 \cos(1000t + 40^\circ) + 2 \cos(2000t) \quad (1)$$

find an expression for the output of the filter $v_{out}(t)$.

Solution: Since our input is composed on two sinusoids with different frequencies we need to analyze them separately. Let's call:

$$v_{in,1} = 2 \cos(1000t + 40^\circ) \quad (2)$$

$$v_{in,2} = 2 \cos(2000t) \quad (3)$$

Let's first analyze the output of $v_{in,1}$. By inspection, we see that $\omega = 1000$. Using the provided graphs of the magnitude and phase, we can determine $|H(j1000)| = 3$ and $\angle H(j1000) = 30^\circ$. Putting this together we have:

$$H(j1000) = 3e^{j30^\circ} = \frac{\tilde{V}_{out,1}}{\tilde{V}_{in,1}} \quad (4)$$

The phasor for the input signal is $\tilde{V}_{in,1} = 2e^{j40^\circ}$, so solving for the output phasor we have:

$$\tilde{V}_{out,1} = H(j1000)\tilde{V}_{in,1} \quad (5)$$

$$= 3e^{j30^\circ} \times 2e^{j40^\circ} \quad (6)$$

$$= 6e^{j70^\circ} \quad (7)$$

Converting the output phasor back into a time function, we have:

$$v_{\text{out},1}(t) = 6 \cos(1000t + 70^\circ) \quad (8)$$

Now, we will apply the same process for $v_{\text{in},2}$. We observe that $\omega = 2000$. Then using the graphs we know that $|H(j2000)| = 2$ and $\angle H(j2000) = 60^\circ$. We also can represent $v_{\text{in},2}(t)$ as a phasor which would be $2e^{j0^\circ} = 2$. Putting this together and solving for the output phasor,

$$\tilde{V}_{\text{out},2} = H(j2000)\tilde{V}_{\text{in},2} \quad (9)$$

$$= 2e^{j60^\circ} \times 2 \quad (10)$$

$$= 4e^{j60^\circ} \quad (11)$$

Converting this into a time function, we get:

$$v_{\text{out},2}(t) = 4 \cos(2000t + 60^\circ) \quad (12)$$

Now combining the two output sinusoids we get:

$$v_{\text{out}}(t) = 6 \cos(1000t + 70^\circ) + 4 \cos(2000t + 60^\circ) \quad (13)$$

2. RC Filter (Hambley Example 6.3)

Suppose you have the RC circuit shown in Figure 2.

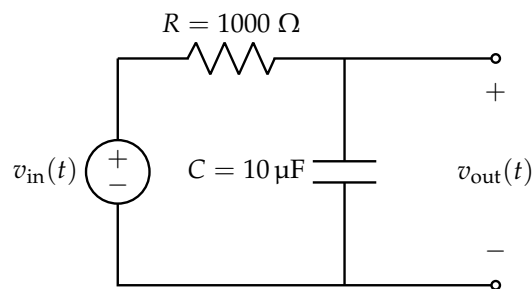


Figure 2: RC Lowpass Circuit

- (a) **Determine the transfer function $H(j\omega)$ of the given circuit. Then, classify what type of filter this circuit is.** Recall that the transfer function $H(j\omega)$ is defined as the ratio of the output phasor to the input phasor.

$$H(j\omega) = \frac{\tilde{V}_{\text{out}}}{\tilde{V}_{\text{in}}} \quad (14)$$

Solution: To determine the transfer function, we can apply a sinusoidal input signal with phasor \tilde{V}_{in} and then analyze the behavior of the circuit as a function of the source frequency ω . The phasor current is given by dividing the input voltage phasor by the complex impedance of the circuit.

$$\tilde{I} = \frac{\tilde{V}_{\text{in}}}{R + \frac{1}{j\omega C}} \quad (15)$$

The phasor for the output voltage would be the product of the phasor current and the impedance of the capacitor:

$$\tilde{V}_{\text{out}} = \frac{1}{j\omega C} \tilde{I} \quad (16)$$

Then, substituting in our expression for \tilde{I} , we have:

$$\tilde{V}_{\text{out}} = \frac{1}{j\omega C} \times \frac{\tilde{V}_{\text{in}}}{R + \frac{1}{j\omega C}} \quad (17)$$

$$\frac{\tilde{V}_{\text{out}}}{\tilde{V}_{\text{in}}} = \frac{1}{j\omega C \left(R + \frac{1}{j\omega C} \right)} \quad (18)$$

$$H(j\omega) = \frac{1}{1 + j\omega RC} \quad (19)$$

An alternate solution (which can actually be applied for a lot of filters and is more concise than the previous method) involves applying the voltage divider principle with the complex impedances of the circuit.

$$\tilde{V}_{\text{out}} = \frac{Z_C}{Z_R + Z_C} \tilde{V}_{\text{in}} \quad (20)$$

$$\frac{\tilde{V}_{\text{out}}}{\tilde{V}_{\text{in}}} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \quad (21)$$

$$H(j\omega) = \frac{1}{1 + j\omega RC} \quad (22)$$

Plugging in the values for R and C , we get that our transfer function is:

$$H(j\omega) = \frac{1}{1 + j\omega(1000 \times 10 \times 10^{-6})} = \frac{1}{1 + j\frac{\omega}{100}} \quad (23)$$

Now, to determine what type of filter this is, we can analyze the behavior for low and high ω . As $\omega \rightarrow 0$, notice that the magnitude of the transfer function $H(j\omega)$ will get closer and closer to 1. On the other hand as $\omega \rightarrow \infty$, we see that the magnitude of the transfer function goes to 0. Therefore, we have the our circuit will attenuate/reduce high frequency and maintain low frequency signals, which leads us to conclude that we have a lowpass RC filter.

(b) Suppose, that you are given:

$$v_{in}(t) = 5 \cos(10t) + 5 \cos(100t) + 5 \cos(1000t) \quad (24)$$

Find an expression for the output signal $v_{out}(t)$ (please use approximations to simplify the calculations).

Solution: Let's call $v_{in,1} = 5 \cos(10t)$, $v_{in,2} = 5 \cos(100t)$, and $v_{in,3} = 5 \cos(1000t)$ and their phasors $\tilde{V}_{in,1}$, $\tilde{V}_{in,2}$, and $\tilde{V}_{in,3}$, respectively.

We have that:

$$\tilde{V}_{in,1} = 5e^{j0^\circ} = 5 \quad (25)$$

$$\tilde{V}_{in,2} = 5e^{j0^\circ} = 5 \quad (26)$$

$$\tilde{V}_{in,3} = 5e^{j0^\circ} = 5 \quad (27)$$

Now, we must analyze the value of the transfer function at each of the different input frequency values. We can notice that $\omega_1 = 10 \frac{\text{rad}}{\text{s}}$, $\omega_2 = 100 \frac{\text{rad}}{\text{s}}$, and $\omega_3 = 1000 \frac{\text{rad}}{\text{s}}$.

$$H(\omega_1) = H(j10) = \frac{1}{1 + j\frac{10}{100}} \approx 1 \quad (28)$$

$$H(\omega_2) = H(j100) = \frac{1}{1 + j\frac{100}{100}} = \frac{1}{\sqrt{2}}e^{-j45^\circ} \quad (29)$$

$$H(\omega_3) = H(j1000) = \frac{1}{1 + j\frac{1000}{100}} \approx \frac{1}{10}e^{-j90^\circ} \quad (30)$$

The output phasor for each input phasor is simply the product of the input phasor with the transfer function evaluated at the given frequency $\tilde{V}_{out} = H(j\omega)\tilde{V}_{in}$. Thus we have:

$$\tilde{V}_{out,1} = H(j\omega_1)\tilde{V}_{in,1} = 1 \times 5 \quad (31)$$

$$= 5 \quad (32)$$

$$\tilde{V}_{out,2} = H(j\omega_2)\tilde{V}_{in,2} = \frac{1}{\sqrt{2}}e^{-j45^\circ} \times 5 \quad (33)$$

$$= \frac{5}{\sqrt{2}}e^{-j45^\circ} \quad (34)$$

$$\tilde{V}_{out,3} = H(j\omega_3)\tilde{V}_{in,3} = \frac{1}{10}e^{-j90^\circ} \times 5 \quad (35)$$

$$= \frac{1}{2}e^{-j90^\circ} \quad (36)$$

Converting the output phasors into their sinusoidal representations, we get:

$$v_{\text{out},1}(t) = 5 \cos(10t) \quad (37)$$

$$v_{\text{out},2}(t) = \frac{5}{\sqrt{2}} \cos(100t - 45^\circ) \quad (38)$$

$$v_{\text{out},3}(t) = \frac{1}{2} \cos(1000t - 90^\circ) \quad (39)$$

Lastly, we sum together the output components to get:

$$v_{\text{out}} = 5 \cos(10t) + \frac{5}{\sqrt{2}} \cos(100t - 45^\circ) + \frac{1}{2} \cos(1000t - 90^\circ) \quad (40)$$

The important concept to understand here is that each input signal is impacted differently by the filter due to their varying frequencies. You can see that the $\omega = 10 \frac{\text{rad}}{\text{s}}$ input signal did not change much in amplitude and phase. On the other hand $\omega = 100 \frac{\text{rad}}{\text{s}}$ had its amplitude reduced by a factor of $\frac{1}{\sqrt{2}}$ and phase shifted by -45° . Lastly the $\omega = 1000 \frac{\text{rad}}{\text{s}}$ signal is reduced by a whole order of magnitude (10^{-1}), demonstrating the lowpass behavior of the filter.

3. LR Filter (Hambley Exercise 6.5)

Suppose you are given the following circuit:

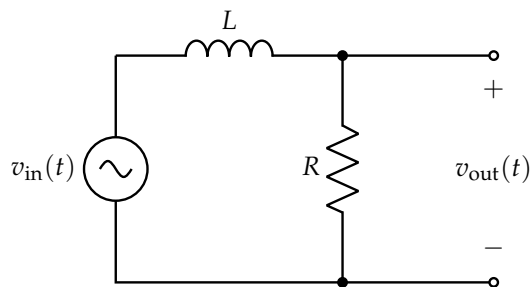


Figure 3: LR Circuit

Derive the transfer function of this filter, classify what type of filter it is, and determine an expression for the cutoff frequency ω_c . (Note: The cutoff frequency can also be called the -3dB frequency, -3dB point, half-power frequency, break frequency, etc. You should be familiar with these equivalent terms since different books and courses may use different terminology to refer to the same concept.)

Solution: Let's first convert our circuit into the phasor domain.

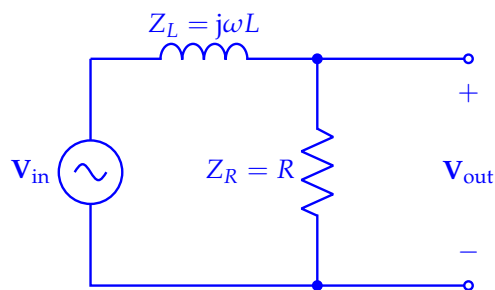


Figure 4: LR Circuit

Now, we can apply the voltage divider principle to write \tilde{V}_{out} in terms of \tilde{V}_{in} . You can also apply node-voltage analysis to solve for the transfer function as well.

$$\tilde{V}_{out} = \frac{Z_R}{Z_R + Z_L} \tilde{V}_{in} \quad (41)$$

$$\tilde{V}_{out} = \frac{R}{R + j\omega L} \tilde{V}_{in} \quad (42)$$

$$\frac{\tilde{V}_{out}}{\tilde{V}_{in}} = \frac{R}{R + j\omega L} \quad (43)$$

$$H(j\omega) = \frac{R}{R + j\omega L} \quad (44)$$

$$H(j\omega) = \frac{1}{1 + j\omega \frac{L}{R}} \quad (45)$$

Notice that we can rewrite our transfer function to take on the same form as the low pass filter:

$$H(j\omega) = \frac{1}{1 + j\frac{\omega}{\omega_c}} = \frac{1}{1 + j\frac{\omega}{\frac{R}{L}}} \quad (46)$$

Another way to determine that this is a lowpass filter is to analyze the magnitude of the transfer function as $\omega \rightarrow 0$ and $\omega \rightarrow \infty$. As $\omega \rightarrow 0$, we notice that the magnitude of the filter approaches 1, whereas when $\omega \rightarrow \infty$, the magnitude of the denominator will go to ∞ , which indicates that the magnitude of the overall transfer function will go to 0. This behavior of maintaining low frequency signals but reducing high frequency signals makes it a lowpass filter.

For this LR filter, we have that the cutoff frequency is:

$$\omega_c = \frac{R}{L} \quad (47)$$