

## 1 Inverter, Capacitor, and Delay

We will now work towards understanding delays in digital circuits. Here, we consider a circuit where the output node  $V_{out}$  of an inverter is connected to a capacitor. Such capacitance is often used to model other logic gates or transistors being driven by, or *loading* the inverter. In the absence of such a capacitive load, the output of the inverter  $V_{out}$  switches immediately after the input  $V_{in}$  switches.

 


Figure 1: CMOS Inverter driving a capacitive load.

In this problem, we will be using the resistor-switch model of a transistor for analysis. These models have been shown here for your reference. Furthermore, the threshold voltages for the transistors are  $V_{tn} = \frac{V_{DD}}{10}$  and  $V_{tp} = \frac{-V_{DD}}{10}$ .

 


Figure 2: Transistor Resistor-switch models for NMOS and PMOS transistors.

- a) Assume that  $V_{in}$  is held at 0 for a long time and then, at time  $t_0$ , it is switched to  $V_{DD}$ . Draw equivalent circuits before and after  $t_0$  using the resistor switch model for the transistors in the inverter.
- b) What is the state of the capacitor  $C_{load}$  at  $t = t_0$ ? Will it charge or discharge from this point on?
- c) Write out a differential equation governing the evolution of  $V_{out}$  after  $t_0$ . How long will it take after  $t_0$  for the output voltage  $V_{out}$  to drop below  $V_{tn} = \frac{V_{DD}}{10}$  so that a subsequent NMOS transistor will switch from on to off?

## 2 Differential equations with piecewise constant inputs

Let  $x(\cdot)$  be a solution to the following differential equation:

$$\frac{d}{dt} x(t) = \lambda (x(t) - u(t)). \quad (1)$$

Let  $T > 0$ . Let  $x[\cdot]$  "sample"  $x(\cdot)$  as follows:

$$x[n] = x(nT). \quad (2)$$

Assume that  $u(\cdot)$  is constant between samples of  $x(\cdot)$ , i.e.

$$u(t) = u[n] \quad \text{when} \quad nT \leq t < (n+1)T. \quad (3)$$

The above described system can be seen as an RC circuit with piecewise constant voltage applied where  $\lambda = -\frac{1}{RC}$  and  $u[n] = V_{in}(t)$  is kept constant when  $nT \leq t < (n+1)T$ .

 


Figure 3: Example Circuit

The solution for the above system is therefore given by

$$x(nT + \tau) = e^{\lambda\tau} x[n] + (1 - e^{\lambda\tau})u[n] \quad \text{for any } n \text{ and } 0 \leq \tau < T. \quad (4)$$

From the solution above, the relation between  $x[n]$  and  $x[n+1]$  is given by

$$x[n+1] = e^{\lambda T} x[n] + (1 - e^{\lambda T})u[n].$$

- a) Solve differential equation (1) for  $nT \leq t \leq (n+1)T$  with the initial condition  $x(nT) = x[n]$  and  $u(t) = u[n]$  for  $nT \leq t \leq (n+1)T$ . Show that the solution is exactly (4).

- b) Let  $T = 1$  and  $\lambda = -100$ . Sketch a piecewise constant input  $u[\cdot]$  of your choice, then sketch  $x(t)$ . Mark  $x[n]$ . Your sketch doesn't have to be exact, but you should be able to supply analysis to

justify why it looks a certain way: how are you using the fact that  $\lambda T$  is large and negative?

c) Let  $T = 1$  and  $\lambda = -1$ . Define  $u[n]$  as follows:

$$u[n] = \begin{cases} 1, & n \text{ is even} \\ -1, & n \text{ is odd} \end{cases} . \quad (5)$$

Sketch  $x(t)$ .

### 3 A circuit with two capacitors

Consider the following circuit given in Figure 4. The devices are set to the following values:  $C_1 = 1\mu F$ ,  $C_2 = \frac{1}{3}\mu F$ ,  $R_1 = \frac{1}{3}M\Omega$ ,  $R_2 = \frac{1}{2}M\Omega$ .

 


Figure 4: Two dimensional system: a circuit with two capacitors, like the one in lecture.

- a) Write the differential equations for the circuit above with the variables being  $V_{C1}$  and  $V_{C2}$ . The result should only contain  $V_{C1}$ ,  $V_{C2}$  and  $V_{in}$  with capacitance and resistance plugged in with their values given above.