

⚠ Students have either already taken or started taking this quiz, so be careful about editing it. If you change any quiz questions in a significant way, you may want to consider regrading students who took the old version of the quiz.

Points 15 ✔ Published



Details

Questions


Show Question Details

⋮ **Question 1** Pick 1 questions, 4.5 pts per question



⋮ **Question**

Given the following circuit,

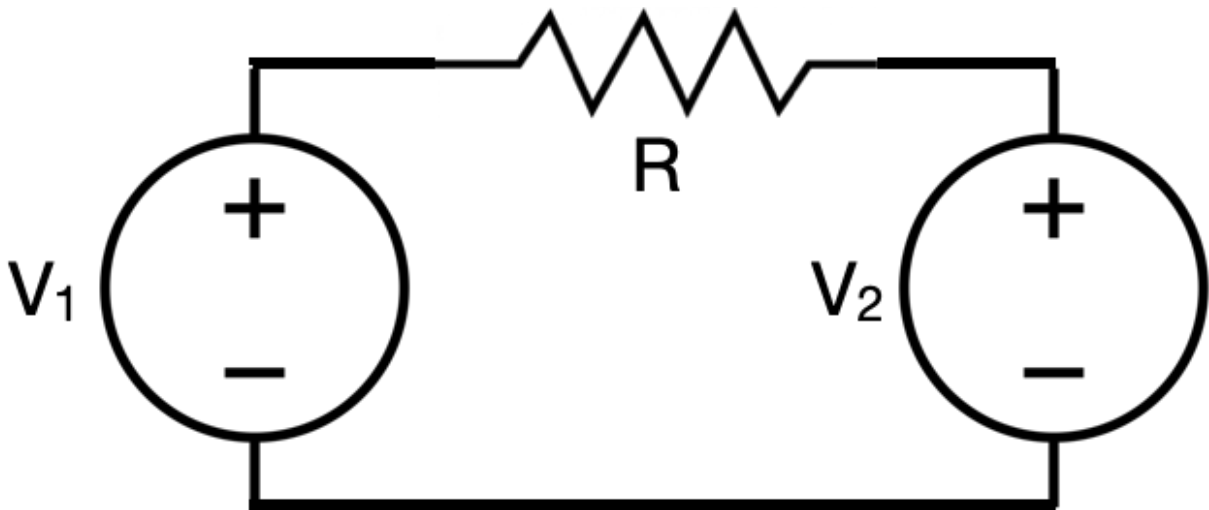

with  $R=1\Omega$ ,  $V_1 = 1V$ ,  $V_2 = 2V$ .


- 1) The absolute value of current through the resistor is [current] Amps.
- 2) The power [RDG] in R is [PR] Watts.
- 3) The power [V1DG] in  $V_1$  is [PV1] Watts.
- 4) The power [V2DG] in  $V_2$  is [PV2] Watts.

Show Answers for

ct Answer 1

### ⋮ Question

Given the following circuit,

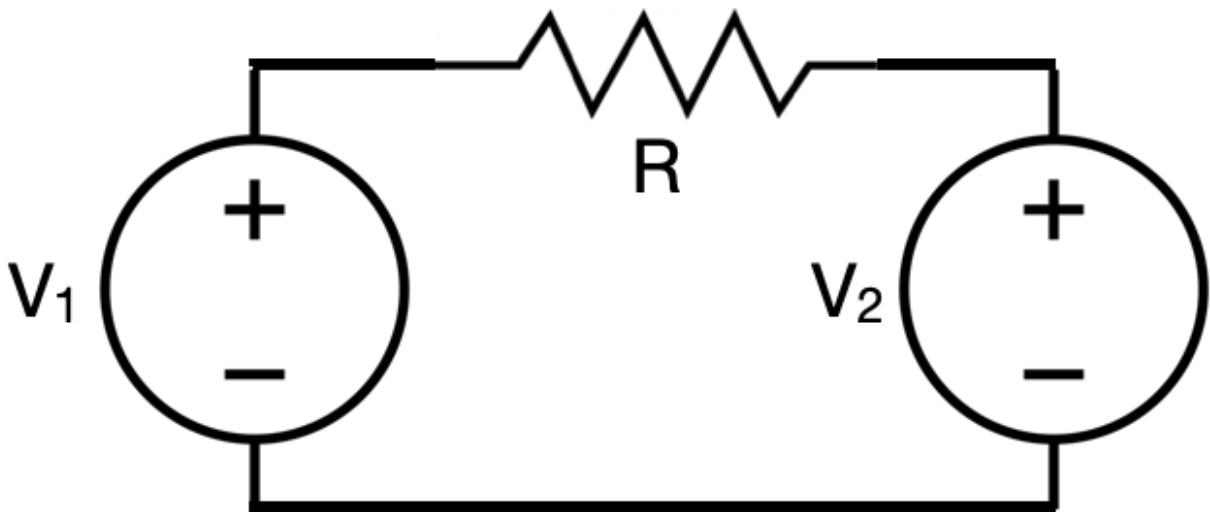

with  $R=1\Omega$ ,  $V_1 = 2V$ ,  $V_2 = 1V$ .


- 1) The absolute value of current through the resistor is [current] Amps.
- 2) The power [RDG] in  $R$  is [PR] Watts.
- 3) The power [V1DG] in  $V_1$  is [PV1] Watts.
- 4) The power [V2DG] in  $V_2$  is [PV2] Watts.

Show Answers for

ct Answer 1

⋮ Question

Given the following circuit,

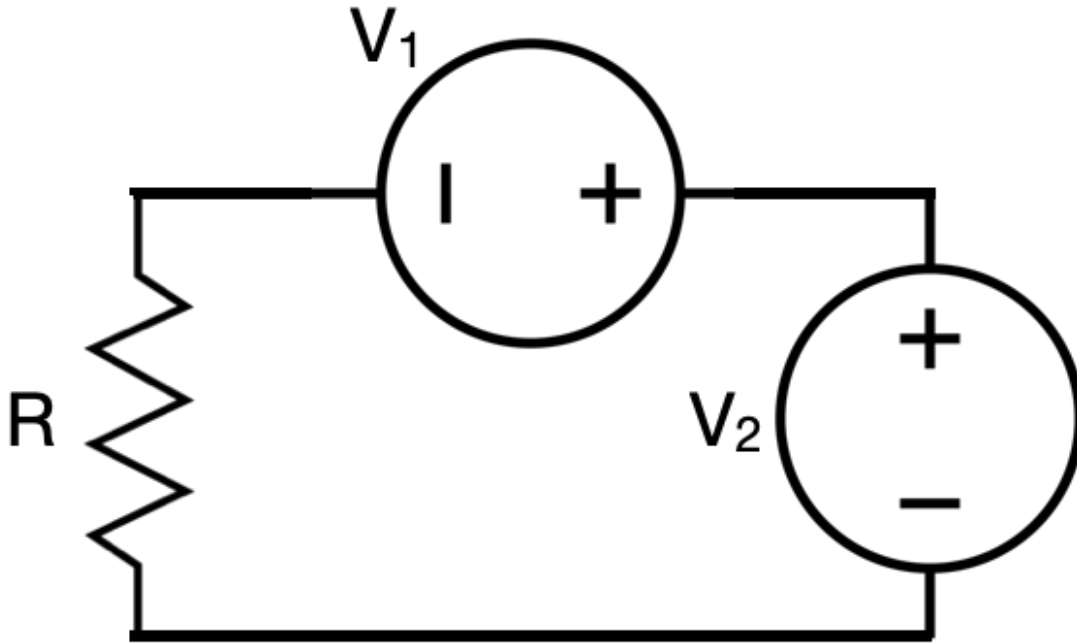

with  $R=1\Omega$ ,  $V_1 = 2V$ ,  $V_2 = 1V$ .

- 1) The absolute value of current through the resistor is [current] Amps.
- 2) The power [RDG] in R is [PR] Watts.
- 3) The power [V1DG] in  $V_1$  is [PV1] Watts.
- 4) The power [V2DG] in  $V_2$  is [PV2] Watts.

Show Answers for

ct Answer 1

⋮ Question

An inverter in this question is a device for which  $V_{in}=0V$  will result in  $V_{out} = V_{dd}$ , and for  $V_{in} = V_{dd}$  will result in  $V_{out} = 0V$


For each of the following circuits, determine if the circuit is an inverter or not.

⋮ Pick 2 questions, 1.5 pts per question



⋮ Question

Is following circuit an inverter?

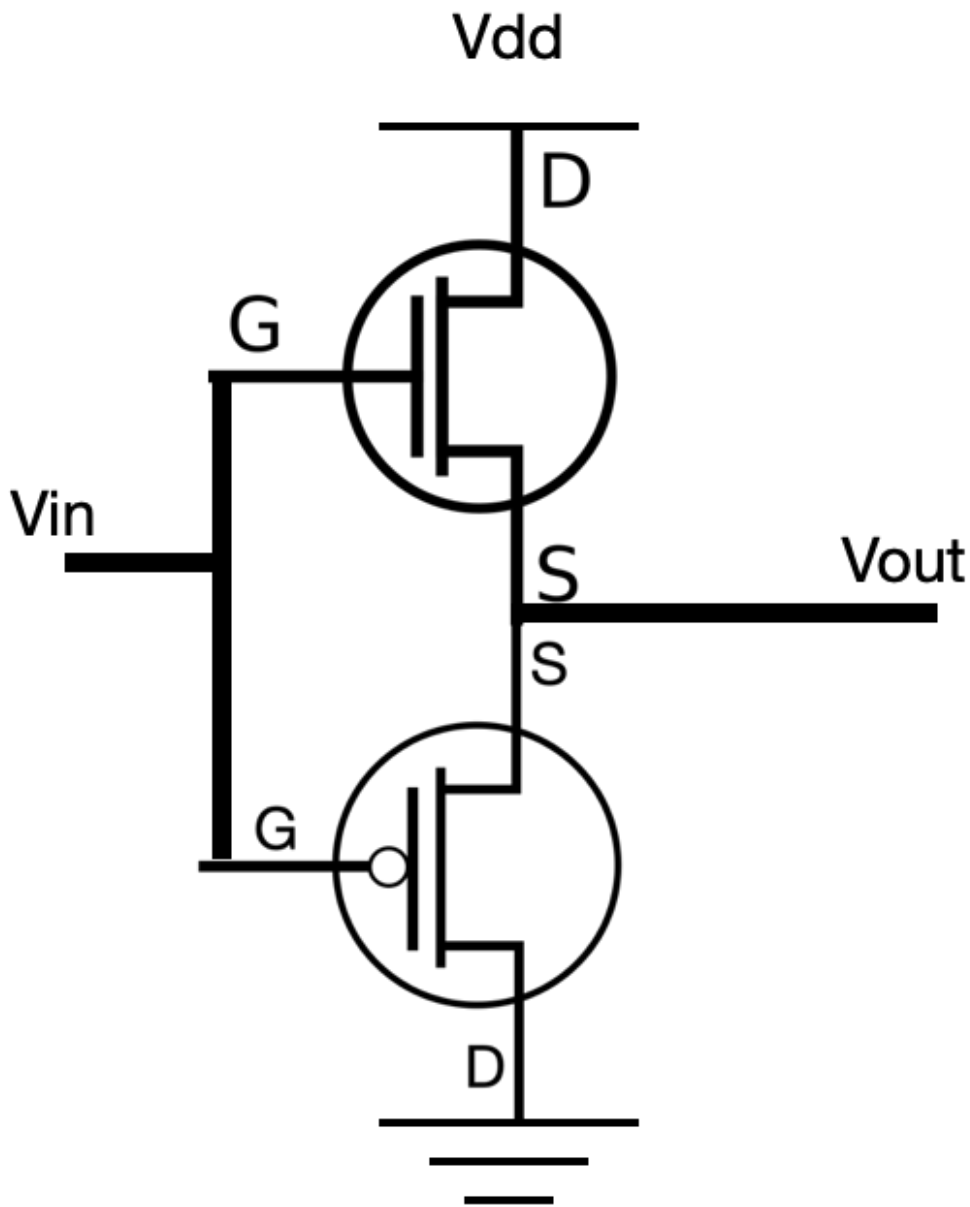


Yes

No

Correct Answer

### ⋮ Question

Is following circuit an inverter?

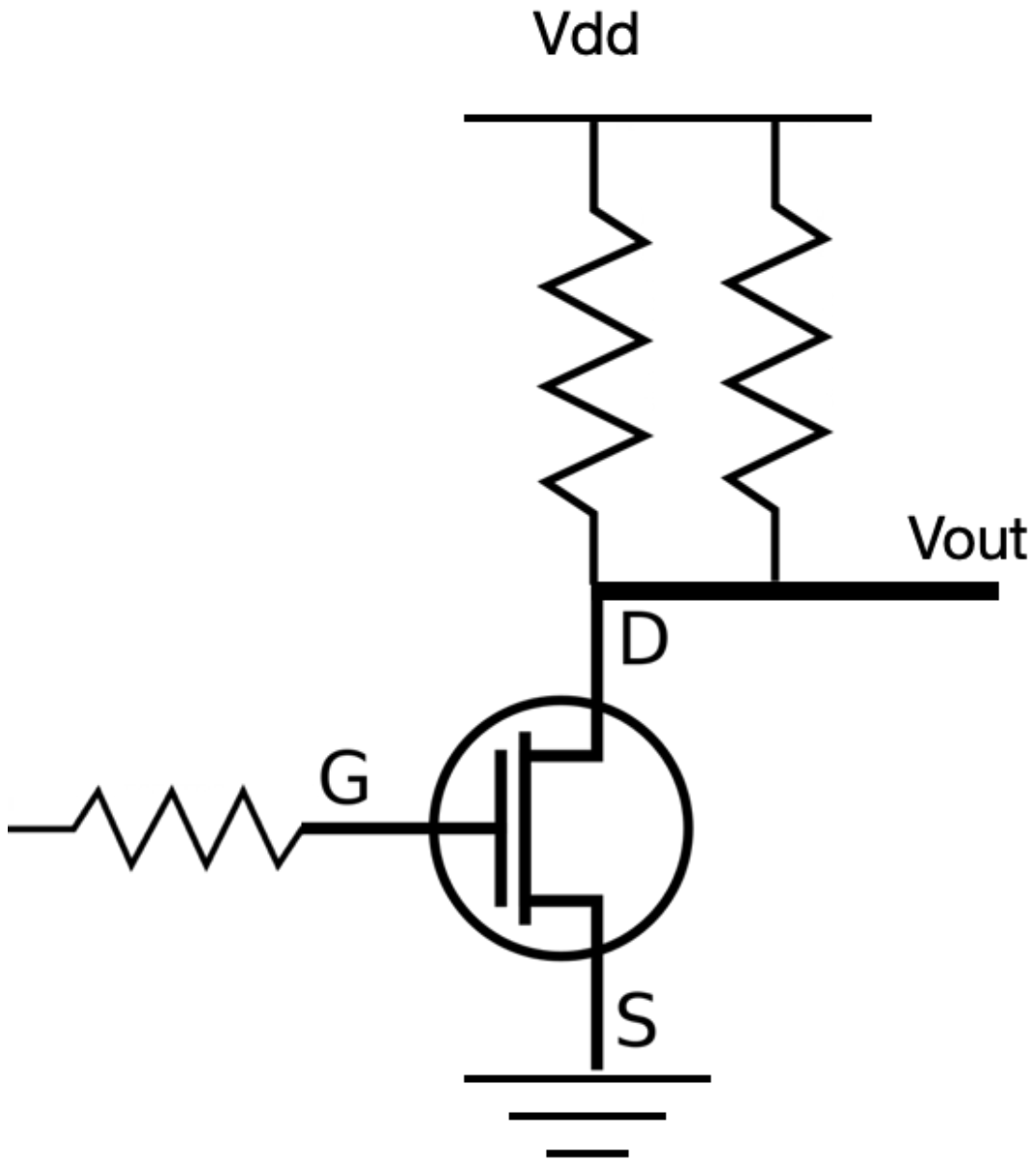


Correct Answer

Yes

No

### ⋮ Question

Is following circuit an inverter?

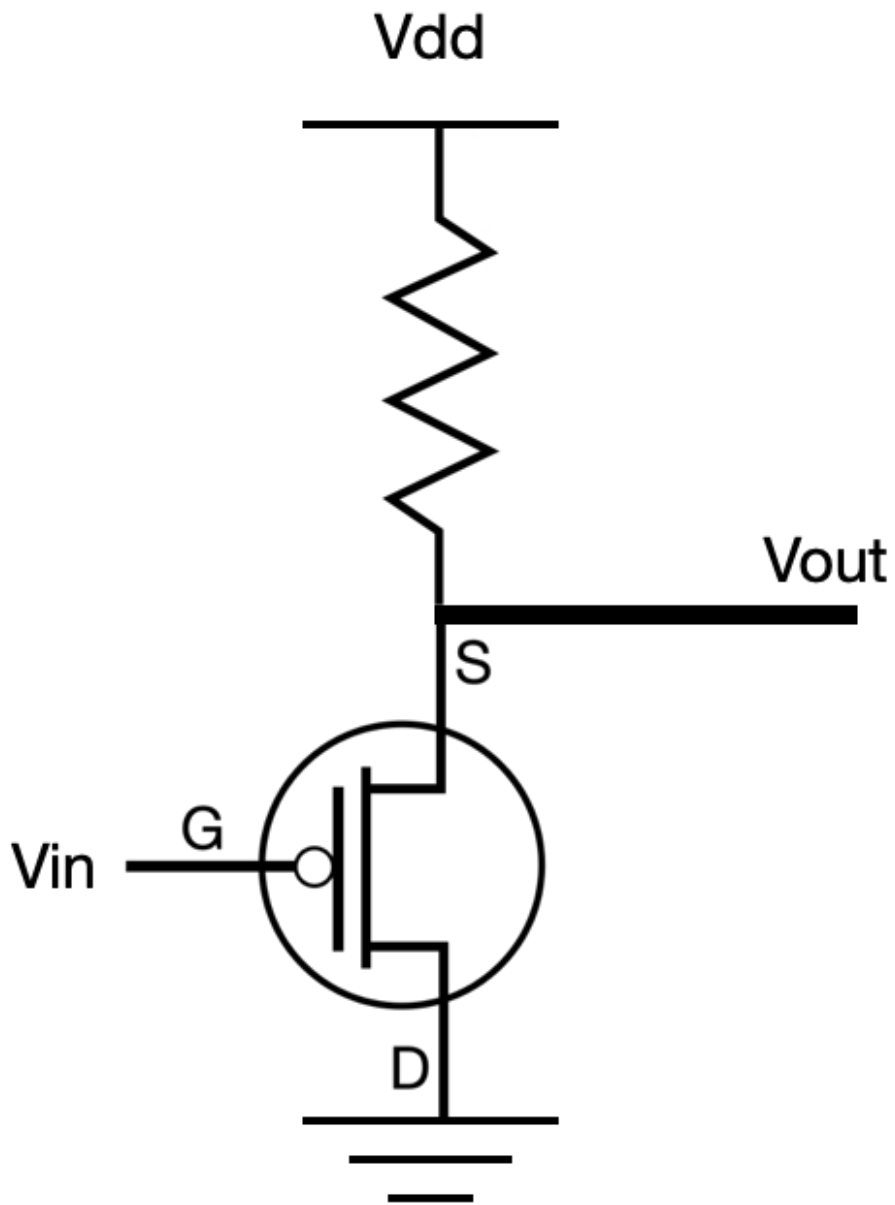


Yes

No

Correct Answer

### ⋮ Question

Is following circuit an inverter?

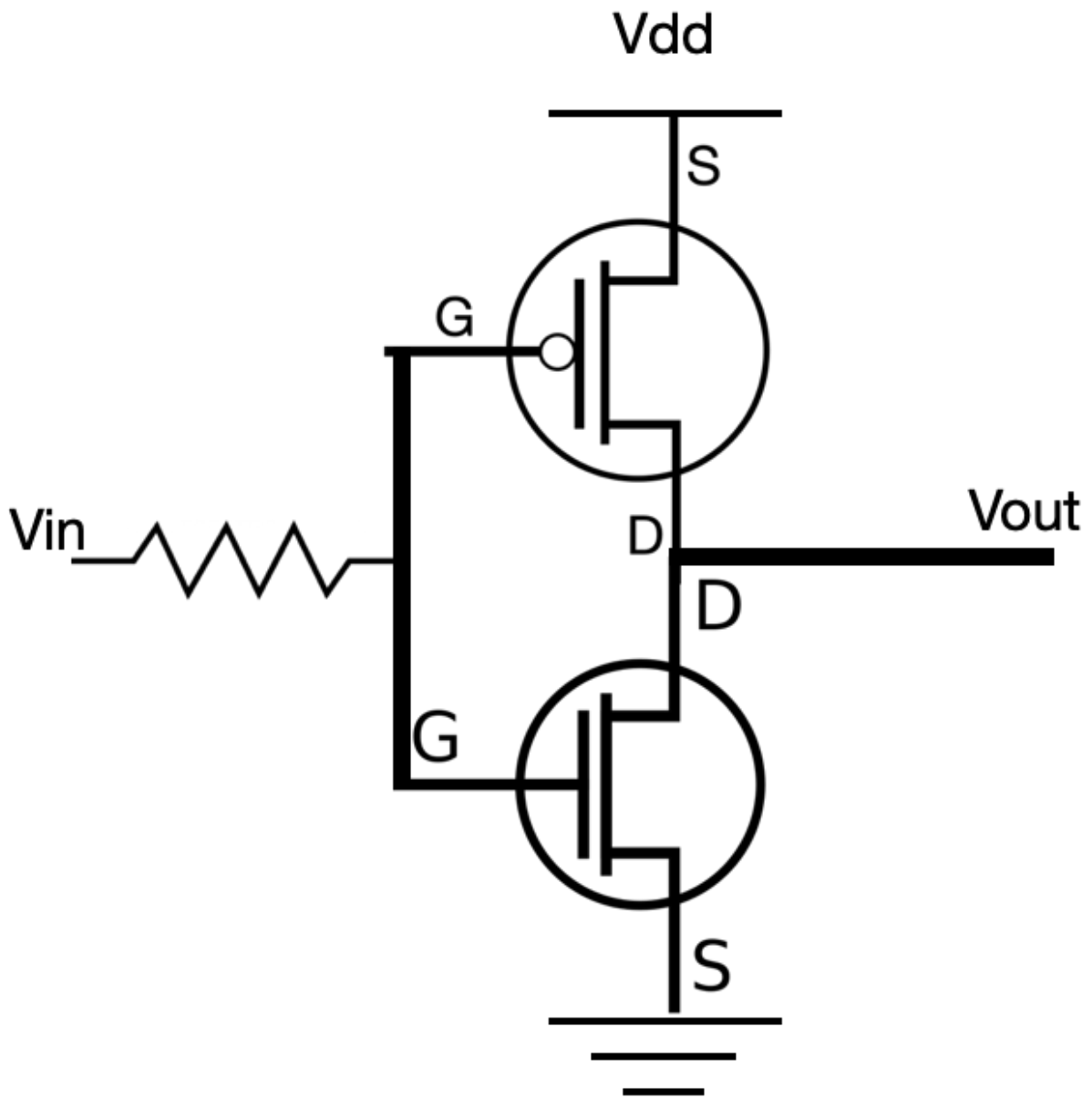

Correct Answer

Yes

No




Pick 2 questions, 1.5 pts per question



Question



Is following circuit an inverter?

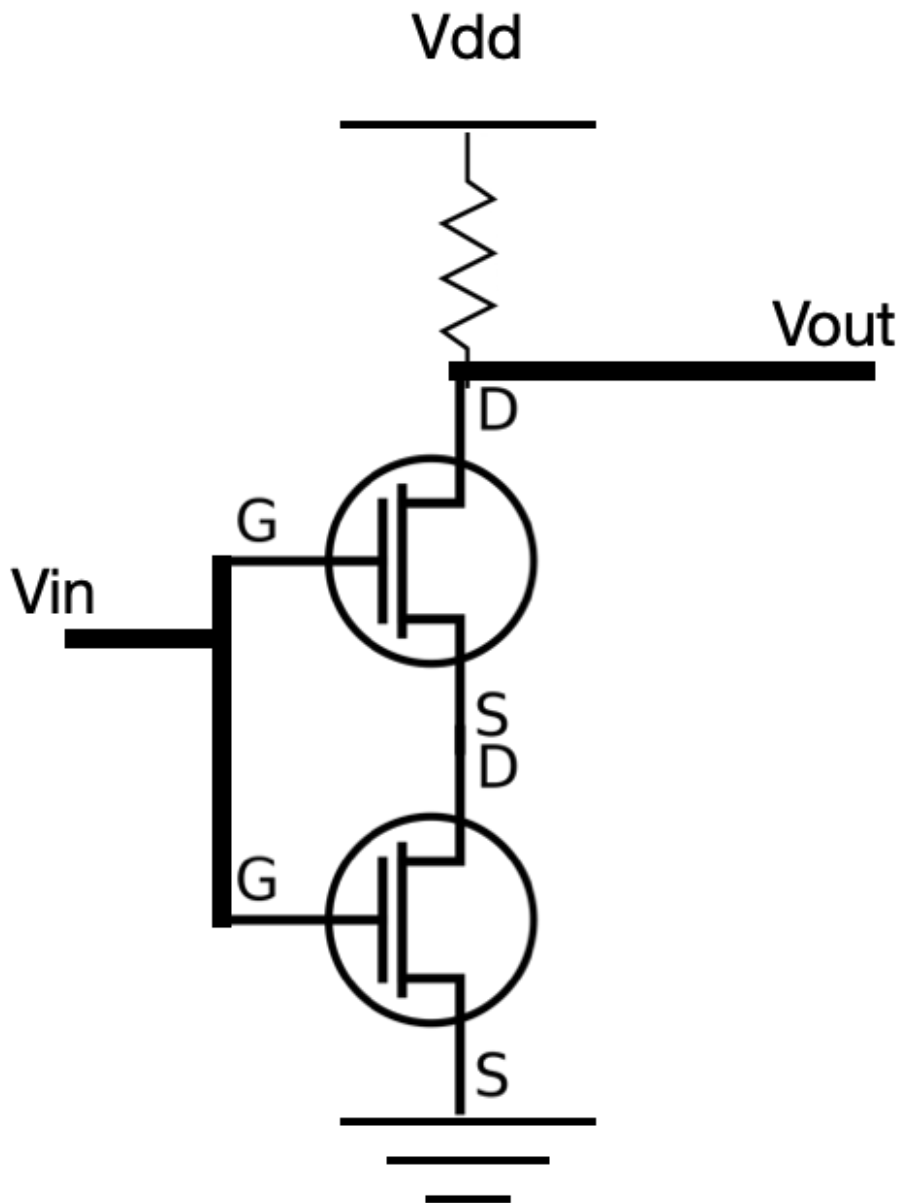


Correct Answer

Yes

No

### ⋮ Question

Is following circuit an inverter?

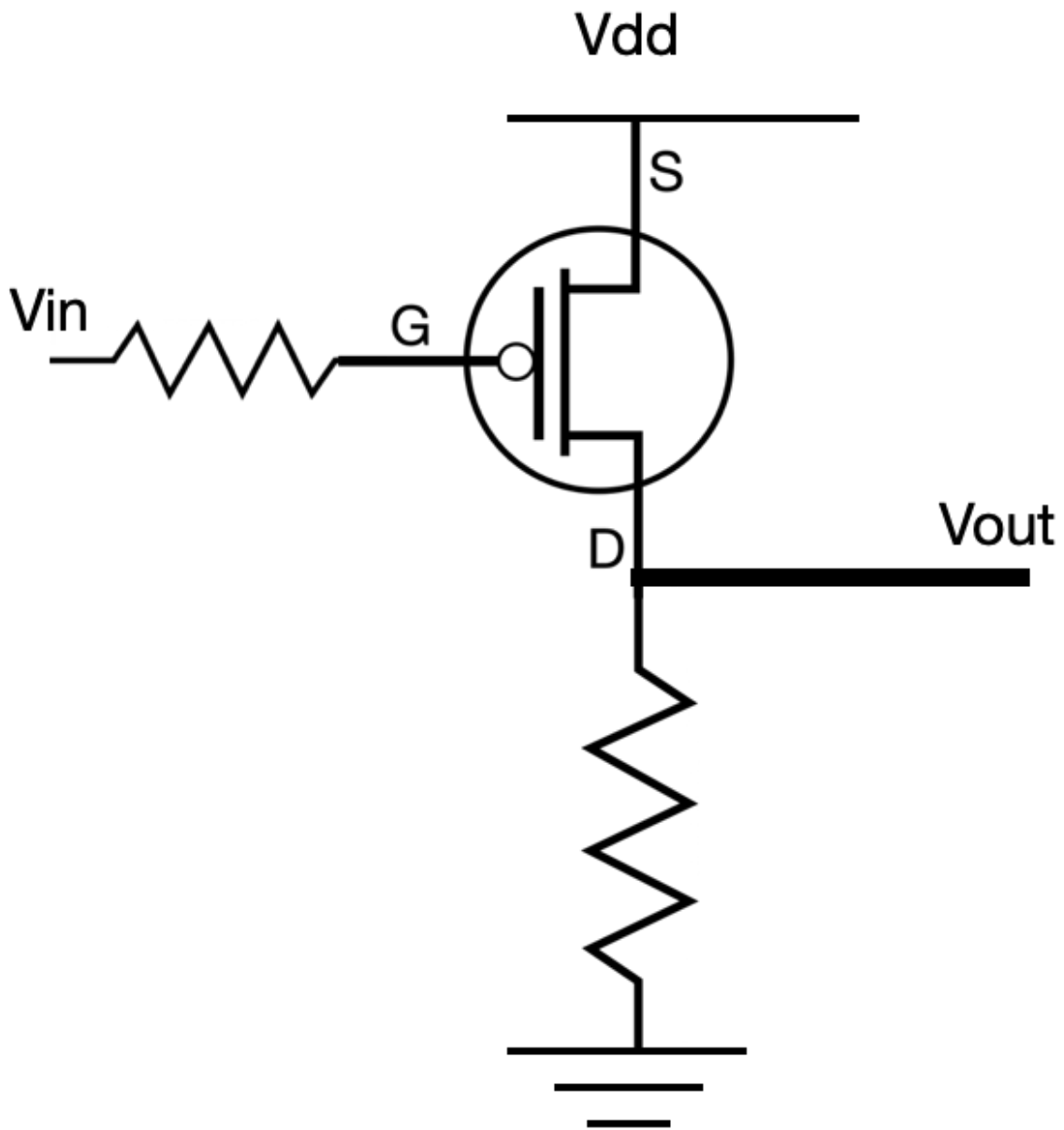


Correct Answer

Yes

No

### ⋮ Question

Is following circuit an inverter?

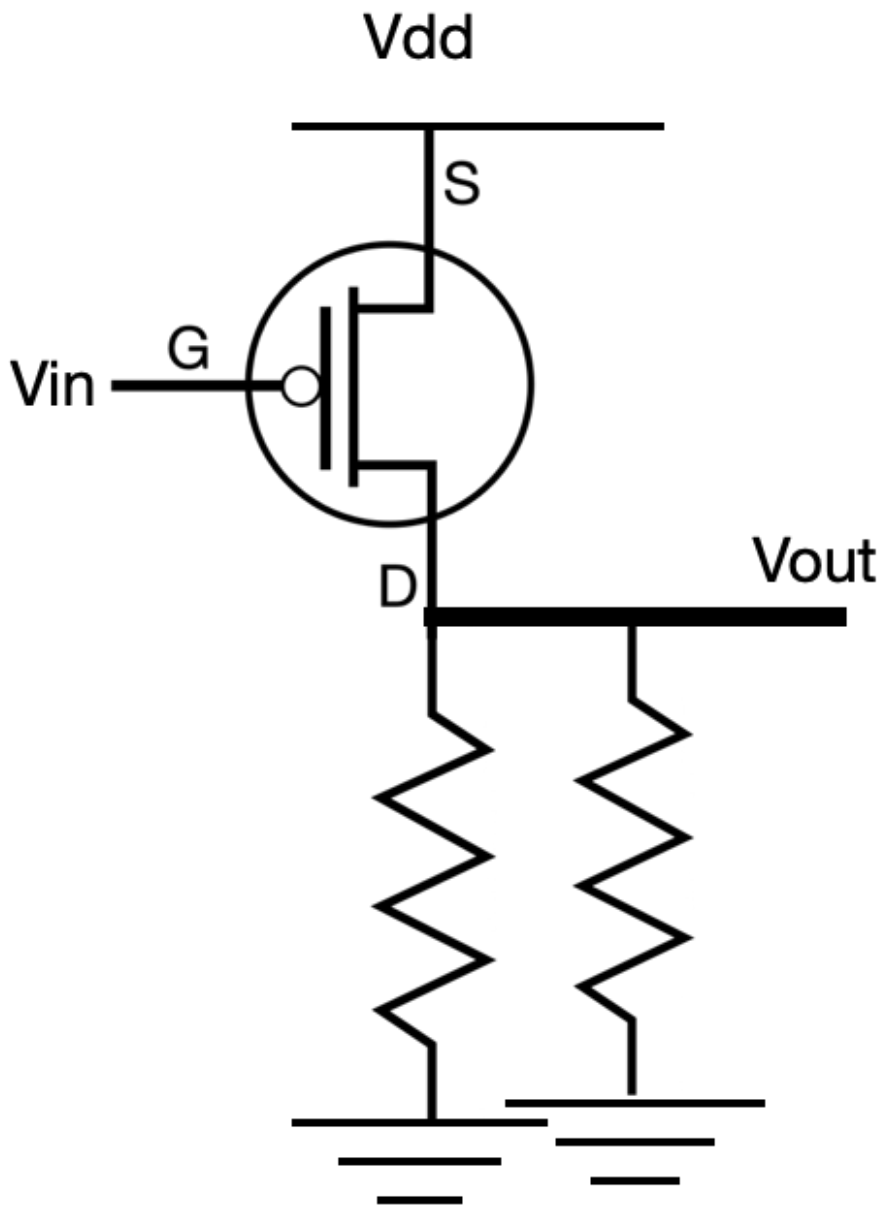


Correct Answer

Yes

No

### ⋮ Question

Is following circuit an inverter?

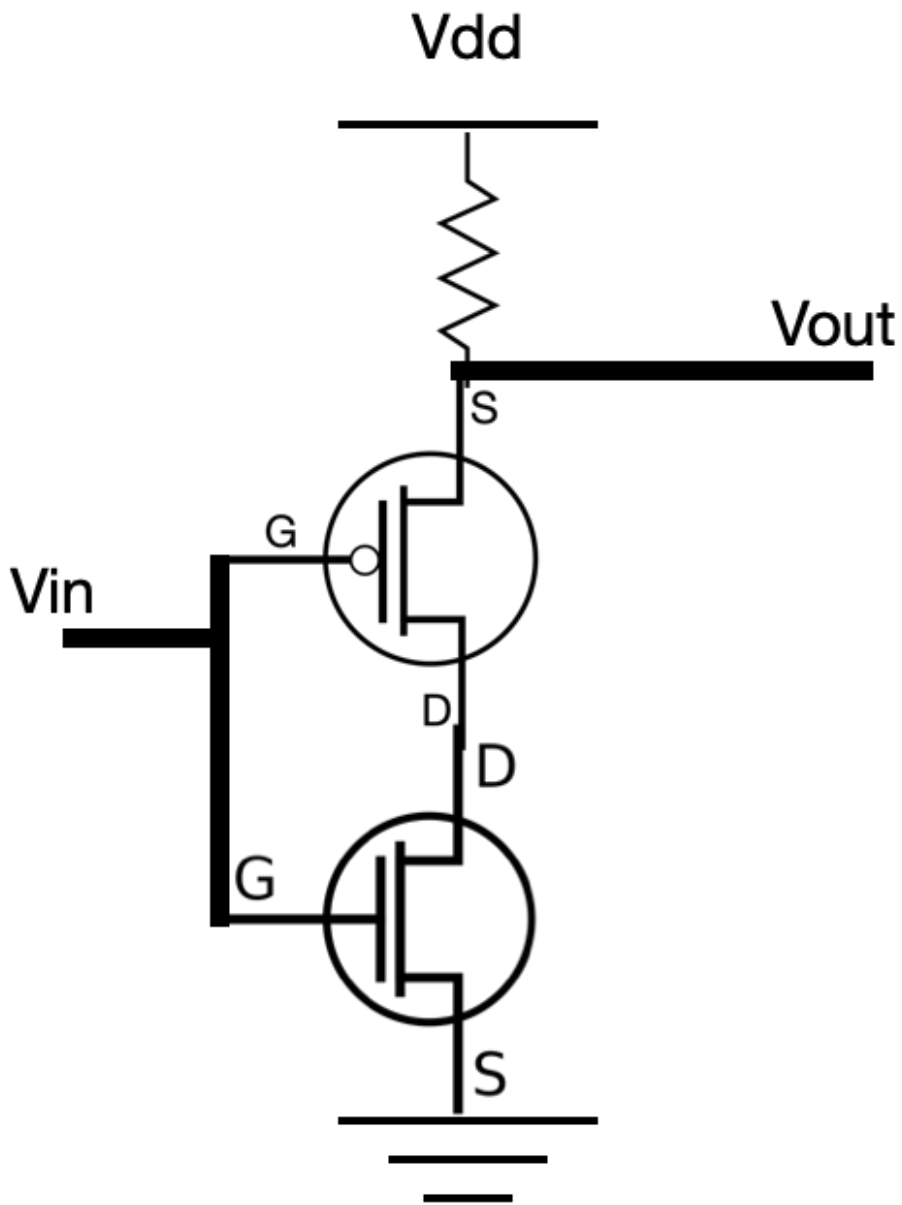

Yes

No

Correct Answer




Pick 1 questions, 4.5 pts per question




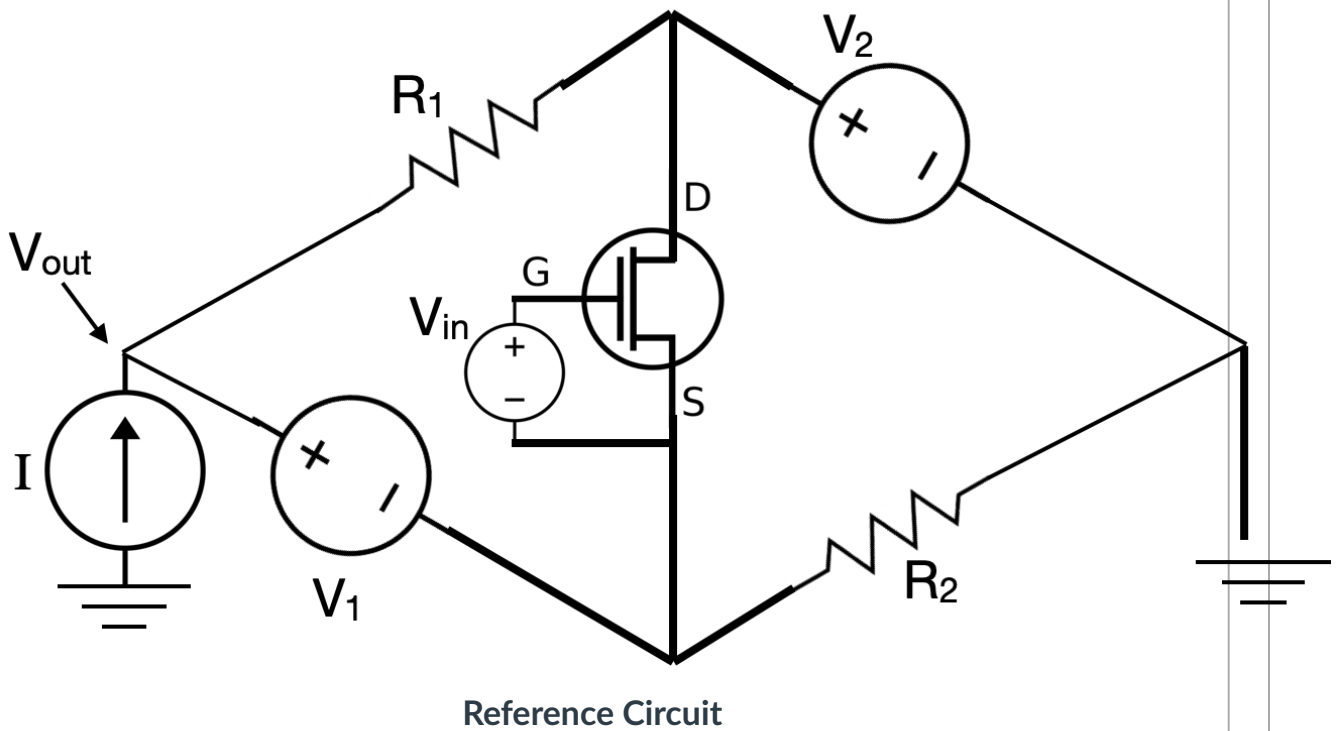Question

Consider the following circuit, with a transistor switch model (Transistor is a short circuit for  $V_{gs} \geq V_{th}$  and open circuit for  $V_{gs} < V_{th}$ ):



Below are several circuits:

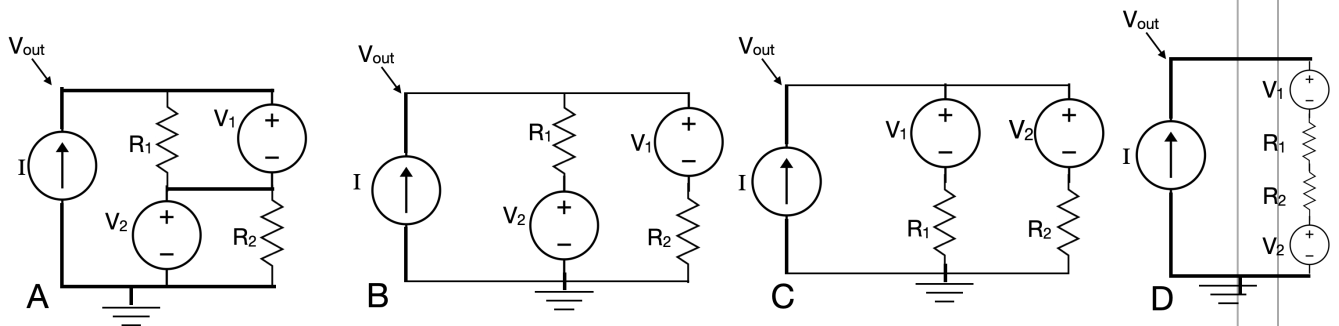


Answer the following questions:

- 1) Circuit [choose\_off] is an equivalent circuit with the same  $V_{out}$  as the reference when  $V_{in} < V_{th}$
- 2) Circuit [choose\_on] is an equivalent circuit with the same  $V_{out}$  as the reference when  $V_{in} \geq V_{th}$


Show Answers for  ▼

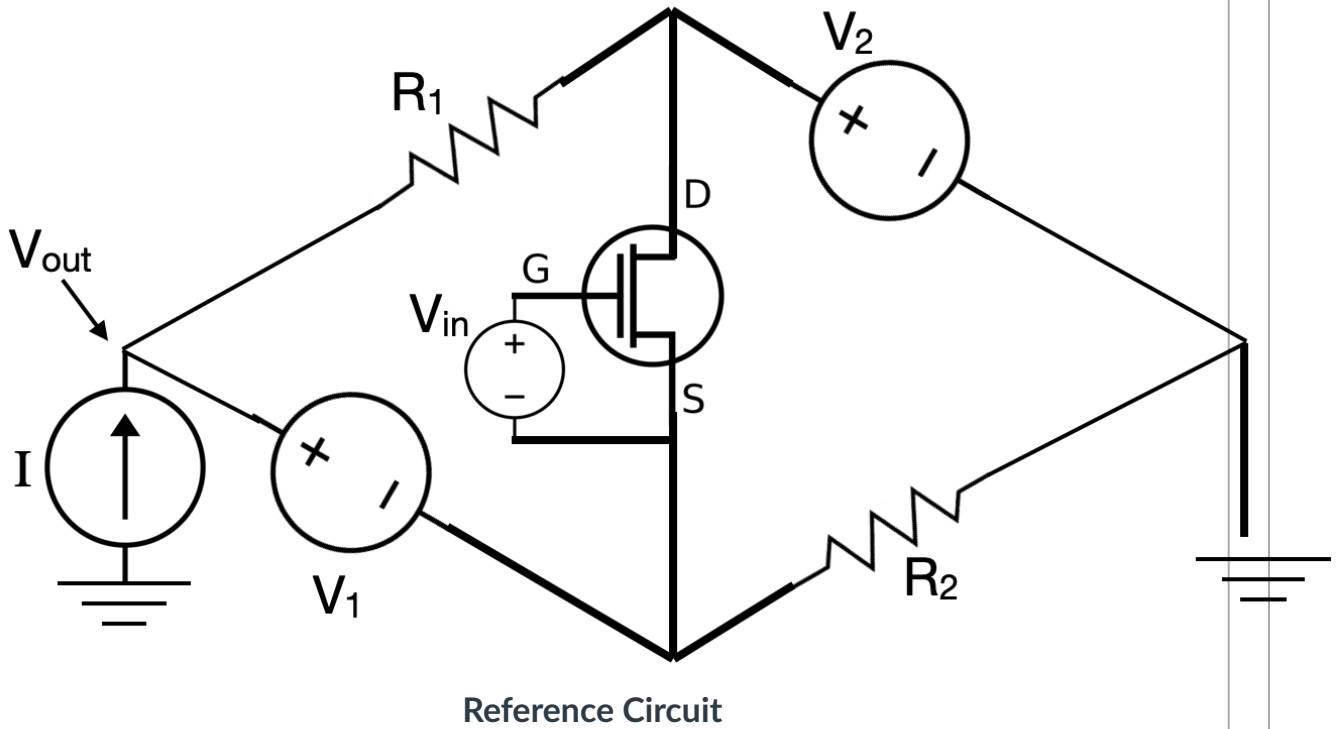Question

Consider the following circuit, with a transistor switch model (Transistor is a short circuit for  $V_{gs} \geq V_{th}$  and open circuit for  $V_{gs} < V_{th}$ ):




Below are several circuits:

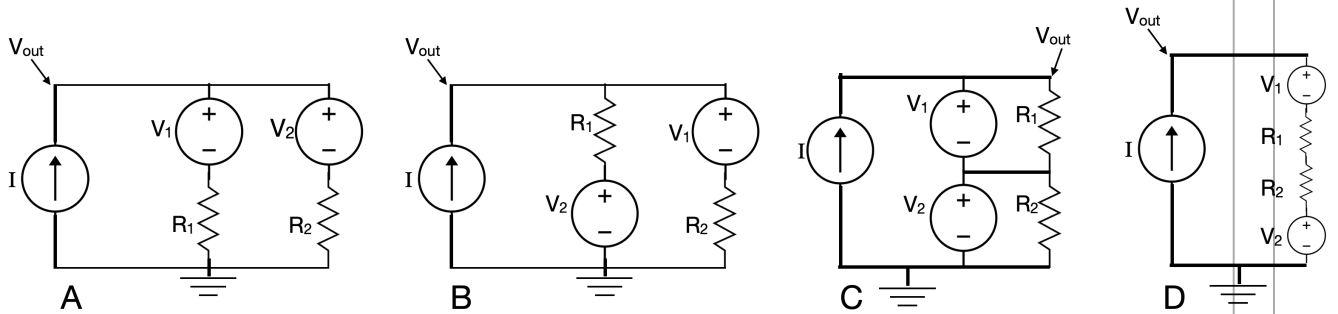

Answer the following questions:

1) Circuit [choose\_off] is an equivalent circuit with the same  $V_{out}$  as the reference when  $V_{in} < V_{th}$

2) Circuit [choose\_on] is an equivalent circuit with the same  $V_{out}$  as the reference when  $V_{in} \geq V_{th}$

Show Answers for  

Correct Answer B

### Question

The questions below are optional, with no credit (!)

### Question

0 pts

- What ..... is your name?

It is [name], King of the Britons.

- What ..... is your quest?

[Quest]. (5 words)

- What... is the air-speed velocity of an unladen swallow?

What do you mean? An [african] or [european] swallow?

Show Answers for

name



Answer Arthur

+ New Question

+ New Question Group

🔍 Find Questions

Notify users this quiz has changed

Cancel

Save